



**Channabasaveshwara Institute of Technology**  
(Affiliated to VTU, Belgaum & Approved by AICTE, New Delhi)  
(NAAC Accredited & ISO 9001:2015 Certified Institution)  
NH 206 (B.H. Road), Gubbi, Tumkur – 572 216. Karnataka.

**QMP 7.1 D/F**



**Department of Electronics & Communication Engineering**

## **VLSI LAB**

**Sub Code: 21ECL66**

**B.E - VI Semester**

**Lab Manual 2023-24**

Name : \_\_\_\_\_

USN : \_\_\_\_\_

Batch : \_\_\_\_\_ Section : \_\_\_\_\_



**Channabasaveshwara Institute of Technology**  
(Affiliated to VTU, Belgaum & Approved by AICTE, New Delhi)  
(NAAC Accredited & ISO 9001:2015 Certified Institution)  
NH 206 (B.H. Road), Gubbi, Tumkur – 572 216. Karnataka.



## Department of Electronics & Communication Engineering

# VLSI LAB

Version 2.0

APRIL 2024

### Prepared by:

Mrs. Bhavya B  
Assistant Professor  
Dept. of ECE

### Reviewed by:

Dr. Sanjeevakumar Harihar  
Associate Professor  
Dept. of ECE

### Approved by:

Dr. Thejaswini R,  
Professor & Head, Dept.  
of ECE



# Channabasaveshwara Institute of Technology

(Affiliated to VTU, Belgaum & Approved by AICTE, New Delhi)

**(NAAC Accredited & ISO 9001:2015 Certified Institution)**

NH 206 (B.H. Road), Gubbi, Tumkur – 572 216. Karnataka



## INSTITUTION VISION

To create centers of excellence in education and to serve the society by enhancing the quality of life through value based professional leadership.

## INSTITUTION MISSION

1. To provide high quality technical and professionally relevant education in a diverse learning environment.
2. To provide the values that prepare students to lead their lives with personal integrity, professional ethics and civic responsibility in a global society.
3. To prepare the next generation of skilled professionals to successfully compete in the diverse global market.
4. To promote a campus environment that welcomes and honors women and men of all races, creeds and cultures, values and intellectual curiosity, pursuit of knowledge and academic integrity and freedom.
5. To offer a wide variety of off-campus education and training programmes to individuals and groups.
6. To stimulate collaborative efforts with industry, universities, government and professional societies.
7. To facilitate public understanding of technical issues and achieve excellence in the operations of the institute.

## VISION OF THE DEPARTMENT

“To Nurture and Develop Competent Electronics and Communication Engineering

Skilled Professionals with values for the betterment of Society”

## MISSION OF THE DEPARTMENT

1. To nurture the technical/professional/engineering and entrepreneurial skills for overall self and societal upliftment through co-curricular and extra-curricular events.
2. To orient the Faculty/Student community towards the higher education, research and development activities.
3. To create the Centres of Excellence in the field of electronics and communication in collaboration with industries/Universities by training the faculty through latest technologies.
4. To impart quality technical education in the field of electronics and communication engineering to meet over the current/future global industry requirements.

## PROGRAM SPECIFIC OUTCOMES

PSO1: Build Analog and Digital Electronic systems for Multimedia Applications, VLSI and

Embedded Systems in Interdisciplinary Research / Development.

PSO2: Design and Develop Communication Systems as per Real Time Applications and Current

Trends.

## PROGRAM EDUCATIONAL OBJECTIVES

PEO1 : Provide technical solutions to real world problems in the areas of electronics

and communication by developing suitable systems.

PEO2 : Pursue engineering career in Industry and/or pursue higher education and

Research.

PEO3: Acquire and follow best professional, ethical practices in Industry relevant to

the Society.

PEO4 : Communicate effectively and Develop an ability to work in team/Individually

## PROGRAMME OUTCOMES

1. **Engineering knowledge:** Apply the knowledge of mathematics, science, engineering fundamentals, and an engineering specialization to the solution of complex engineering problems.
2. **Problem analysis:** Identify, formulate, review research literature, and analyze complex engineering problems reaching substantiated conclusions using first principles of mathematics, natural sciences, and engineering sciences.
3. **Design/development of solutions:** Design solutions for complex engineering problems and design system components or processes that meet the specified needs with appropriate consideration for the public health and safety, and the cultural, societal, and environmental considerations.
4. **Conduct investigations of complex problems:** Use research-based knowledge and research methods including design of experiments, analysis and interpretation of data, and synthesis of the information to provide valid conclusions.
5. **Modern tool usage:** Create, select, and apply appropriate techniques, resources, and modern engineering and IT tools including prediction and modeling to complex engineering activities with an understanding of the limitations.
6. **The engineer and society:** Apply reasoning informed by the contextual knowledge to assess societal, health, safety, legal and cultural issues and the consequent responsibilities relevant to the professional engineering practice.
7. **Environment and sustainability:** Understand the impact of the professional engineering solutions in societal and environmental contexts, and demonstrate the knowledge of, and need for sustainable development.
8. **Ethics:** Apply ethical principles and commit to professional ethics and responsibilities and norms of the engineering practice.
9. **Individual and team work:** Function effectively as an individual, and as a member or leader in diverse teams, and in multidisciplinary settings.
10. **Communication:** Communicate effectively on complex engineering activities with the engineering community and with society at large, such as, being able to comprehend and write effective reports and design documentation, make effective presentations, and give and receive clear instructions.
11. **Project management and finance:** Demonstrate knowledge and understanding of the engineering and management principles and apply these to one's own work, as a member and leader in a team, to manage projects and in multidisciplinary environments.
12. **Life-long learning:** Recognize the need for, and have the preparation and ability to engage in independent and life-long learning in the broadest context of technological change.

## LIST OF LAB EXPERIMENTS

Exp. No.	Name of the Experiment	Page No.
<b>ASIC Digital Design</b>		
	Introduction	1 – 3
1	<b>4Bit Adder</b> <ul style="list-style-type: none"> <li>Write Verilog Code</li> <li>Verify the Functionality using Test-bench</li> <li>Synthesize the design by setting proper constraints and obtain the netlist.</li> </ul> <p>From the report generated identify Critical path, Maximum delay, Total number of cells, Power requirement and Total area required</p>	4 – 6
2	<b>4 – Bit Booth Multiplier</b> <ul style="list-style-type: none"> <li>Write Verilog Code</li> <li>Verify the Functionality using Test – bench</li> <li>Synthesize the design by setting proper constraints and obtain the netlist.</li> </ul> <p>From the report generated identify Critical path, Maximum delay, Total number of cells, Power requirement and Total area required.</p>	7 - 9
3	<b>32Bit ALU Supporting 4-Logical and 4-Arithmetic operations, using case and ifstatement for ALU Behavioral Modeling</b> <ul style="list-style-type: none"> <li>Write Verilog Code</li> <li>Verify functionality using Test-bench</li> <li>Synthesize the design targeting suitable library and by setting area and timing constraints</li> <li>Tabulate the Area, Power and Delay for the Synthesized netlist</li> <li>Identify Critical path</li> </ul>	10 - 13
4	<b>Latch and Flip-Flop</b> Synthesize the design and compare the synthesis report (D, SR, JK)	14 - 20
<b>ASIC Analog Design</b>		
5	<b>Introduction &amp;</b> <b>a)</b> Capture the schematic of CMOS inverter with load capacitance of 0.1pF and set the widths of Inverter with $W_n = W_p$ , $W_n = 2W_p$ , $W_n = W_p/2$ and length at selected technology. Carry out the following: <ol style="list-style-type: none"> <li>Set the input signal to a pulse with rise time, fall time of 1ns and pulse width of 10ns and the time period of 20ns and plot the input voltage and output voltage of designed inverter?</li> <li>From the simulation result compute <math>t_{pHL}</math>, <math>t_{pLH}</math> and <math>t_d</math> for all three geometrical settings of width?</li> <li>Tabulate the results of delay and find the best geometry for minimum delay for CMOS inverter?</li> </ol> <b>b)</b> Draw layout of inverter with $W_p/W_n = 40/20$ , use optimum layout methods. Verify for DRC and LVS, extract parasitic and perform post layout simulations, compare the results with prelayout simulations. Record the observations.	21 - 27
6	<b>a)</b> Capture the schematic of 2-input CMOS NAND gate having similar delay as that of CMOS inverter computed in experiment above. Verify the functionality of NAND gate and also find out the delay $t_d$ for all four possible combinations of input vectors. Table the results. Increase the drive strength to 2X and 4X and tabulate the results. <b>b)</b> Draw the layout of NAND with $W_p/W_n = 40/20$ , use optimum layout methods. Verify for DRC and LVS, extract parasitic and perform post layout simulations, compare the results with prelayout simulations. Record the observations.	28 – 34
7	<b>a)</b> Capture schematic of Common Source Amplifier with PMOS Current Mirror Load and find its transient response and AC response? Measure the Unit Gain Bandwidth (UGB), amplification factor by varying transistor geometries, study the impact of variation in width to UGB. <b>b)</b> Draw Layout of common source amplifier, use optimum layout methods. Verify for DRC & LVS, extract parasitic and perform post layout simulations, compare the results with pre-layout simulations. Record the observations.	35 – 39

8	<p><b>a)</b> Capture schematics of two-stage operational amplifier and measure the following:</p> <ol style="list-style-type: none"> <li>UGB</li> <li>dB Bandwidth</li> <li>Gain Margin and phase margin with and without coupling capacitance</li> <li>Use the op-amp in the inverting and non-inverting configuration and verify its functionality.</li> <li>Study the UGB, 3dB bandwidth, gain and power requirement in op-amp by varying the stage wise transistor geometries and record the observations.</li> </ol> <p><b>b)</b> Draw layout of two-stage operational amplifier with minimum transistor width set to 300 (in 180/90/45 nm technology), choose appropriate transistor geometries as per the results obtained in part a. Use optimum layout methods. Verify for DRC and LVS, extract parasitic and perform post layout simulations, compare the results with pre-layout simulations. Record the observations.</p>	40 – 46
<b>Demonstration Experiments ( For CIE )</b>		
9	<p>UART</p> <ul style="list-style-type: none"> <li>Write Verilog Code</li> <li>Verify the Functionality using Test-bench</li> <li>Synthesize the design targeting suitable library and by setting area and timing constraints</li> <li>Tabulate the Area, Power and Delay for the Synthesized netlist</li> <li>Identify Critical path</li> </ul>	47 – 54
10	<p>For synthesized netlist carry out the following:</p> <ul style="list-style-type: none"> <li>Floor planning</li> <li>Placement and Routing</li> <li>Record the parameters such as no. of metal layers used for routing, flip method for placement of standard cells</li> <li>Physical Verification and record the DRC and LVS reports</li> <li>Generate GDSII</li> </ul>	55 – 84

## SYLLABUS

VLSI Laboratory				
Course Code		21ECL66	CIE Marks	50
Teaching Hours/Week (L: T: P: S)		0:0:2:0	SEE Marks	50
Credits		1	Exam Hours	3
Sl.No.	Experiments			
ASIC Digital Design				
1	4-Bit Adder <ul style="list-style-type: none"><li>• Write Verilog Code</li><li>• Verify the Functionality using Test-bench</li><li>• Synthesize the design by setting proper constraints and obtain the netlist.</li></ul> From the report generated identify Critical path, Maximum delay, Total number of cells, Powerrequirement and Total area required			
2	4-Bit Booth Multiplier <ul style="list-style-type: none"><li>• Write Verilog Code</li><li>• Verify the Functionality using Test-bench</li><li>• Synthesize the design by setting proper constraints and obtain the netlist.</li></ul> From the report generated identify Critical path, Maximum delay, Total number of cells, Power requirement and Total area required			
3	32-Bit ALU Supporting 4-Logical and 4-Arithmetic operations, using case and if statement for ALUBehavioral Modeling <ul style="list-style-type: none"><li>• Write Verilog Code</li><li>• Verify functionality using Test-bench</li><li>• Synthesize the design targeting suitable library and by setting area and timing constraints</li><li>• Tabulate the Area, Power and Delay for the Synthesized netlist</li><li>• Identify Critical path</li></ul>			
4	Latch and Flip-Flop <ul style="list-style-type: none"><li>• Synthesize the design and compare the synthesis report (D, SR, JK)</li></ul>			
ASIC Analog Design				
5	a) Capture the schematic of CMOS inverter with load capacitance of 0.1pF and set the widths ofInverter with $W_n = W_p$ , $W_n = 2W_p$ , $W_n = W_p/2$ and length at selected technology. Carry out the following: <ul style="list-style-type: none"><li>i. Set the input signal to a pulse with rise time, fall time of 1ns and pulse width of 10ns and the time period of 20ns and plot the input voltage and output voltage of designed inverter?</li><li>ii. From the simulation result compute <math>t_{pHL}</math>, <math>t_{pLH}</math> and <math>t_d</math> for all three geometrical settings of width?</li><li>iii. Tabulate the results of delay and find the best geometry for minimum delay for CMOS inverter?</li></ul> b) Draw layout of inverter with $W_p/W_n = 40/20$ , use optimum layout methods. Verify for DRC and LVS, extract parasitic and perform post layout simulations, compare the results with pre-layout simulations. Record the observations.			
6	a) Capture the schematic of 2-input CMOS NAND gate having similar delay as that of CMOS inverter computed in experiment above. Verify the functionality of NAND gate and also find out the delay $t_d$ for all four possible combinations of input vectors. Table the results. Increase the drive strength to 2X and 4X and tabulate the results. b) Draw the layout of NAND with $W_p/W_n = 40/20$ , use optimum layout methods. Verify for DRC and LVS, extract parasitic and perform post layout simulations, compare the results with pre- layout simulations. Record the observations.			
7	a) Capture schematic of Common Source Amplifier with PMOS Current Mirror Load and find its transient response and AC response? Measure the Unit Gain Bandwidth (UGB), amplification factor by varying transistor geometries, study the impact of variation in width to UGB. b) Draw Layout of common source amplifier, use optimum layout methods. Verify for DRC & LVS, extract parasitic and perform post layout simulations, compare the results with pre-layout simulations. Record the observations.			



8	<p>a) Capture schematics of two-stage operational amplifier and measure the following:</p> <ol style="list-style-type: none"> <li>UGB</li> <li>dB Bandwidth</li> <li>Gain Margin and phase margin with and without coupling capacitance</li> <li>Use the op-amp in the inverting and non-inverting configuration and verify its functionality.</li> <li>Study the UGB, 3dB bandwidth, gain and power requirement in op-amp by varying the stage wise transistor geometries and record the observations.</li> </ol> <p>b) Draw layout of two-stage operational amplifier with minimum transistor width set to 300 (in 180/90/45 nm technology), choose appropriate transistor geometries as per the results obtained in part a. Use optimum layout methods. Verify for DRC and LVS, extract parasitic and perform post layout simulations, compare the results with pre-layout simulations. Record the observations.</p>
<b>Demonstration Experiments ( For CIE )</b>	
9	<p>UART</p> <ul style="list-style-type: none"> <li>Write Verilog Code</li> <li>Verify the Functionality using Test-bench</li> <li>Synthesize the design targeting suitable library and by setting area and timing constraints</li> <li>Tabulate the Area, Power and Delay for the Synthesized netlist, Identify Critical path</li> </ul>
10	<p>For synthesized netlist carry out the following:</p> <ul style="list-style-type: none"> <li>Floor planning</li> <li>Placement and Routing</li> <li>Record the parameters such as no. of metal layers used for routing, flip method for placement of standard cells</li> <li>Physical Verification and record the DRC and LVS reports</li> <li>Generate GDSII</li> </ul>
11	<p>Design and characterize 6T binary SRAM cell and measure the following:</p> <ul style="list-style-type: none"> <li>Read Time, Write Time, SNM, Power</li> <li>Draw Layout of 6T SRAM, use optimum layout methods. Verify for DRC &amp; LVS, extract parasitic and perform post layout simulations, compare the results with pre-layout simulations. Record the observations.</li> </ul>

#### Assessment Details (both CIE and SEE)

The weightage of Continuous Internal Evaluation (CIE) is 50% and for Semester End Exam (SEE) is 50%. The minimum passing mark for the CIE is 40% of the maximum marks (20 marks). A student shall be deemed to have satisfied the academic requirements and earned the credits allotted to each course. The student has to secure not less than 35% (18 Marks out of 50) in the semester-end examination (SEE).

#### Continuous Internal Evaluation (CIE):

CIE marks for the practical course is **50 Marks**.

The split-up of CIE marks for record/ journal and test are in the ratio **60:40**.

- Each experiment to be evaluated for conduction with observation sheet and record write-up. Rubrics for the evaluation of the journal/write-up for hardware/software experiments designed by the faculty who is handling the laboratory session and is made known to students at the beginning of the practical session.
- Record should contain all the specified experiments in the syllabus and each experiment write-up will be evaluated for 10 marks.
- Total marks scored by the students are scaled down to 30 marks (60% of maximum marks).
- Weightage to be given for neatness and submission of record/write-up on time.
- Department shall conduct 02 tests for 100 marks, the first test shall be conducted after the 8<sup>th</sup> week of the semester and the second test shall be conducted after the 14<sup>th</sup> week of the semester.
- In each test, test write-up, conduction of experiment, acceptable result, and procedural knowledge will carry a weightage of 60% and the rest 40% for viva-voce.
- The suitable rubrics can be designed to evaluate each student's performance and learning ability. Rubrics suggested in Annexure-II of Regulation book
- The average of 02 tests is scaled down to **20 marks** (40% of the maximum marks).

The Sum of scaled-down marks scored in the report write-up/journal and average marks of two tests is the total CIE marks scored by the student.

**Semester End Evaluation (SEE):**

SEE marks for the practical course is 50 Marks.

SEE shall be conducted jointly by the two examiners of the same institute, examiners are appointed by the University

All laboratory experiments are to be included for practical examination.

(Rubrics) Breakup of marks and the instructions printed on the cover page of the answer script to be strictly adhered to by the examiners. **OR** based on the course requirement evaluation rubrics shall be decided jointly by examiners.

Students can pick one question (experiment) from the questions lot prepared by the internal /external examiners jointly.

Evaluation of test write-up/ conduction procedure and result/viva will be conducted jointly by examiners.

General rubrics suggested for SEE are mentioned here, writeup-20%, Conduction procedure and result in -60%, Viva-voce 20% of maximum marks. SEE for practical shall be evaluated for 100 marks and scored marks shall be scaled down to 50 marks (however, based on course type, rubrics shall be decided by the examiners).

Change of experiment is allowed only once and 15% Marks allotted to the procedure part to be made zero.

The duration of SEE is 03 hours.

Rubrics suggested in Annexure-II of Regulation book

## Department of Electronics and Communication Engineering

### VLSI LAB

### Course Objectives and Outcomes

**Course objectives:** This course will enable students to:

- Design, model, simulate and verify digital circuits.
- Design layouts and perform physical verification of CMOS digital circuits.
- Perform ASIC design flow and understand the process of synthesis, synthesis constraints and evaluating the synthesis reports to obtain optimum gate level netlist.
- Perform RTL-GDSII flow and understand the stages in ASIC.

**Course outcomes:** After studying this course, students will be able to:

- Design and simulate combinational and sequential digital circuits using Verilog HDL.
- Understand the synthesis process of digital circuits using EDA tool.
- Perform ASIC design flow and understand the process of synthesis, synthesis constraints and evaluating the synthesis reports to obtain optimum gate level netlist.
- Design and simulate basic CMOS circuits like inverter, common source amplifier, differential amplifier, SRAM.
- Perform RTL\_GDSII flow and understand the stages in ASIC design.

## INSTRUCTIONS TO THE STUDENT

1. Come prepared to the lab with relevant theory about the experiment you are conducting.
2. Each experiment will be evaluated for 20 marks. More weightage will be given for preparation and understanding.
3. Handle the desktop system and interfacing boards with care
4. Do not delete or change the system settings and files.
5. For any missing items, penalty will be imposed on the respective batch.
6. Maintain professional attitude and discipline during lab sessions.

---

## INTRODUCTION

VLSI stands for Very Large Scale Integration, which is a technology used to create integrated circuits (ICs) by combining thousands or millions of transistors into a single chip. VLSI technology has revolutionized the electronics industry by enabling the production of compact, powerful and low-cost microprocessors, memory chips, digital signal processors, and other advanced electronic devices.

As of 2020, the scale of integration in VLSI technology has reached nanometer level processes, with feature sizes on the order of 7-5 nm, allowing for the integration of billions of transistors on a single chip. The latest processors and integrated circuits are being manufactured using 7nm and 5nm process nodes, enabling greater performance and power efficiency.

CIT GUBBI ECE DEPT

# **ASIC Design Flow**

**(Digital Design)**

**PART - A**


### What Is an ASIC ?

An ASIC (Application-Specific Integrated Circuit) is a type of integrated circuit (IC) that is designed to perform a specific task or function. It is customized for a particular application, unlike general-purpose ICs such as microprocessors and memory chips.

ASICs are typically used in high-performance applications where specific processing requirements need to be met, such as in networking, telecommunications, and consumer electronics. ASICs are designed and manufactured for a specific customer or application and can include digital, analog, and mixed-signal components on a single chip.

The complete ASIC design process can be divided into two parts.

1. Front End Design
2. Back End Design

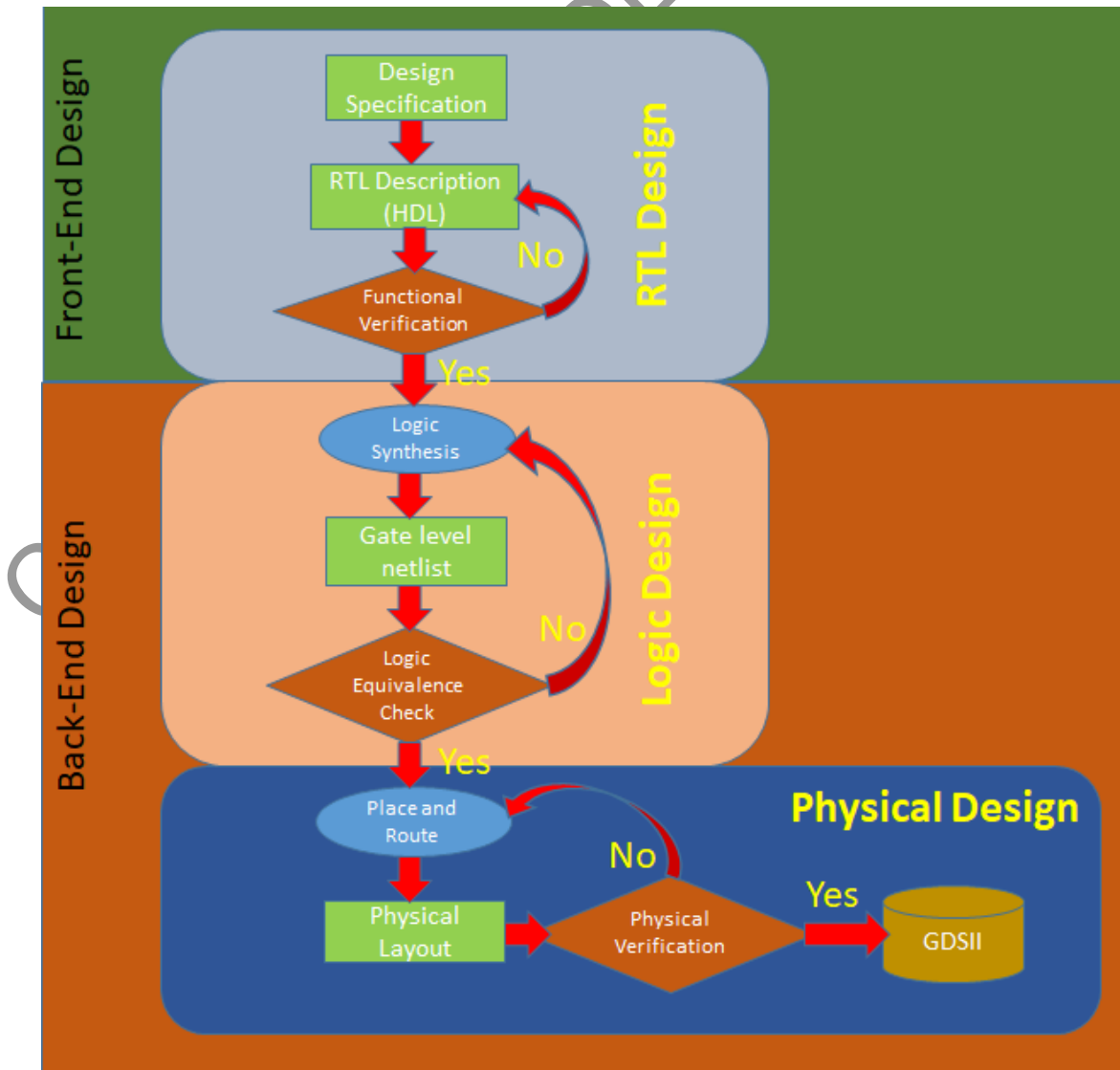

#### Tool Required:

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

## Lab 1: 4-Bit Adder

**Aim:** To write a verilog code for 4bit adder and verify the functionality using Test bench.

- Synthesize, Analyse Reports and Netlist, Critical Path and Max Operating Frequency.
- From the report generated find the total number of cells, power requirement and total area requirement.

**Tool Required:**

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

**Design Information and Block Diagram:**

A full adder is a combinational circuit that performs the arithmetic sum of three input bits  $A_i$ , addend  $B_i$  and carry in  $C_i$  from the previous adder. Its results contain the sum  $S_i$  and the carryout,  $C_{out}$  to the next stage. So to design a 4-bit adder circuit we start by designing the 1-bit full adder then connecting the four 1-bit full adders to get the 4-bit adder as shown in the diagram below. For the 1-bit full adder, the design begins by drawing the Truth Table for the three input and the corresponding output SUM and CARRY.

Fig: Diagram and truth table of full adder

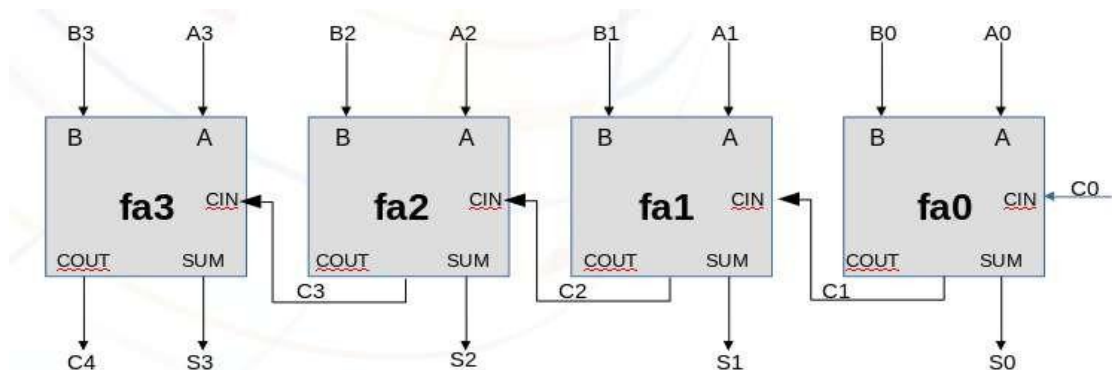
 


Fig: Diagram of 4 Bit Adder

**Creating a Work space :**

- Create a new sub-Directory for the Design and open a terminal from the Sub-Directory.

**a) Verify the Functionality**

- Three Codes shall be written for implementation of 4-bit Adder as follows,
  - fa.v → Single Bit 3-Input Full Adder [Sub-Module / Function]
  - fa\_4bit.v → Top Module for Adding 4-bit Inputs.
  - fa\_test.v → Test bench



Source Code – fa.v :-

```

module full_adder( A,B,CIN,S,COU);
input A,B,CIN;
output S,COU;
assign S = A^B^CIN;
assign COU = (A&B) | (CIN&(A^B));
endmodule

```

Source Code – fa\_4bit.v :-

```

module four_bit_adder(A,B,C0,S,C4);
input [3:0] A,[3:0] B,C0;
output [3:0] S,C4;
wire C1,C2,C3;
    full_adder fa0 (A[0],B[0],C0,S[0],C1);
    full_adder fa1 (A[1],B[1],C1,S[1],C2);
    full_adder fa2 (A[2],B[2],C2,S[2],C3);
    full_adder fa3 (A[3],B[3],C3,S[3],C4);
endmodule


```

Test Bench – fa\_test.v :-

```

module test_4_bit;
    reg [3:0] A;
    reg [3:0] B;
    reg C0;
    wire [3:0] S;
    wire C4;
    four_bit_adder dut(A,B,C0,S,C4);
    initial begin
        A = 4'b0011;B=4'b0011;C0 = 1'b0; #10;
        A = 4'b1011;B=4'b0111;C0 = 1'b1; #10;
        A = 4'b1111;B=4'b1111;C0 = 1'b1; #10;
    endinitial
    #50 $finish;
endmodule

```

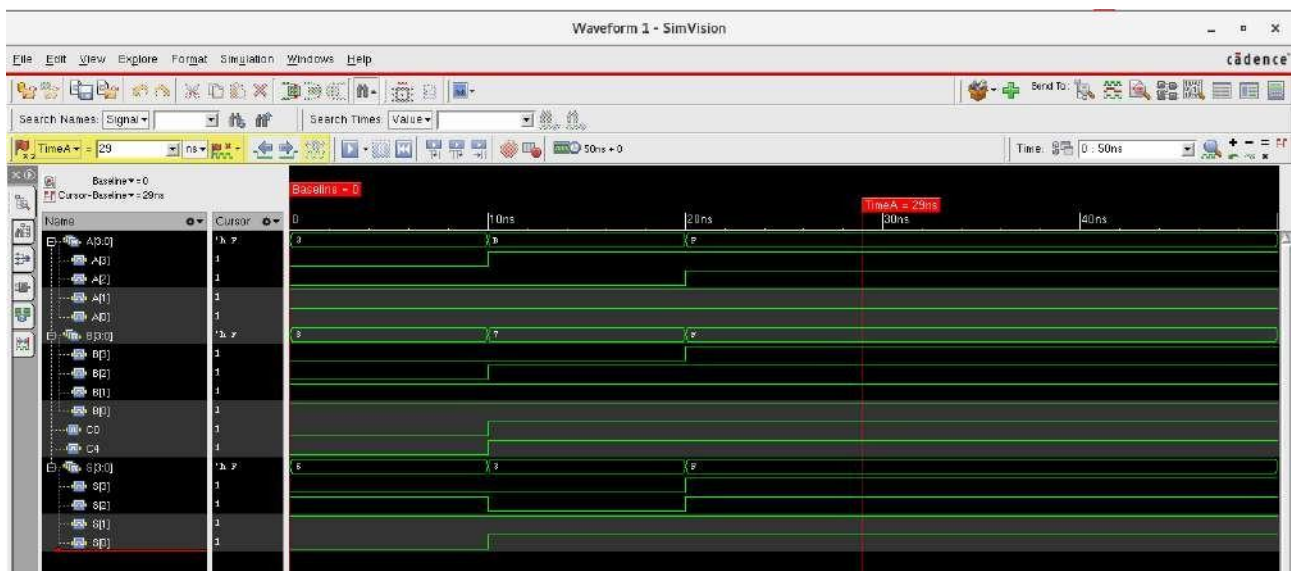
Waveform :

## b) Synthesis and Report/Output Analysis

### Note 1:-

1. The Cells given in the netlist can be checked in the .lib files for their properties.
2. The Max Operating Frequency does not apply for Purely Combinational Circuit.

### Synthesis RTL Schematic :

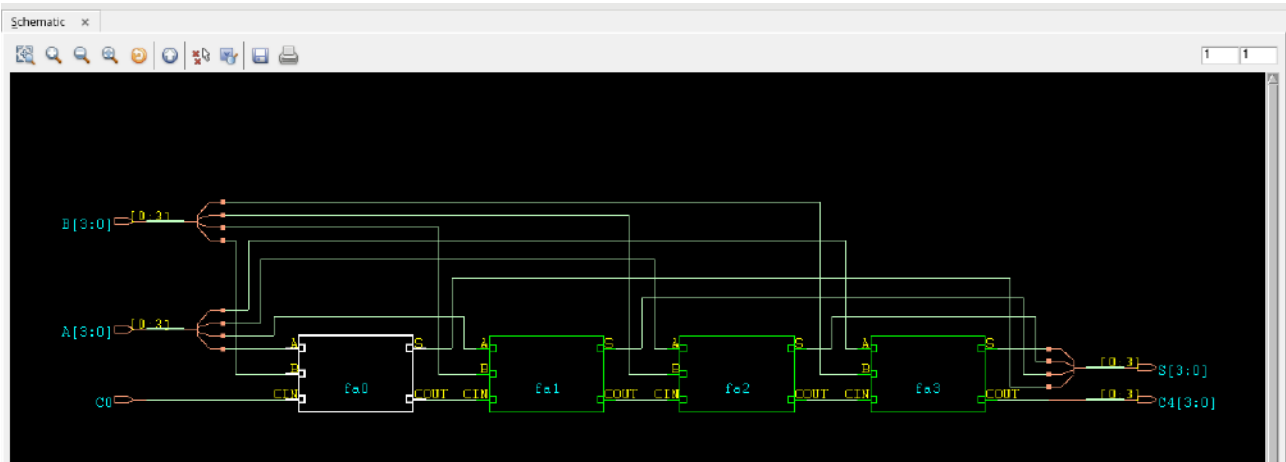

Some Common Constraints are given below for reference

### Common SDC Constraints

#### Operating conditions

- set\_operating\_conditions

#### Wire-load models

- set\_wire\_load\_mode
- set\_wire\_load\_model
- set\_wire\_load\_selection\_group

#### Environmental

- set\_drive
- set\_driving\_cell
- set\_load
- set\_fanout\_load
- set\_input\_transition
- set\_port\_fanout\_number

#### Design rules

- set\_max\_capacitance
- set\_max\_fanout
- set\_max\_transition

#### Timing

- create\_clock
- create\_generated\_clock
- set\_clock\_latency
- set\_clock\_transition
- set\_disable\_timing
- set\_propagated\_clock
- set\_clock\_uncertainty
- set\_input\_delay
- set\_output\_delay

#### Exceptions

- set\_false\_path
- set\_max\_delay
- set\_multicycle\_path

#### Power

- set\_max\_dynamic\_power
- set\_max\_leakage\_power

### Note 2:-

1. You can tabulate Area, Power and Timing Constraints using any of the SDC Constraints as instructed.
2. Make sure, during synthesis the Report File Names are changed so that the latest reports don't overwrite the earlier ones.

## Lab 2: 4 – Bit Booth Multiplier

**Aim:** To write a verilog code for 4bit Booth Multiplier and verify the functionality using Test bench.

- Synthesize, Analyse Reports and Netlist, Critical Path and Max Operating Frequency.
- From the report generated find the total number of cells, power requirement and total area requirement.

**Tool Required:**

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

**Design Information and Block Diagram:**

In Booth's multiplier works on Booth's Algorithm that does the multiplication of 2's complement notation of two signed binary numbers.

**Advantages:**

1. Less complexity
2. Faster Multiplication
3. Consecutive additions are replaced
4. Ease in scaling

**Disadvantage:**

1. High power consumption
2. Large chip area

**Algorithm:**

Registers used: A, M, Q, Qres (Qres is the residual bit after a right shift of Q), n (counter)

**Step 1:** Load the initial values for the registers.

A = 0 (Accumulator), Qres = 0, M = Multiplicand, Q = Multiplier and n is the count value which equals the number of bits of multiplier.

**Step 2:** Check the value of {Q0, Qres}. If 00 or 11, goto step 5. If 01, goto step 3. If 10, goto step 4.


**Step 3:** Perform  $A = A + M$ . Goto step 5.

**Step 4:** Perform  $A = A - M$ .

**Step 5:** Perform Arithmetic Shift Right of {A, Q, Qres} and decrement count.

**Step 6:** Check if counter value n is zero. If yes, goto next step. Else, goto step 2.

**Step 7:** Stop

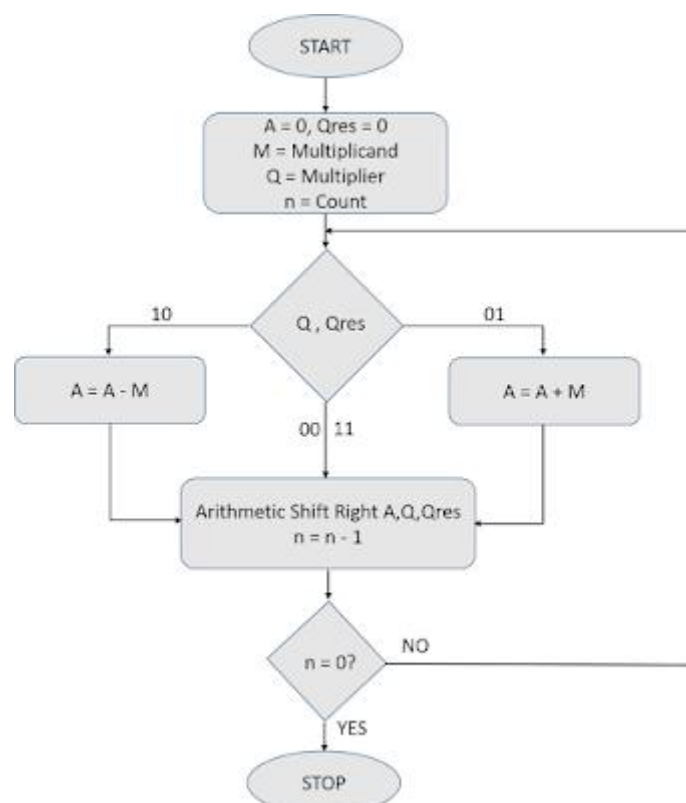

Creating a Work space :

- Create a new sub-Directory for the Design and open a terminal from the Sub-Directory.

**a) To Verify the Functionality using Test Bench**Source Code – boothmul.v :-

```

module BoothMulti (X, Y, Z);
input signed [3:0] X, Y;
output signed [7:0] Z;
reg signed [7:0] Z;
reg [1:0] temp;
integer i;
reg E1;
reg [3:0] Y1;
always @ (X, Y)
    begin
        Z = 8'd0;
        E1 = 1'd0;
        for (i = 0; i < 4; i = i + 1)
            begin
                temp = {X[i], E1};
                Y1 = - Y;
                case (temp)
                    2'd2 : Z [7 : 4] = Z [7 : 4] + Y1;
                    2'd1 : Z [7 : 4] = Z [7 : 4] + Y;
                    default : begin end
                endcase
                Z = Z >> 1;
                Z[7] = Z[6];
                E1 = X[i];
            end
        if (Y == 4'd8)
            begin
                Z = - Z;
            end
        end
    endmodule

```

Test Bench – boothmul\_test.v :-

```

module BoothTB;
    // Inputs
    reg [3:0] X;
    reg [3:0] Y;
    // Outputs
    wire [7:0] Z;
    // Instantiate the Unit Under Test (UUT)
    BoothMulti uut (
        .X(X),
        .Y(Y),
        .Z(Z)
    );
    initial begin
        // Initialize Inputs
        X = 0;
        Y = 0;
        // Wait 100 ns for global reset to finish


```

```

#10;
X=-5;
Y=7;
#100;
X=-4;
Y=6;
#100;
X=-5;
Y=-5;
// Add stimulus here
end

```

**Waveform :**

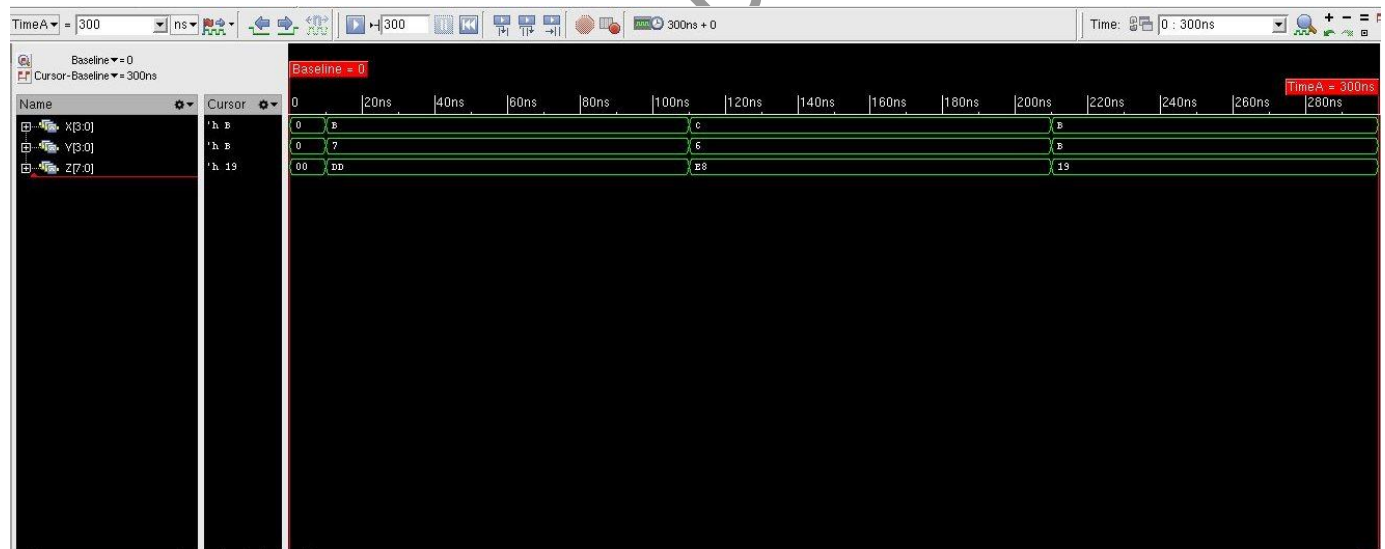


## b) Synthesis and Report/Output Analysis

### Note 1:-

1. The Cells given in the netlist can be checked in the .lib files for their properties.
2. The Max Operating Frequency does not apply for Purely Combinational Circuit.

### Synthesis RTL Schematic :

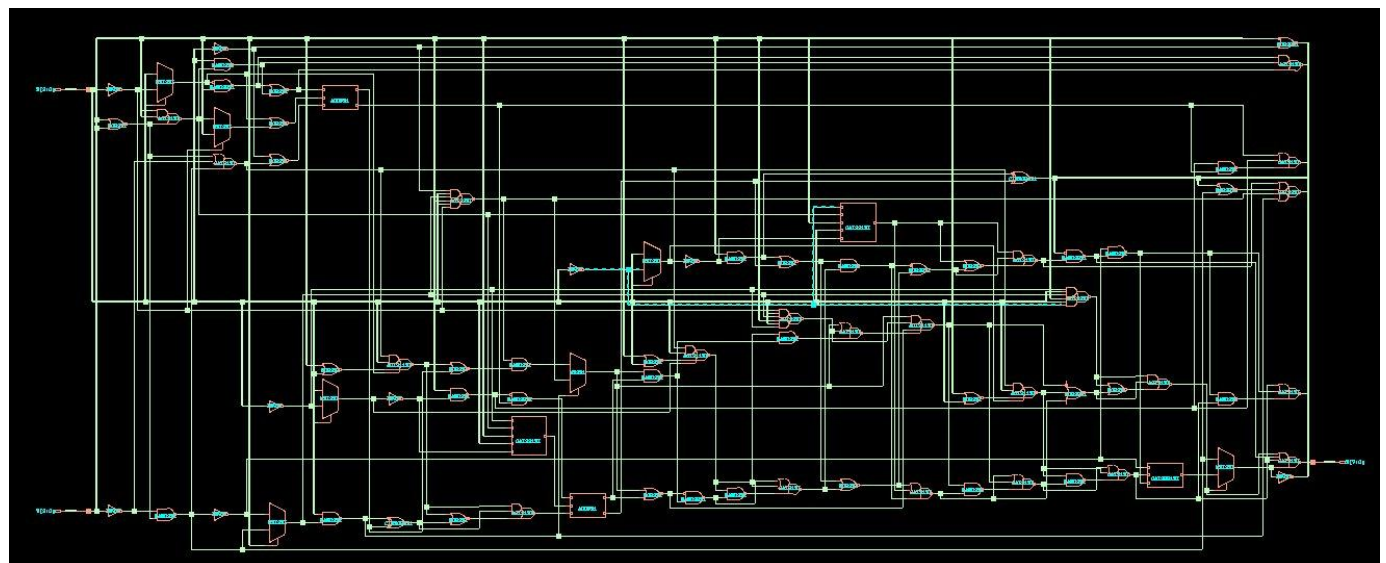

Some Common Constraints are given below for reference

**Lab 3 : 32-bit ALU**

**Aim:** Write a verilog code for 32 bit ALU supporting four logical and four arithmetic operations, use case statement and if statement for ALU behavioral modeling.

- To Verify the Functionality using Test Bench
- Synthesize and compare the results using if and case statements
- Identify Critical Path and constraints

**Tool Required:**

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

**Design Information and Block Diagram:**

The ALU will take in two 32-bit values, and control line. An Arithmetic unit does the following task like addition subtraction, multi-fiction and logical operations. As the input is given in 32 bit we get 32 bit output. The arithmetic will show only one output at a time so a selector is necessary to select one of the operator.

**Creating a Work space :**

- Create a new sub-Directory for the Design and open a terminal from the Sub-Directory.

**To Verify the Functionality using Test Bench****Source Code – Using Case Statement :**

```
module 32bit_alu_case(a, b, f, y);
input [31:0]a;
input [31:0]b;
input [2:0]f;
output reg [31:0]y;
always @ (*)
begin
case (f)
3'b000: y=a&b;           //AND Operation
3'b001: y=a|b;           //OR Operation
3'b010: y=~(a&b);        //NAND Operation
3'b011: y=~(a|b);        //NOR Operation
3'b100: y=a+b;           //Addition
3'b101: y=a-b;           //Subtraction
3'b110: y=a*b;           //Multiply
default: y=32'bx;
endcase
end
endmodule
```

Test Bench :

```

module 32bit_alu_case_tb;
reg [31:0]a;
reg [31:0]b;
reg [2:0]f;
wire [31:0]y;
32bit_alu_case test2(.a(a),.b(b),.f(f),.y(y));
initial
begin
a=32'h00000000;
b=32'hFFFFFFF;
#10 f=3'b000;
#10 f=3'b001;
#10 f=3'b010;
#10 f=3'b011;
#10 f=3'b100;
#10 f=3'b101;
#10 f=3'b110;
end
initial
#50 $finish;
endmodule

```

Source Code - Using If Statement :

```

module 32bit_alu_if(y,a,b,f);
input [31:0]a;
input [31:0]b;
input [2:0]f;
output reg [31:0]y;
always@(*)
begin
if(f==3'b000)
y=a&b;           //AND Operation
else
if (f==3'b001)
y=a|b;           //OR Operation
else
if (f==3'b010)
y=a+b;           //Addition
else
if (f==3'b011)
y=a-b;           //Subtraction
else
if (f==3'b100)
y=a*b;           //Multiply
else
y=32'bx;
end
endmodule

```

Test bench :

```

module 32bit_alu_tb_if;
reg [31:0]a;
reg [31:0]b;


```

```

reg [2:0]f;
wire [31:0]y;
32bit_alu_if test(.y(y),.a(a),.b(b),.f(f));
initial
begin
a=32'h00000000;
b=32'hFFFFFFF;
#10 f=3'b000;
#10 f=3'b001;
#10 f=3'b010;
#10 f=3'b100;
end
initial
#50 $finish;
endmodule

```

### Wave Forms :

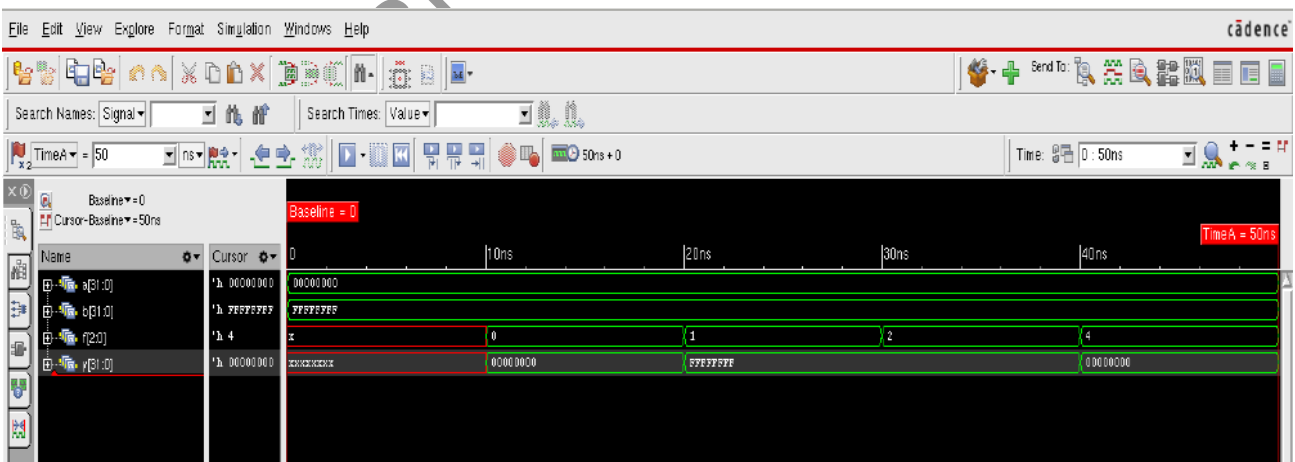

### a) Synthesize Design

- Run the synthesis Process one time for each code and make sure the output File names are changed accordingly.



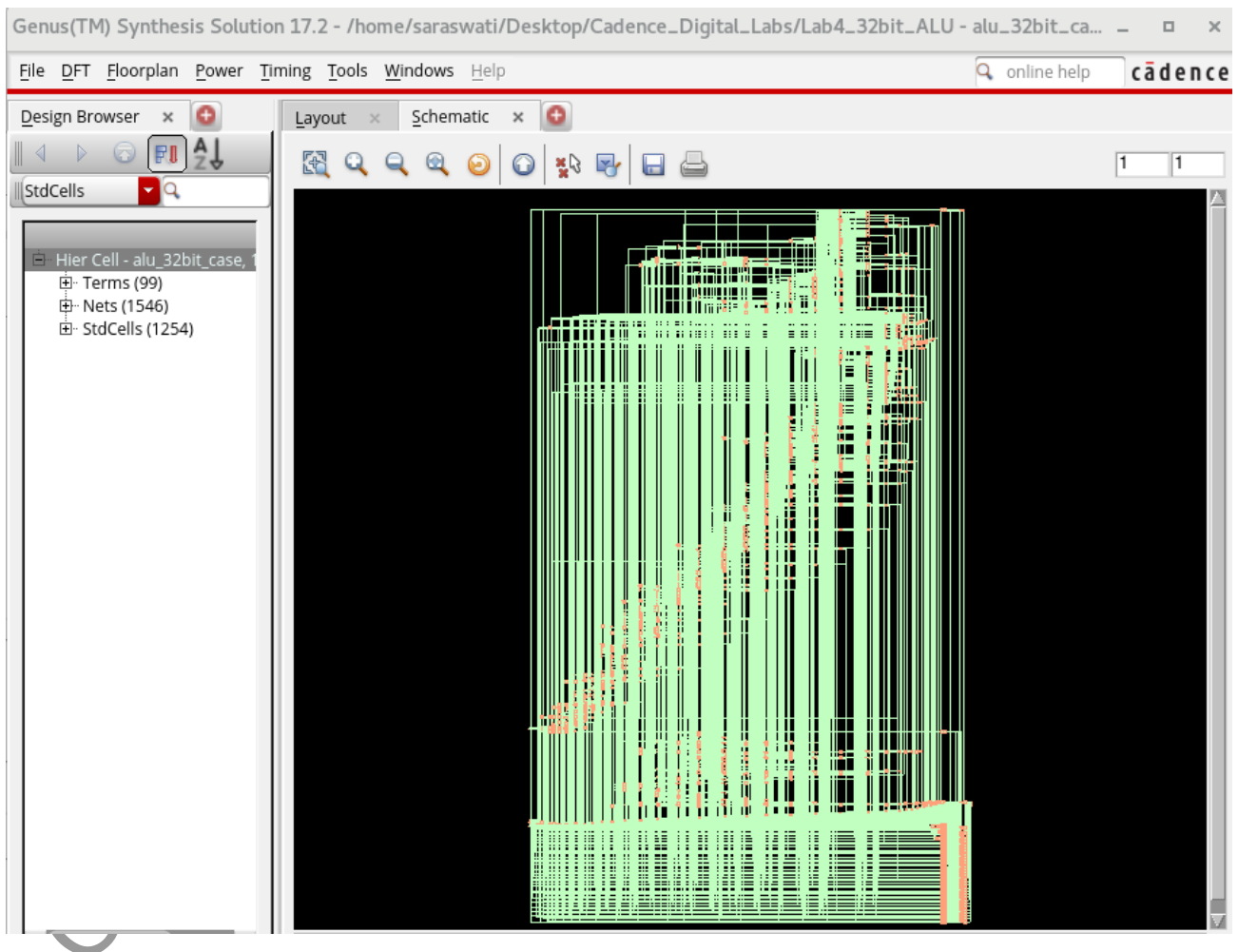
Synthesis RTL Schematic :

Fig: Schematic Capture of 32 Bit ALU

**Note :-**

1. You can tabulate Area, Power and Timing Constraints using any of the SDC Constraints as instructed.
2. Make sure, during synthesis the Report File Names are changed so that the latest reports donot overwrite the earlier ones.

### Lab 4: Latches and Flip Flops

**Aim :** Write a verilog code for Latch and Flip-flops (D, SR, JK), Synthesize the design and compare the synthesis report.

**Tool Required:**

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus


**Design Information and Block Diagram:**

Latches and flip-flops are the basic elements for storing information. One latch or flip-flop can store one bit of information. The main difference between latches and flip-flops is that for latches, their outputs are constantly affected by their inputs as long as the enable signal is asserted.

In other words, when they are enabled, their content changes immediately when their inputs change. Flip-flops, on the other hand, have their content change only either at the rising or falling edge of the enable signal. This enable signal is usually the controlling clock signal. After the rising or falling edge of the clock, the flip-flop content remains constant even if the input changes.

There are basically four main types of latches and flip-flops: SR, D, and JK. The major differences in these flip-flop types are the number of inputs they have and how they change state. For each type, there are also different variations that enhance their operations.

Example: D-Flip-flop

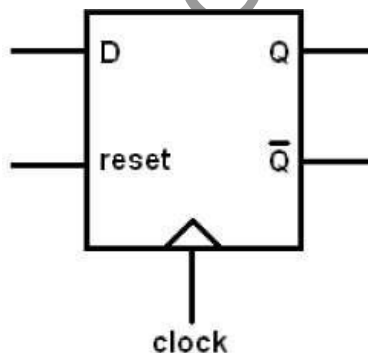

Input			Output	
D	reset	clock	Q	Q'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	0	1

Fig: Block Diagram and truth table of D-Flip Flop

**Creating a Work space :**

- Create a new sub-Directory for the Design and open a terminal from the Sub-Directory.

**a) Verilog Codes for D-Flip Flop, JK-Flip Flop and SR-Flip Flop.**

Source code for D-Flip Flop :

```
`timescale 1ns/1ps
module DFF( Q, Qbar, D, Clk, Reset);
output reg Q;
output Qbar;
input D, Clk, Reset;
always @(posedge Clk)
begin
if (Reset == 1'b1)      //If at reset
Q <= 1'b0;
Else
Q <= D;
end
assign Qbar = ~Q;
endmodule
```

Test bench :

```

`timescale 1ns/1ps
module DFF_test;
reg clk, reset, D;
wire q, qbar;
initial
begin
clk=0;
reset=1; #20;
reset=0;
end
initial
begin
D=0; #100;
D=1; #100;
D=0;
end
dff uut(Q, Qbar, D,clk, reset);
always #5 clk=~clk; // Inverting clk every 5ns
Initial
#1400 $finish; // Finishing Simulation at t=1400ns
endmodule

```

Wave Forms :Source code for D-Latch :

```

`timescale 1ns/1ps
module Dlatch ( Q, Qbar, D, en, Reset);
output reg Q;
output Qbar;
input D, en, Reset;
always @(en or Reset or D)
begin
if (Reset == 1) //If at reset
Q <= 1'b0;
else
if (en)
Q <= D;
end
assign Qbar = ~Q;
endmodule

```

Test bench :

```

`timescale 1ns/1ps
module Dlatch_test;
reg en, reset, D;
wire Q, Qbar;
initial
begin
en=0;

```

```

reset=1; #20;
en=1; #50;
reset=0;
end
initial
begin
D=0; #10;
D=1; #100;
D=0;
end
Dlatch uut (Q, Qbar, D, en, reset);
endmodule

```

### Wave Forms :



### Source code for SR Flip Flop :

```

`timescale 1ns/1ps
module srff (clk, rst_n, s,r, q, q_bar);
input clk, rst_n;
input s,r;
output reg q;
output q_bar;
// always@(posedge clk or negedge rst_n) // for asynchronous reset
always@(posedge clk)
begin
if(rst_n)
q <= 0;
else
begin
case({s,r})
2'b00: q <= q; // No change
2'b01: q <= 1'b0; // reset
2'b10: q <= 1'b1; // set
2'b11: q <= 1'bx; // Invalid inputs
endcase
end
end
assign q_bar = ~q;
endmodule

```

### Test bench :

```

`timescale 1ns/1ps
module srff_test;
reg clk, rst_n;
reg s, r;
wire q, q_bar;
initial begin
clk = 0;
rst_n = 1; #10; rst_n = 0;
end


```

```

initial begin
s=0; r=0; #20;
s=0; r=1; #20;
s=1; r=0; #20;
s=1; r=1;
end
srff uut (clk, rst_n, s, r, q, q_bar);
always #5 clk = ~clk;
initial
#1400 $finish;
endmodule

```

### Wave Forms :

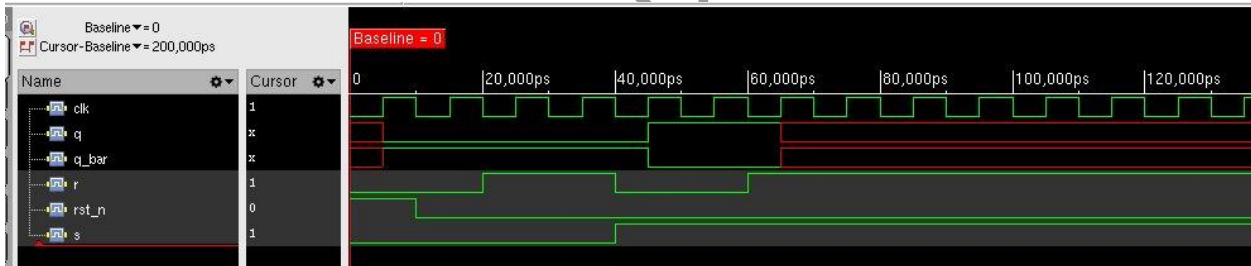

### Source Code for SR Latch :

```

module srlatch (q, qbar, s, r, en, rst);
output reg q;
output q;
input s, r, en, rst;
always @ (en or rst or s or r)
begin
if (rst)
q<=0;
else
if (en)
begin
case ({s,r})
2'b00: q<=q;
2'b01: q<=1'b0;
2'b10: q<=1'b1;
2'b11: q<=1'bx;
endcase
end
end
assign qbar=~q;
endmodule

```

### Test bench :

```

`timescale 1ns/1ps
module srlatch_test;
reg en, rst;
reg s, r;
wire q, qbar;
initial
begin
en=0; rst=1; #10;
en=1; rst=0; #10;
rst =0;

```

```

end
initial begin
s=0; r=0; #20;
s=0; r=1; #20;
s=1; r=0; #20;
s=1; r=1; #20;
end
srlatch uut (q, qbar, s, r, en, rst);
initial
#1400 $finish;
endmodule

```

### Wave Forms :



### Source Code for JK Flip Flop :

```

module jkff (clk, rst, J, K, q, qbar);
input J, K, clk, rst;
output reg Q;
output qbar;
always @(posedge clk)
begin
if (rst)
q<=0;
else
begin
case ({j,k})
2'b00: q<= q;
2'b01: q<= 1'b0;
2'b10: q<= 1'b1;
2'b11: q<= ~q;
endcase
end
end
assign qbar= ~q;
endmodule

```

### Test bench :

```

Module jkff_test;
reg clk, rst, j, k;
wire q, qbar;
initial begin
clk =0; rst =1; #10;
rst =0;
end
initial begin
j=0; k=0; #20;
j=0; k=1; #20;
j=1; k=0; #20;


```

```

j=1; k=1; #20;
end
jkff uut (clk, rst, j, k, q, qbar);
always #5 clk =~clk;
endmodule

```

### Wave Forms :

 

### Source of JK Latch :

```

module jkff(en, rst, j, k, q, qbar);
input en, rst, j, k;
output reg q;
output qbar;
always @(en or rst or j or k)
begin
if (rst)
q<=0;
else
if (en)
begin
case ({j, k})
2'b00: q<=q;
2'b01: q<=1'b0;
2'b10: q<=1'b1;
2'b11: q<=~q;
endcase
end
end
assign qbar=~q;
endmodule

```


### Test bench :

```

Module jklatch_test;
reg en, rst, j, k;
wire q, qbar;
initial begin
en=1; rst=0; #10;
en=0; #5;
en=1;
rst=1; #10;
rst=0;
end
initial begin
j=0; k=0; #20;
j=0; k=1; #20;
j=1; k=0; #20;
j=1; k=1; #20;
end
jklatch uu (en, rst, j, k, q, qbar);
endmodule

```

### Wave Forms

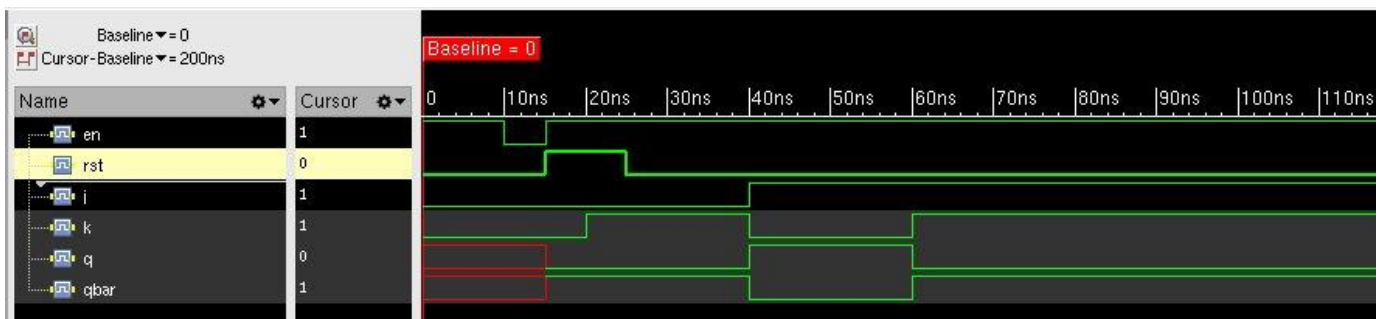

### a) Synthesize the Design & Comparing Reports

#### Example for SDC:

```
constraints_top_ff.sdc
~/Desktop/VTU_Manuals/ff_latch

create_clock -name Clk -period 2 -waveform {0 1} [get_ports "Clk"]
set_clock_transition -rise 0.1 [get_clocks "Clk"]
set_clock_transition -fall 0.1 [get_clocks "Clk"]
set_clock_uncertainty 0.01 [get_clocks "Clk"]
set_input_delay -max 1.0 [get_ports "Reset"] -clock [get_clocks "Clk"]
set_input_delay -max 1.0 [get_ports "D"] -clock [get_clocks "Clk"]
set_output_delay -max 1.0 [get_ports "Q"] -clock [get_clocks "Clk"]
set_output_delay -max 1.0 [get_ports "Qbar"] -clock [get_clocks "Clk"]
```

The Above is the example SDC for a D Flip Flop

```
constraints_top_latch.sdc
~/Desktop/VTU_Manuals/ff_latch

set_input_delay -max 1.0 [get_ports "Reset"]
set_input_delay -max 1.0 [get_ports "en"]
set_input_delay -max 1.0 [get_ports "D"]
set_output_delay -max 1.0 [get_ports "Q"]
set_output_delay -max 1.0 [get_ports "Qbar"]
```

The above is an Example for SDC File for D Latch.

#### Synthesis RTL Schematic :

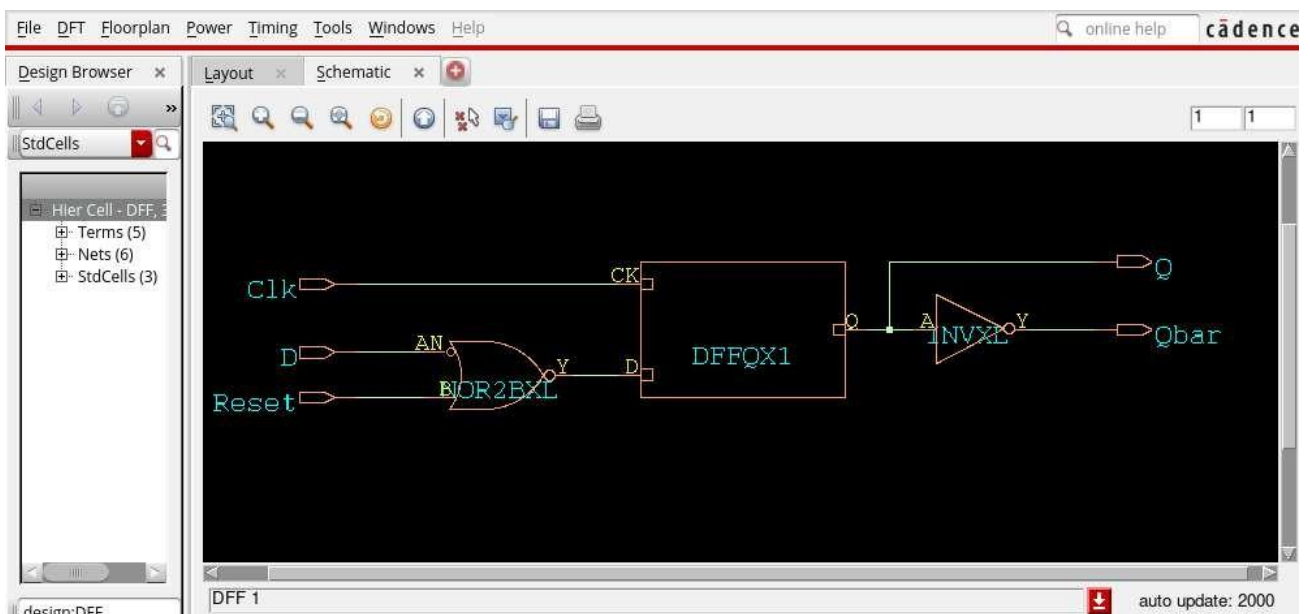


Fig: Schematic of D-Flip Flop

#### Note :-

1. You can tabulate Area, Power and Timing Constraints using any of the SDC Constraints as instructed.
2. Make sure, during synthesis the Report File Names are changed so that the latest reports do not overwrite the earlier ones.



**Custom IC Design Flow  
(ASIC Analog Design)**

**PART – B**

**LAB – 01: CMOS INVERTER****Objective:**

- (a) Capture the Schematic of a CMOS Inverter with Load Capacitance of 0.1 pF and set the Widths of Inverter with
- $W_N = W_P$
  - $W_N = 2 W_P$
  - $W_N = W_P / 2$
- and Length at selected Technology. Carry out the following:
- Set the Input Signal to a pulse with Rise Time, Fall Time of 1 ps and Pulse Width of 10 ns, Time Period of 20 ns and plot the input voltage and output voltage of the designed Inverter
  - From the Simulation Results, compute  $t_{PHL}$ ,  $t_{PLH}$  and  $t_{PD}$  for all the three geometrical settings of Width
  - Tabulate the results of delay and find the best geometry for minimum delay for CMOS Inverter

**Solution:****(i) SCHEMATIC CAPTURE FOR THE CMOS INVERTER**

For the CMOS Inverter circuit, PMOS and NMOS transistors are required. The parameters for the devices as given in the requirement are considered as in Table – 1, Table – 2 and Table – 3.

**Table – 1: Length and Width of NMOS and PMOS Transistors for the condition  $W_N = W_P$** 

Library Name	Cell Name	Comments / Properties
gpd180	Nmos	Width, $W_N = 850$ n Length, $L = 180$ n
gpd180	Pmos	Width, $W_P = 850$ n Length, $L = 180$ n

**Table – 2: Length and Width of NMOS and PMOS Transistors for the condition  $W_N = 2 * W_P$** 

Library Name	Cell Name	Comments / Properties
gpd180	Nmos	Width, $W_N = 850$ n Length, $L = 180$ n
gpd180	Pmos	Width, $W_P = 1.7$ u Length, $L = 180$ n

**Table – 3: Length and Width of NMOS and PMOS Transistors for the condition  $W_N = W_P / 2$** 

Library Name	Cell Name	Comments / Properties
gpd180	Nmos	Width, $W_N = 850$ n Length, $L = 180$ n
gpd180	Pmos	Width, $W_P = 425$ n Length, $L = 180$ n

 
 
 
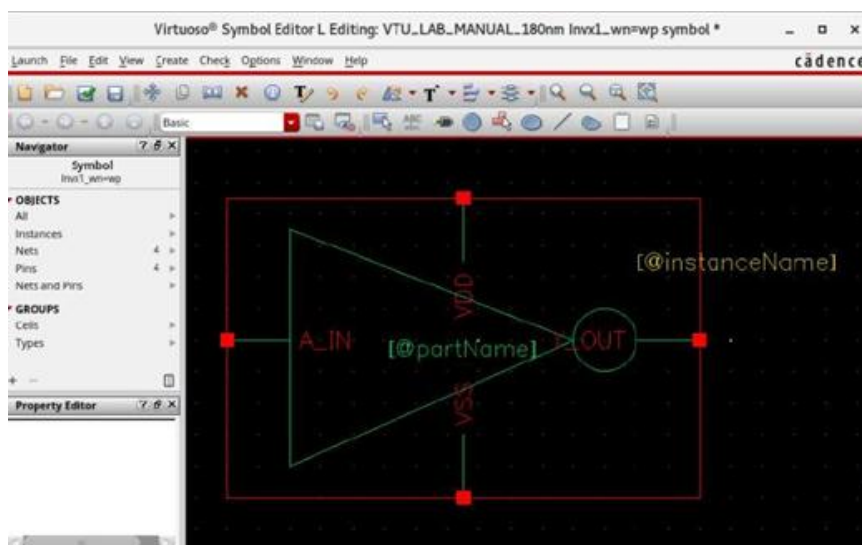
Figure – 1.25(a):  $W_N = W_P$ Figure – 1.25(b):  $W_N = 2 * W_P$ Figure – 1.25(c):  $W_N = W_P / 2$ **SYMBOL CREATION:**

Figure – 1.35: Customized Symbol of an Inverter

**(1) TEST CIRCUIT FOR SIMULATION:**

The complete circuit after instantiating all the devices and interconnections is shown in Figure – 1.42.

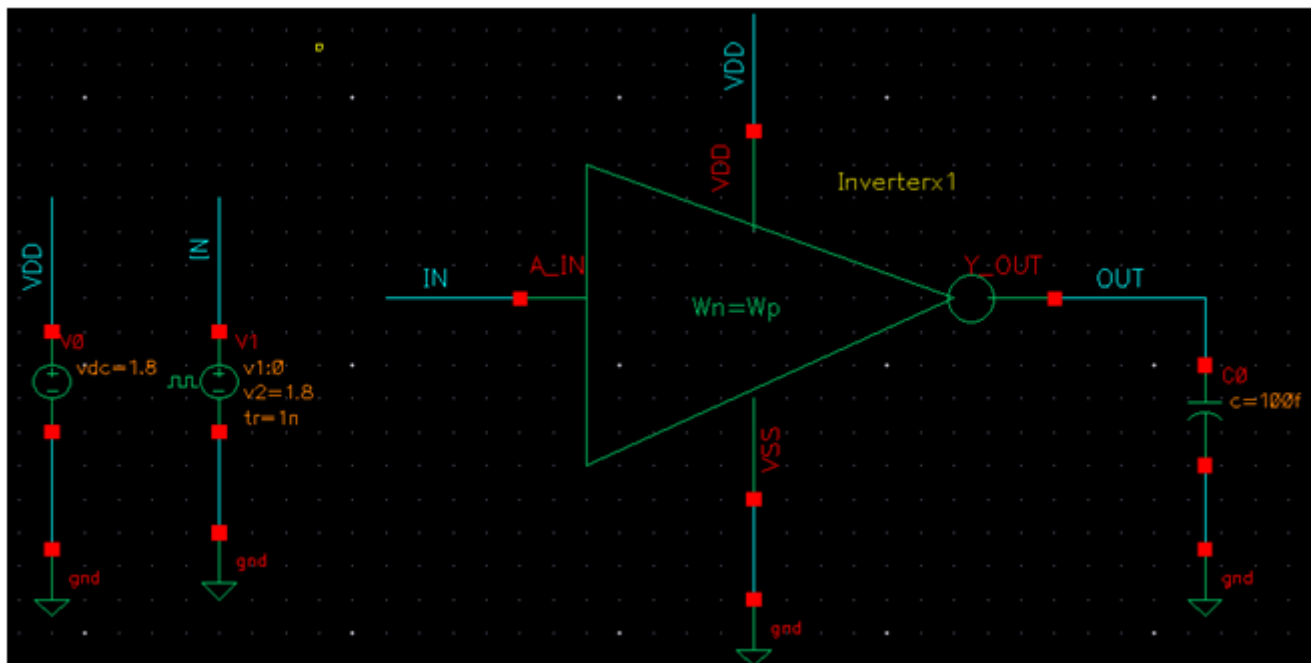


Figure – 1.42: Complete Test Schematic

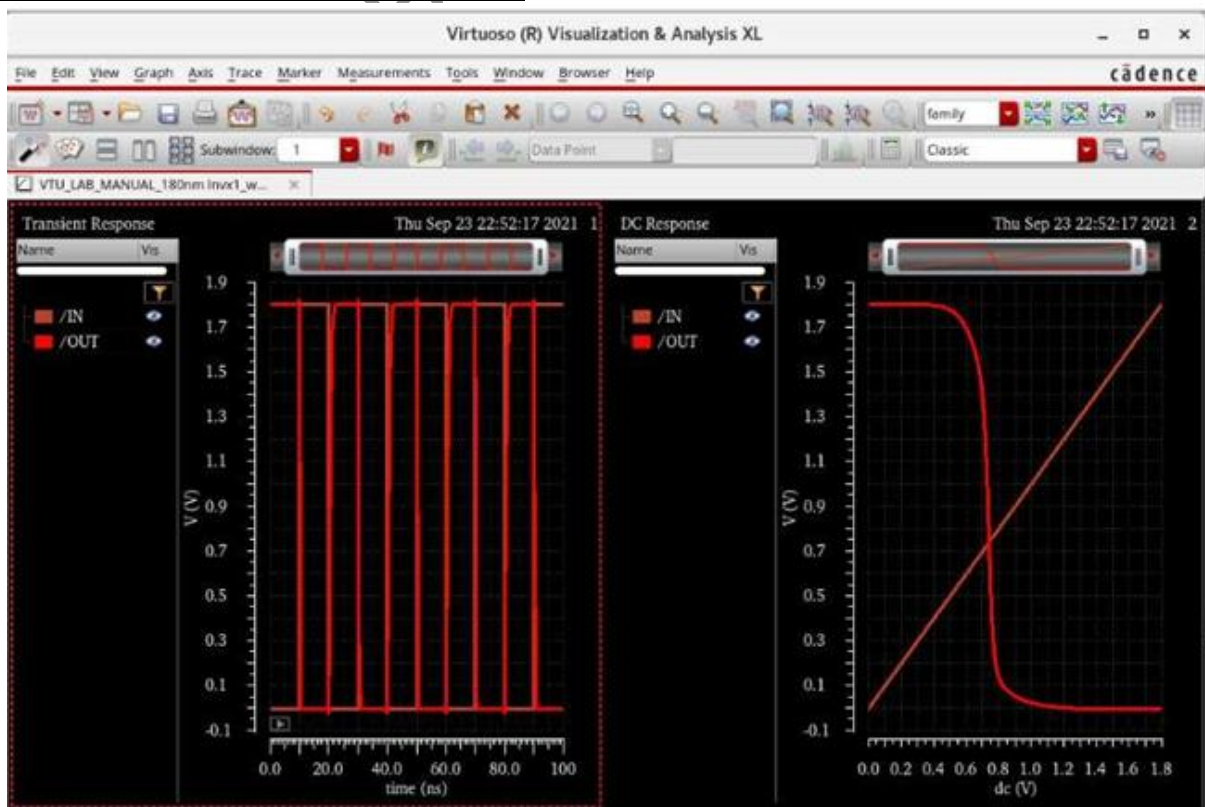
**FUNCTIONAL SIMULATION WITH SPECTRE:**

Figure –

**1.70: Simulated waveforms**

The Input and Output Signals can be split up by selecting “**Graph —> Split All Strips**” as in Figure – 1.71.

**(1) CALCULATION OF  $t_{PHL}$ ,  $t_{PLH}$  AND  $t_{PD}$ :**

To calculate the Propagation Delay ( $t_{PD}$ ), the formula used is

$$t_{PD} = \frac{(t_{PLH} + t_{PHL})}{2}$$

where,  $t_{PLH}$  —> Low – High Propagation Delay and  $t_{PHL}$  —> High – Low Propagation Delay.

To calculate  $t_{PLH}$  and  $t_{PHL}$  use the Calculator option from the “**Virtuoso (R) Visualization and Analysis**” window. So, select “**Tools —> Calculator**” or click on the icon as shown in Figure – 1.78.

**(2) TABULATED VALUES OF DELAY:**

The results of  $tp_{HL}$ ,  $tp_{LH}$  and  $tp_{PD}$  for all the required geometrical settings are tabulated below in Table – 5.

**Table – 5: Values of  $tp_{HL}$ ,  $tp_{LH}$  and  $tp_{PD}$  for different geometries**

Width Settings	MOSFET	Width	$tp_{LH}$	$tp_{HL}$	$tp_{pd}$
$W_p = W_n$	PMOS	850n	3.233E-10	7.049E-10	5.141E-10
	NMOS	850n			
$W_n = 2W_p$	PMOS	850n	3.337E-10	4.700E-10	4.019E-10
	NMOS	1.7u			
$W_n = W_p/2$	PMOS	425n	1.141E-09	3.154E-10	7.282E-10
	NMOS	850n			

(a) Layout of CMOS Inverter with  $\frac{W_p}{W_n} = \frac{40}{20}$

**Objective:**

To draw the Layout of CMOS Inverter with  $\frac{W_p}{W_n} = \frac{40}{20}$  using optimum Layout Methods. Verify for DRC and LVS, extract the Parasitics and perform the Post-Layout Simulations, compare the results with Pre-Layout Simulations and record the observations.


**SCHEMATIC CAPTURE:**

Create a New Library, Create a Cellview and instantiate the required devices through “Create Instance” option. The parameter for PMOS and NMOS Transistors are listed in Table – 6 shown below.

**Table – 6: Parameters for NMOS and PMOS Transistors**

Library Name	Cell Name	Comments / Properties
gpd180	Nmos	Width, $W_N = 20 \mu$ Length, $L = 180 \text{ n}$
gpd180	Pmos	Width, $W_P = 40 \mu$ Length, $L = 180 \text{ n}$

Follow the techniques demonstrated in Lab – 01 to complete the Schematic. The completed CMOS Inverter circuit is shown in Figure – 1.85.

 

**Figure – 1.85: Schematic for CMOS Inverter with  $\frac{W_p}{W_n} = \frac{40}{20}$**

The symbol for the CMOS Inverter is shown in Figure – 1.86.

 


Figure – 1.86: Symbol for CMOS Inverter with  $\frac{W_p}{W_n} = \frac{40}{20}$

**SIMULATION:**

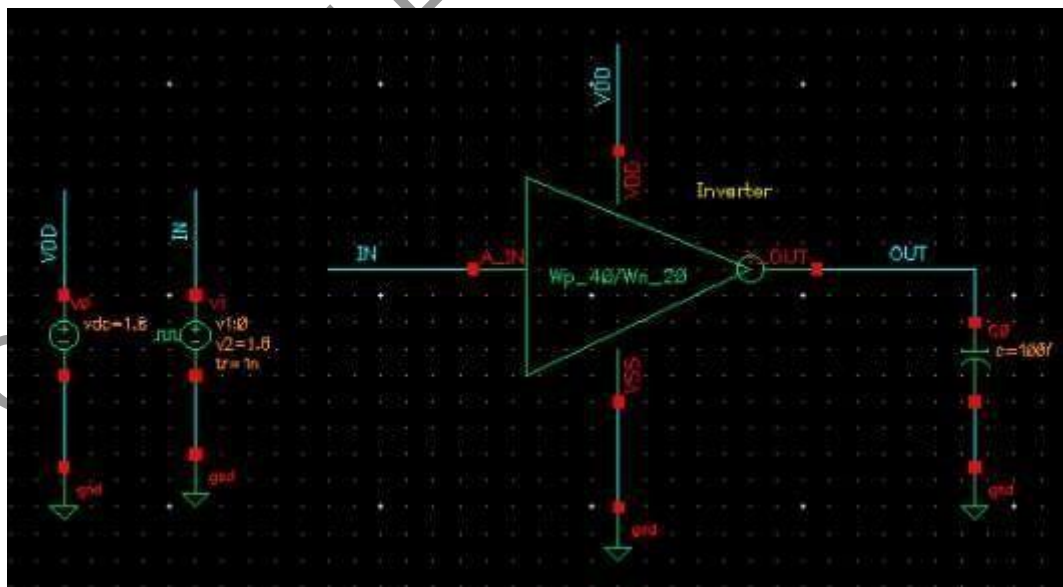


Figure – 1.88: Updated ADE L window

 


Figure – 1.89: Transient Analysis for CMOS Inverter with  $\frac{W_p}{W_n} = \frac{40}{20}$

Similarly, the signals plotted after DC Analysis are shown in Figure – 1.90.



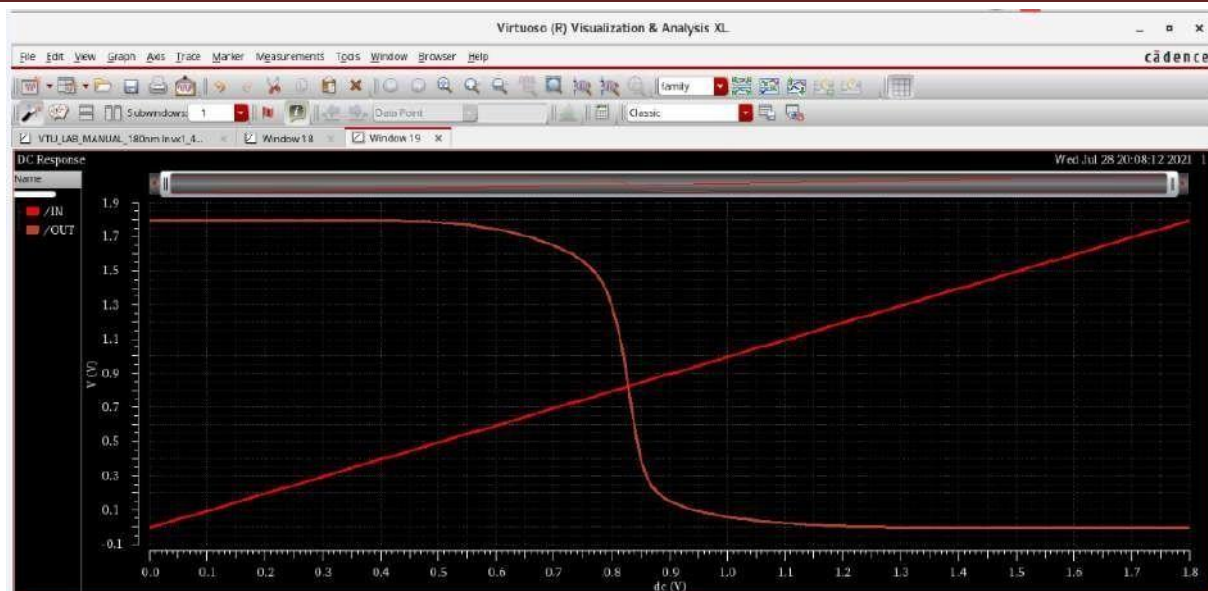


Figure – 1.90: DC Analysis for CMOS Inverter with  $\frac{W_p}{W_n} = \frac{40}{20}$

**VALUES OF  $t_{pHL}$ ,  $t_{pLH}$  AND  $t_{pD}$ :**

Obtain the values of  $t_{pHL}$ ,  $t_{pLH}$  and  $t_{pD}$  by referring to “CALCULATION OF  $t_{pHL}$ ,  $t_{pLH}$  AND  $t_{pD}$ ” in the previous section. The values are tabulated as shown in Table – 7

Table – 7: Values  $t_{pHL}$ ,  $t_{pLH}$  AND  $t_{pD}$  for CMOS Inverter with  $\frac{W_p}{W_n} = \frac{40}{20}$

MOSFET	Length	Width	$t_{pLH}$	$t_{pHL}$	$t_{pD}$
PMOS	180n	40u	1.228E-10	3.550E-11	7.920E-11
NMOS	180n	20u			

## LAB – 02: 2 – INPUT CMOS NAND GATE

### Objective:

(a) Capture the Schematic of a 2 – input CMOS NAND Gate having similar delay as that of CMOS Inverter computed in Lab – 01. Verify the functionality of the NAND Gate and also find out the delay for all the four possible combinations of input vectors. Tabulate the results. Increase the drive strength to 2X and 4X and tabulate the results.

(b) Draw the layout of NAND with  $\frac{W_p}{W_n} = \frac{40}{20}$  use optimum layout methods. Verify DRC

and LVS, extract the parasitics and perform the post layout simulation, compare the results with pre layout simulations. Record the observations.

### Solution – (a):

#### SCHEMATIC CAPTURE:

Following the techniques demonstrated in Lab – 01, Create a New Library using the option “File → New → Library”, create a New Cell View upon selecting the newly created library using the option “File → New → Cell View” and instantiate the required devices using the “Create → Instance” option.

The device parameters are listed in Table – 9.

**Table – 9: Width and Length of NMOS and PMOS Transistors for CMOS NAND Gate**

Library Name	Cell Name	Comments / Properties
gpd180	Nmos	Width, $W_N = 1.7 \mu$ Length, $L = 180 \text{ n}$
gpd180	Pmos	Width, $W_P = 1.275 \mu$ Length, $L = 180 \text{ n}$

Similarly, the device parameters for the 2 – input CMOS NAND Gate with drive strength 2 and drive strength 4 are listed in Table – 10 and Table – 11.

**Table – 10: Width and Length of NMOS and PMOS Transistors for CMOS NAND Gate with Drive Strength “2”**

Library Name	Cell Name	Comments / Properties
gpd180	Nmos	Width, $W_N = 3.4 \mu$ Length, $L = 180 \text{ n}$
gpd180	Pmos	Width, $W_P = 2.55 \mu$ Length, $L = 180 \text{ n}$

**Table – 11: Width and Length of NMOS and PMOS Transistors for CMOS NAND Gate with Drive Strength “4”**

Library Name	Cell Name	Comments / Properties
gpd180	Nmos	Width, $W_N = 6.8 \mu$ Length, $L = 180 \text{ n}$
gpd180	Pmos	Width, $W_P = 5.1 \mu$ Length, $L = 180 \text{ n}$



The completed Schematic for all the three dimensions are shown in Figure – 2.1, Figure – 2.2 and Figure – 2.3.

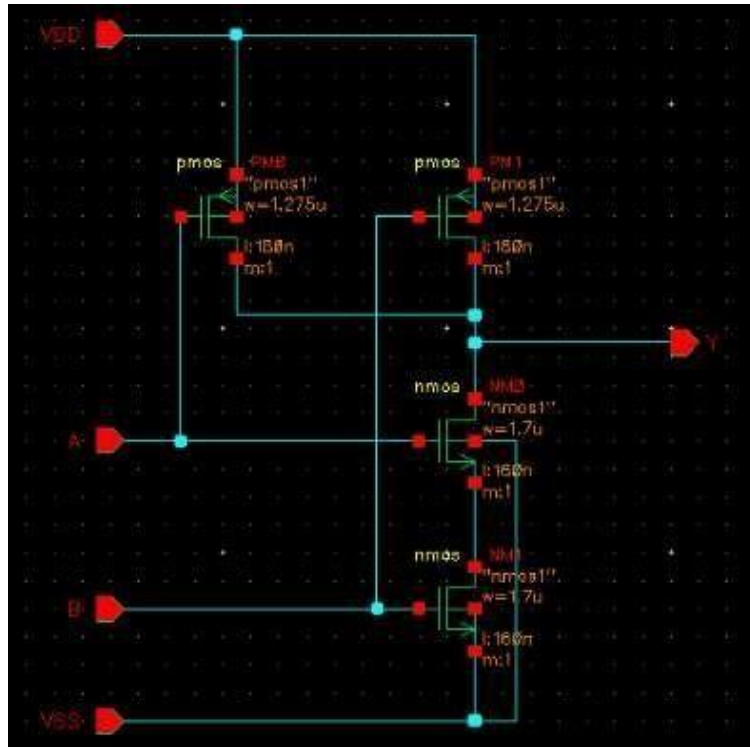


Figure – 2.1: Schematic Capture of 2 – input CMOS NAND Gate (NAND2X1)

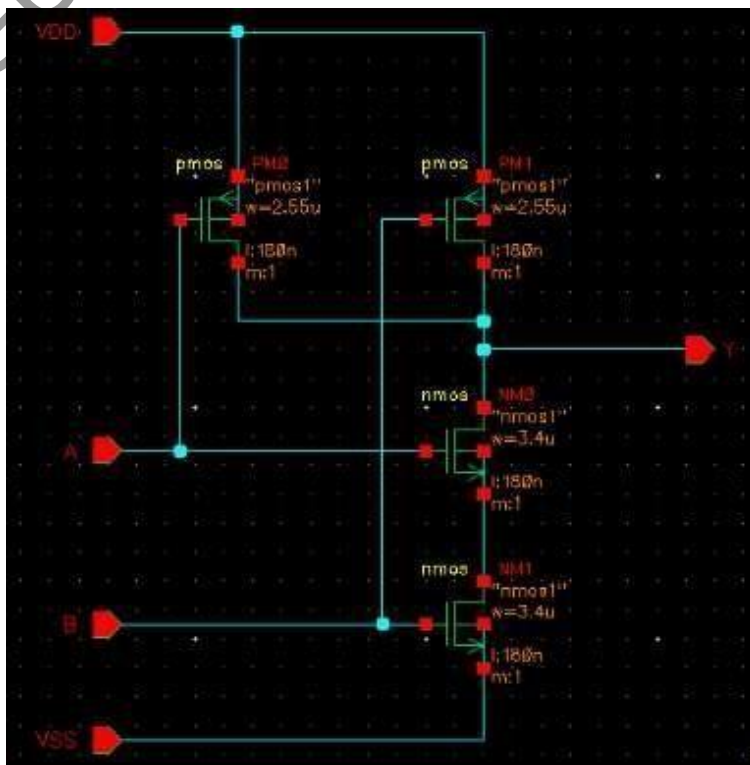
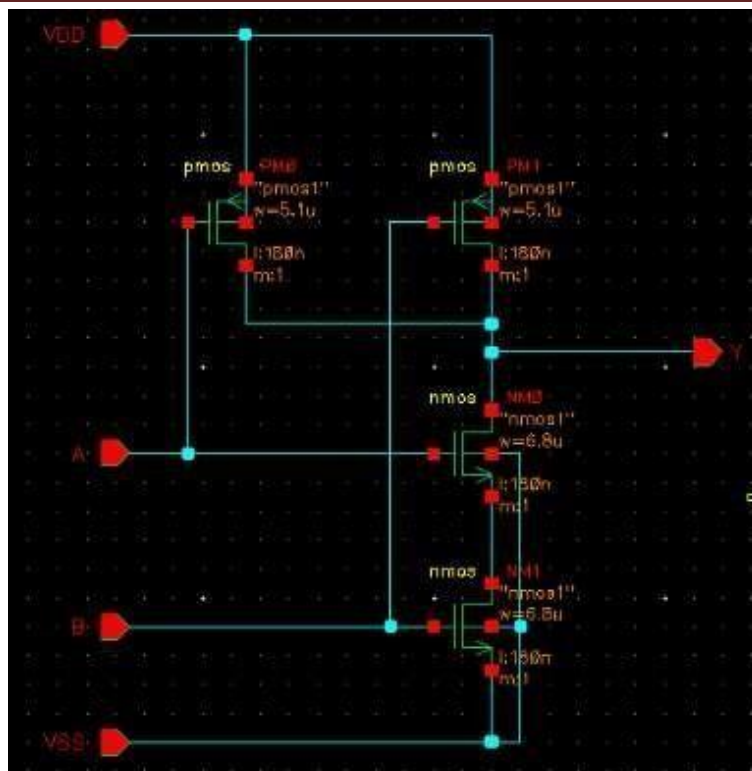
 


Figure – 2.2: Schematic Capture of 2 – input CMOS NAND Gate with drive strength 2(NAND2X2)

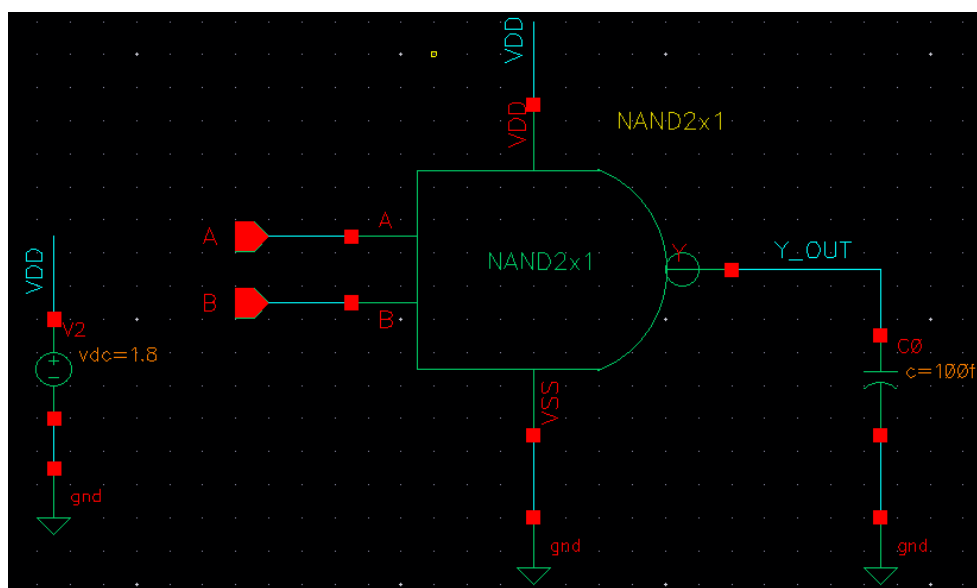


**Figure – 2.3: Schematic Capture of 2 – input CMOS NAND Gate with drive strength 2(NAND2X4)**  
The symbol for the CMOS NAND Gate is shown in Figure – 2.4.



**Figure – 2.4: Symbol of 2 – input NAND Gate**

#### FUNCTIONAL SIMULATION:



**Figure – 2.5: Test Schematic for 2 – input CMOS NAND Gate**

The Simulated waveforms can be seen as shown in Figure – 2.9.



**Figure – 2.9: Transient Analysis of 2 – input CMOS NAND Gate**

The delay values are obtained using the “Calculator” option as demonstrated in Lab – 01. The results are tabulated as shown in Table – 12.

**Table – 12: Values of Delay for 2 – input CMOS NAND2X1, NAND2X2 and NAND 2X4**

NAND Type	MOSFET	Length	Width	tpLH	tpHL	tpd
NAND2X1	PMOS	180n	$1.5 * 850n = 1.275u$	3.720E-10	3.340E-10	3.530E-10
	NMOS		$2 * 850n = 1.7u$			
NAND2X2	PMOS	180n	$1.5 * 850n * 2 = 2.55u$	2.610E-10	2.200E-10	2.400E-10
	NMOS		$2 * 850n * 2 = 3.4u$			
NAND2X4	PMOS	180n	$1.5 * 850n * 4 = 5.1u$	1.900E-10	1.650E-10	1.780E-10
	NMOS		$2 * 850n * 4 = 6.8u$			

Solution – (b):

#### SCHEMATIC CAPTURE:

Following the techniques demonstrated in Lab – 01, Create a New Library, a New Cell View and instantiate the devices as per the Schematic of 2 – input CMOS NAND Gate. The device parameters for the NMOS and PMOS Transistors are listed in Table – 13.

**Table – 13: Device parameters for 2 – input CMOS NAND Gate with  $\frac{W_p}{W_n} = \frac{40}{20}$**

Library Name	Cell Name	Comments / Properties
gpd180	Nmos	Width, $W_N = 20 u$ Length, $L = 180 n$
gpd180	Pmos	Width, $W_P = 40 u$ Length, $L = 180 n$

The Schematic as per the dimensions of NMOS and PMOS transistors listed above is shown in Figure – 2.10.

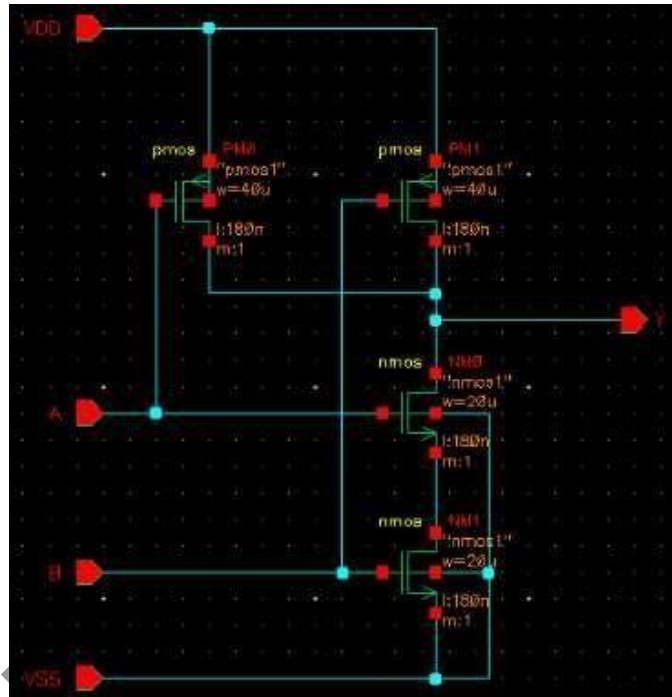


Figure – 2.10: Schematic for 2 – input CMOS NAND with  $\frac{W_p}{W_n} = \frac{40}{20}$   
Symbol for the Schematic in Figure – 2.10 is shown in Figure – 2.11.

 


Figure – 2.11: Symbol for 2 – input CMOS NAND with  $\frac{W_p}{W_n} = \frac{40}{20}$

#### FUNCTIONAL SIMULATION:

The Test Schematic for the functionality check of the 2 – input CMOS NAND Gate is shown in Figure – 2.12.

 


Figure – 2.12: Test Schematic for 2 – input CMOS NAND with  $\frac{W_p}{W_n} = \frac{40}{20}$



 


Figure – 2.14: Simulated Waveforms for 2 – input CMOS NAND with  $\frac{W_p}{W_n} = \frac{40}{20}$

The values of delay elements are tabulated in Table – 14.

Table – 14: Delay Elements for 2 – input CMOS NAND Gate with  $\frac{W_p}{W_n} = \frac{40}{20}$   
(Pre Layout **Simulation**)

MOSFET	Length	Width	tpLH	tpHL	tpd
PMOS	180n	40u	3.64E-11	1.55E-10	9.57E-11
NMOS	180n	20u			

#### LAYOUT:

Follow the techniques demonstrated in Lab – 01 to open the Layout Editor, import the devices from the Schematic, place the devices as per the requirement and complete the routing. The completed layout can be seen as shown in Figure – 2.15.

 


Figure – 2.15: Layout for 2 – input CMOS NAND Gate with  $\frac{W_p}{W_n} = \frac{40}{20}$

#### DRC:

To check for the DRC violations, browse the “assura\_tech.lib” file, select “Assura —> Run DRC”, verify the Layout Design Source, mention a “Run Name”, select “Technology —> gpdk180” and click on “OK” as demonstrated in Lab – 01.

**LVS:**

To check for the LVS violations, select “**Assura** —> **Run LVS**”, verify the Schematic Design Source and the Layout Design Source, mention a “**Run Name**”, select “**Technology** —> **gpdk180**” and click on “**OK**” as demonstrated in Lab – 01.

**QRC:**

To extract the Parasitics, select “**Assura** —> **Quantus**”, select “**Technology** —> **gpdk180**”, “**Output** —> **Extracted View**” from the “**Setup**” option, select “**Extraction Type** —> **RC**” and “**Ref Node** —> **VSS**” from the “**Extraction**” and click on “**OK**” as demonstrated in Lab – 01. The result can be checked from the Library Manager.

**BACKANNOTATION:**

Import the parasitics into the Test Schematic and re-run the simulation to check their impact by calculating the delay elements as demonstrated in Lab – 01.

The values of delay are shown in Table – 15.

Table – 15: Delay Elements for 2 – input CMOS NAND Gate with  $\frac{W_p}{W_n} = \frac{40}{20}$  (Post Layout **Simulation**)

<b>MOSFET</b>	<b>Length</b>	<b>Width</b>	<b>tpLH</b>	<b>tpHL</b>	<b>tpd</b>
PMOS	180n	40u	3.64E-11	1.55E-10	9.57E-11
NMOS	180n	20u			

### LAB – 03: COMMON SOURCE AMPLIFIER WITH PMOS CURRENT MIRROR LOAD

#### Objective:

- Capture the Schematic of a Common Source Amplifier with PMOS Current Mirror Load and find its Transient Response and AC Response. Measure the UGB and Amplification Factor by varying transistor geometries, study the impact of variation in width to UGB.
- Draw the layout of Common Source Amplifier, use optimum layout methods. Verify DRC and LVS, extract the parasitics and perform the post layout simulation, compare the results with pre layout simulations. Record the observations.

#### Solution – (a):

#### SCHEMATICCAPTURE:


Following the techniques demonstrated in Lab – 01, Create a New Library using the option “File → New → Library”, create a New Cell View upon selecting the newly created library using the option “File → New → Cell View” and instantiate the required devices using the “Create → Instance” option.

The device parameters are listed in Table–16.

Table –16: Width and Length of NMOS and PMOS Transistors


LibraryName	CellName	Comments/Properties
gpdk180	Nmos	Width, $W_N = 6 \mu$ Length, $L = 180 \text{ n}$
gpdk180	Pmos	Width, $W_P = 8.85 \mu$ Length, $L = 180 \text{ n}$

The completed Schematic is shown in Figure–3.1.

 

**Figure – 3.1: Schematic of Common Source Amplifier with PMOS Current Mirror Load**


The symbol for the Common Source Amplifier with PMOS Current Mirror Load is shown in Figure – 3.2.

 

**Figure – 3.2: Symbol of Common Source Amplifier with PMOS Current Mirror Load**

**FUNCTIONAL SIMULATION:**

Using the symbol created, build the Test Schematic. Create a New Cell View, instantiate the symbol of Common Source Amplifier with PMOS Current Mirror Load, DC Voltage Source, Current Source, AC Voltage Source, Capacitance, Resistance and Ground, connect the using wires

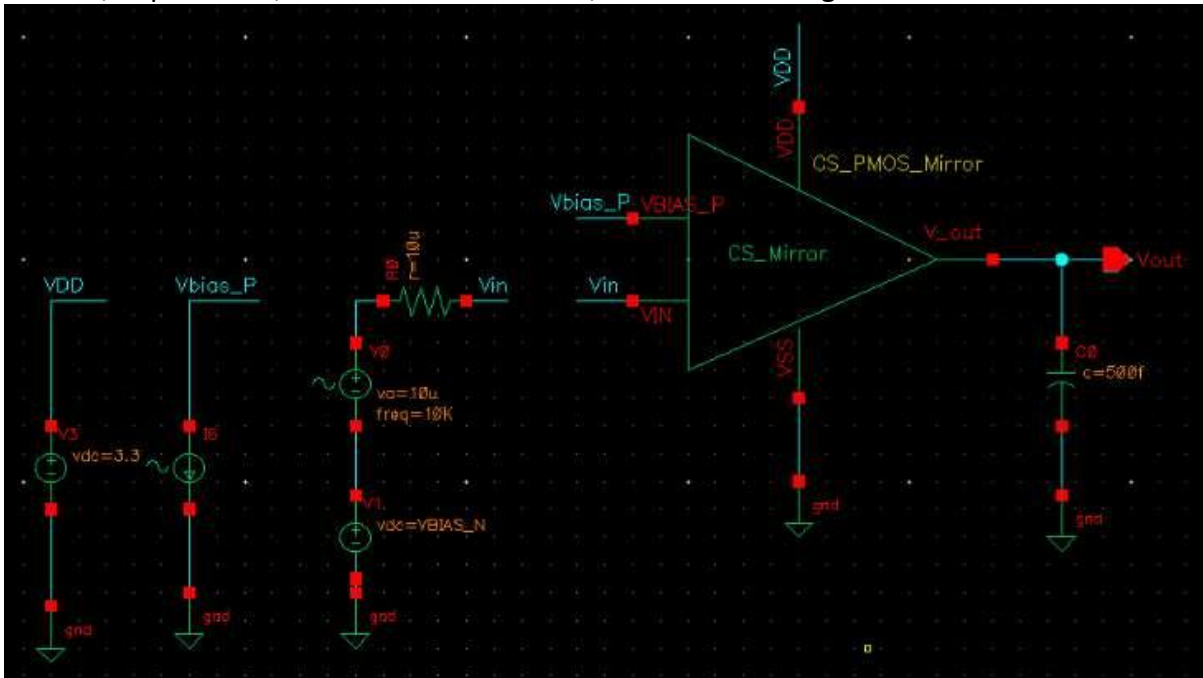


**Figure – 3.3: Test Schematic for 2 – input CMOS NAND Gate**

The parameters for remaining devices are shown in Table – 17.

Library Name	Cell Name	Comments / Properties
analogLib	vdc	DC voltage = 3.3 V (VDD)
analogLib	vdc	DC voltage = VBIAS_N V (Vin)
analogLib	isin	DC current = 100u A (Vbias_P)
analogLib	vsin	AC Magnitude = 1 V, Amplitude = 10u V, Frequency = 10K Hz (Vin)
analogLib	cap	Capacitance = 500f F
analogLib	res	Resistance = 10u Ohms
analogLib	gnd	


**Table – 17: Parameters for the devices used in Test Schematic**

The Simulated waveforms can be seen as shown in Figure – 3.5 and Figure – 3.6.

 

**Figure – 3.5: Transient Analysis**



 


**Figure – 3.6: AC Analysis**

To measure the Gain and Unity Gain Bandwidth, go back to the ADE L window, select “**Results → Direct Plot → AC Magnitude & Phase**” as shown in Figure – 3.7.

The Test Schematic window pops up, select the output net as shown in Figure – 3.8 and click on “**Esc**” key on the keyboard.

The waveform can be seen as shown in Figure – 3.9. The marker placed on the low frequency part of the response gives the DC Gain, use the bind key “**M**” to place the marker.

Place a horizontal cursor at “**0 dB**” and the crossing frequency gives the Unity Gain Bandwidth (UGB) as shown in Figure 3.9.

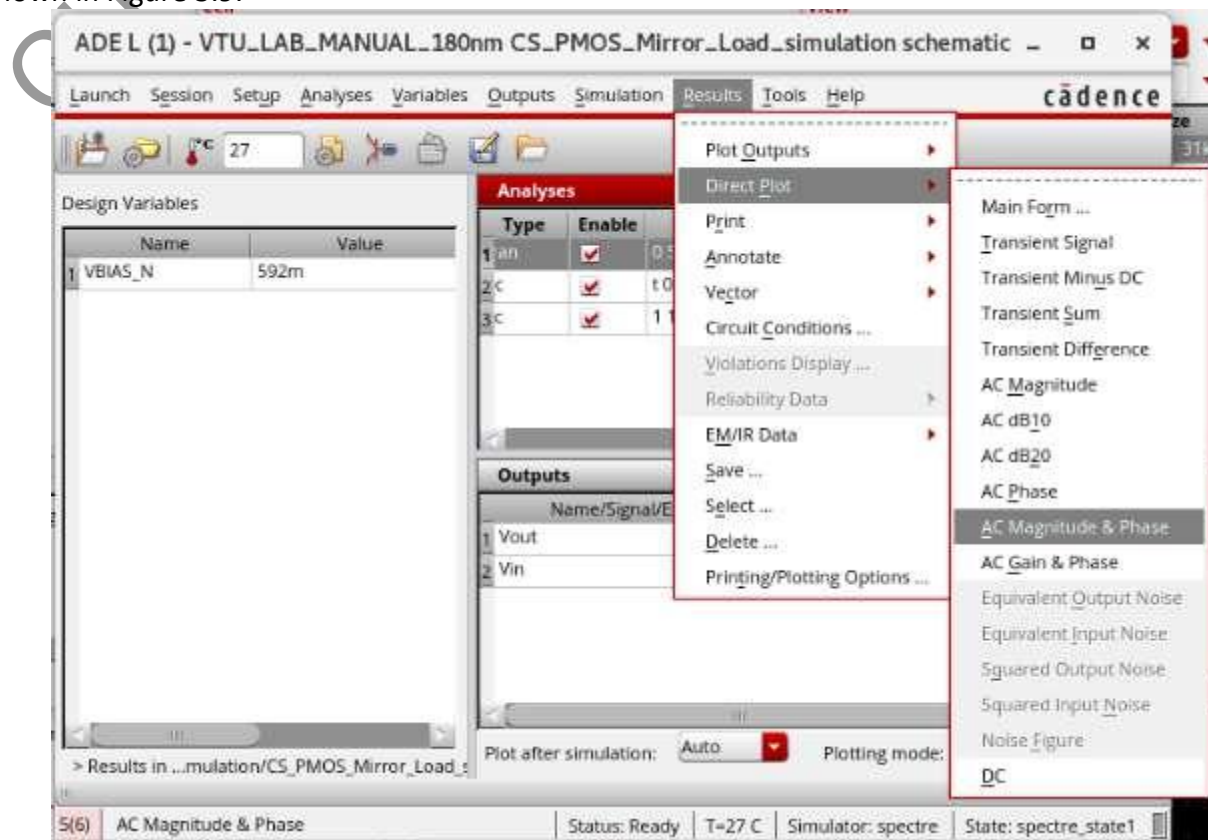

**Figure – 3.7: Results → Direct Plot → AC Magnitude & Phase**

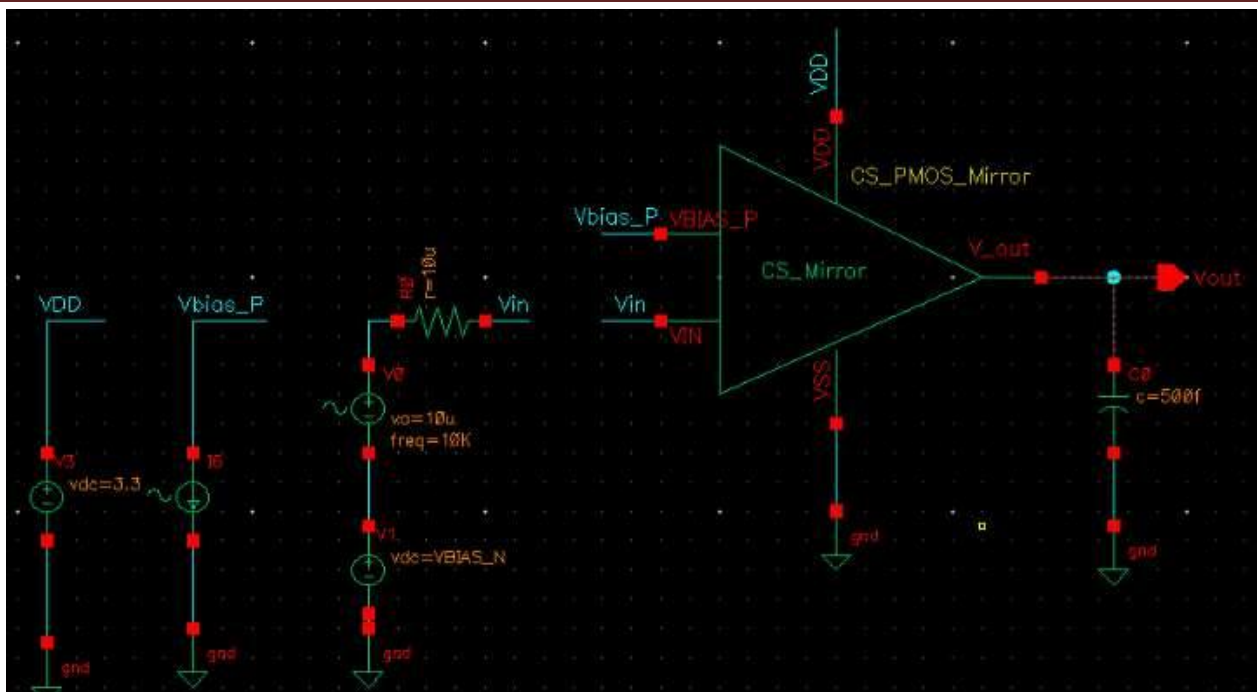


Figure – 3.8: Selecting Output Net from the Test Schematic

 


Figure – 3.9: Gain and Phase plot

#### Solution – (b): LAYOUT:

Follow the techniques demonstrated in Lab – 01 to open the Layout Editor, import the devices from the Schematic, place the devices as per the requirement and complete the routing. The completed layout can be seen as shown in Figure – 3.10.



**Figure – 3.10: Layout for Common Source Amplifier with PMOS Current Mirror Load**

#### **DRC:**

To check for the DRC violations, browse the “assura\_tech.lib” file, select “Assura → Run DRC”, verify the Layout Design Source, mention a “Run Name”, select “Technology → gpdk180” and click on “OK” as demonstrated in Lab – 01.

#### **LVS:**

To check for the LVS violations, select “Assura → Run LVS”, verify the Schematic Design Source and the Layout Design Source, mention a “Run Name”, select “Technology → gpdk180” and click on “OK” as demonstrated in Lab – 01.

#### **QRC:**

To extract the Parasitics, select “Assura → Quantus”, select “Technology → gpdk180”, “Output → Extracted View” from the “Setup” option, select “Extraction Type → RC” and “Ref Node → VSS” from the “Extraction” and click on “OK” as demonstrated in Lab – 01. The result can be checked from the Library Manager.

#### **BACKANNOTATION:**

Import the parasitics into the Test Schematic and re-run the simulation to check their impact by calculating the delay elements as demonstrated in Lab – 01.



## LAB – 04: 2 – STAGE OPERATIONAL AMPLIFIER

### Objective:

- a) Capture the Schematic of a 2 – Stage Operational Amplifier and measure the following:
  1. UGB
  2. dB Bandwidth
  3. Gain Margin and Phase Margin with and without coupling capacitance
  4. Use the Op-Amp in the Inverting and Non-Inverting configuration and verify its functionality
  5. Study the UGB, 3 dB Bandwidth, Gain and Power Requirement in Op-Amp by varying the stage wise transistor geometries and record the observations
- b) Draw the layout of 2 – stage Operational Amplifier with the maximum transistor width set to 300 (in 180 / 90/ 45n m Technology), choose appropriate transistor geometries as per the results obtained in 4(a). Use optimum layout methods. Verify DRC and LVS, extract the parasitics and perform the post layout simulation, compare the results with pre layout simulations. Record the observations.


### Solution – (a):

#### SCHEMATIC CAPTURE:

**Table – 18: Device Parameters for 2 – Stage Operational Amplifier**

Library Name	Transistor	Cell Name	Comments / Properties
gpdK045	M0, M1	pmos2v	Width, W = 465 n Length, L = 150 n
gpdK045	M3, M4	nmos2v	Width, W = 490 n Length, L = 150 n
gpdK045	M5, M7	nmos2v	Width, W = 1.09 u Length, L = 150 n
gpdK045	M2	pmos2v	Width, W = 10 u Length, L = 150 n
gpdK045	M6	nmos2v	Width, W = 6.88 u Length, L = 150 n
gpdK045	M8	pmoscap2v	Calculated Parameter = Capacitance Capacitance = 250.043 f

The completed Schematic as per the dimensions mentioned in Table – 18 is shown in Figure – 4.2.

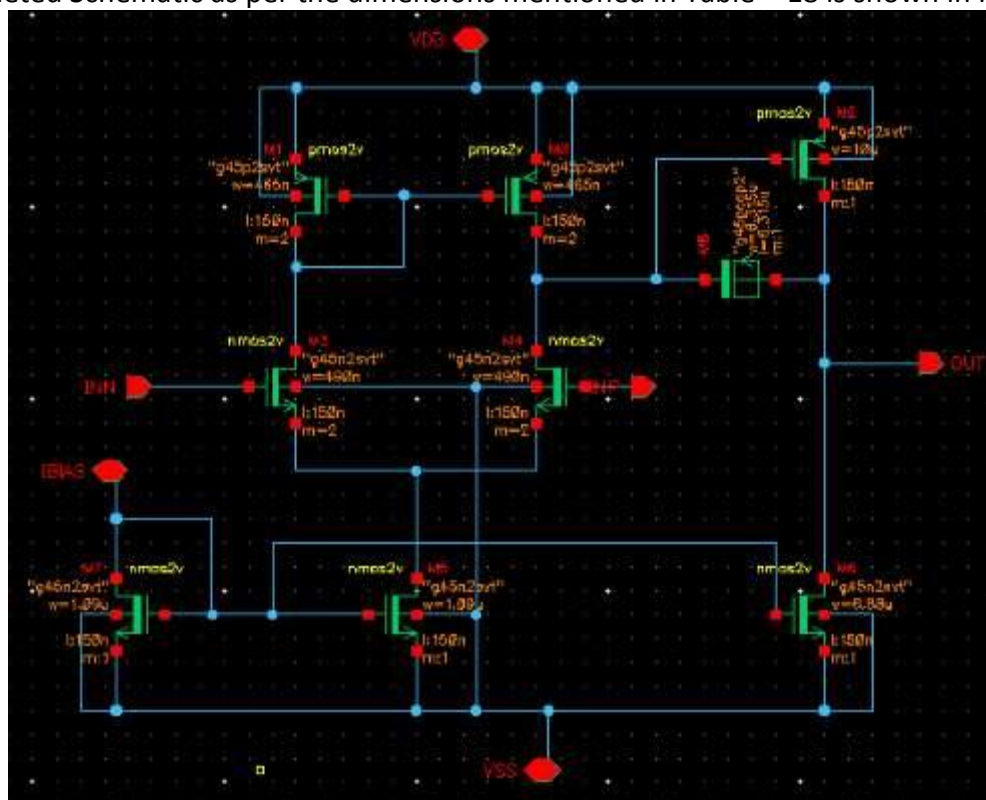

**Figure – 4.2: Schematic of 2 – Stage Operational Amplifier**

The Symbol created according to the Techniques demonstrated in Lab – 01 is shown in Figure – 4.3.

 


Figure – 4.3: Symbol for 2 – Stage Operational Amplifier

#### FUNCTIONAL SIMULATION USING ADE EXPLORER AND ASSEMBLER:

Table – 19: Device Parameters for 2 – Stage Operational Amplifier Test Schematic

Library Name	Cell Name	Comments / Properties
analogLib	vdc	DC voltage = vdd V
analogLib	vdc	DC voltage
analogLib	vpulse	Voltage 1 = vdc + 0.3 V, Voltage 2 = vdc - 0.3 V, Period = 10u s, Rise time = 10p s, Fall time = 10p s
analogLib	idc	DC current = ibias A
analogLib	cap	Capacitance = CL F
analogLib	gnd	

The Test Schematic after completion of all the interconnections can be seen as shown in Figure – 4.4.

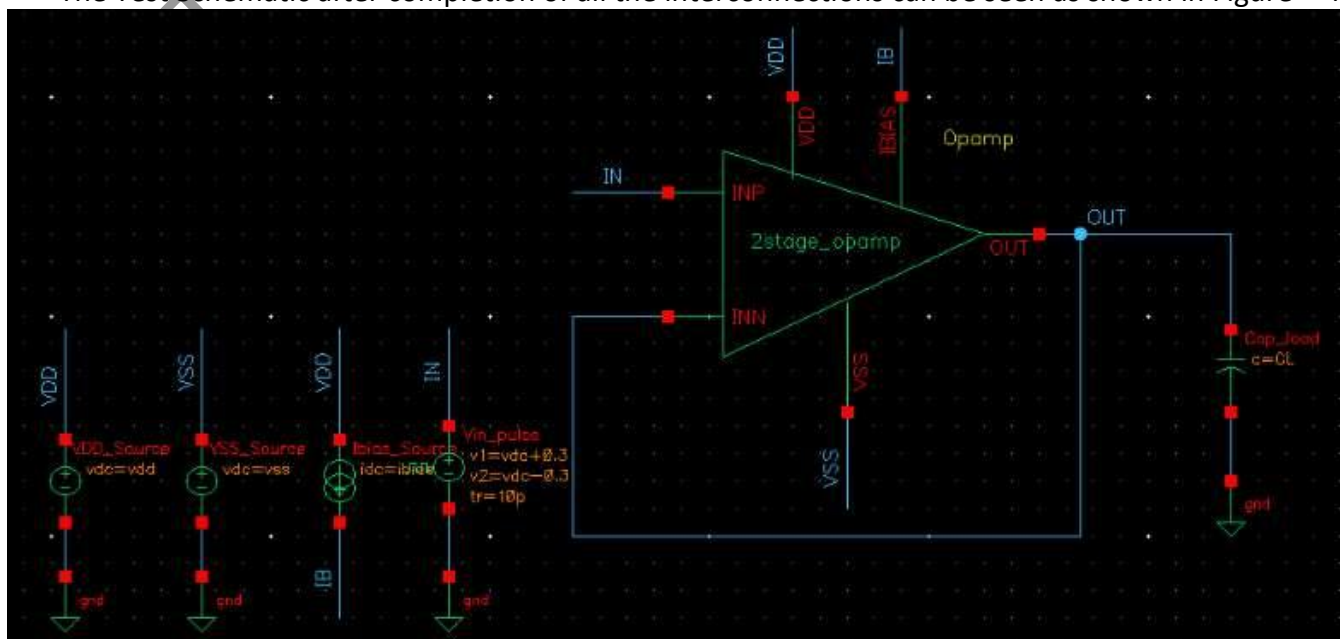


Figure – 4.4: Test Schematic for 2 – Stage Operational Amplifier

The specification that has to be achieved on simulating the design are as follows:

- Slew Rate  $\geq 50$  MV/s
- DC Open Loop Gain  $\geq 60$  dB (1000 V/V)
- Unity Gain Bandwidth  $\geq 50$  MH
- Output Offset  $\leq \pm 10$  mV
- Settling Time  $\leq 50$  ns

The steps to be carried out are listed below:

#### Step – 1:

Select “Launch → ADE Explorer” as shown in Figure – 4.5.

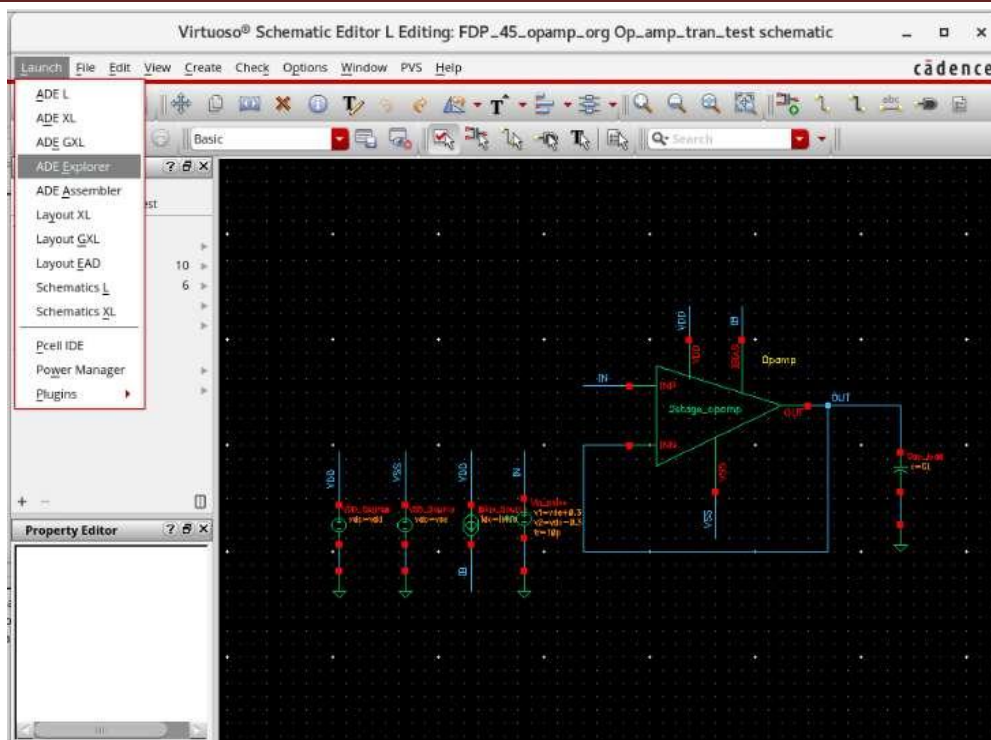


Figure – 4.5: Launch → ADE Explorer

Name of the Variable	Value
CL	1p
ibias	10u
vdc	1
vdd	2
vss	0



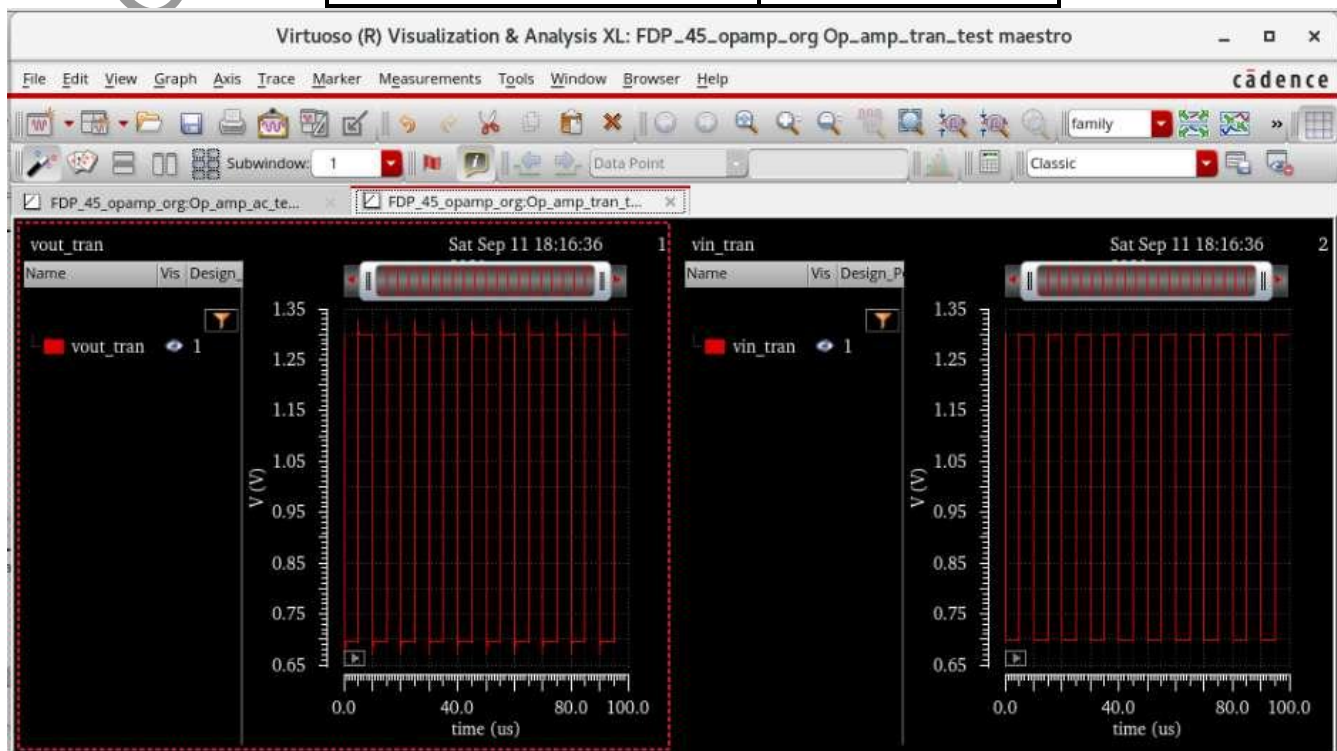


Figure – 4.40: Plotted Waveforms

 


**Figure – 4.44: Isolated Waveforms**

Use left mouse click and drag and drop to combine the waveforms as shown in Figure – 4.45.

 

**Figure – 4.45: Combined Waveforms**


Use the bind key “M” to setup a Marker at the required time instance as shown in Figure – 4.46.

 

**Figure – 4.46: Waveform with Marker**

Use the bind key “H” to setup horizontal cursors at 1.294 V and 1.306 V as shown in Figure – 4.47.



 

**Figure – 4.47: Horizontal cursors at 1.294 V and 1.306 V**

Use the zooming options to zoom-in and zoom-out as and when required. Setup a marker on the lower horizontal cursor as shown in Figure – 4.48.




**Figure – 4.48: Marker on the 2<sup>nd</sup> horizontal cursor**

The difference between the timing instances gives the **Settling Time** as **12.5n s**. Without closing the waveform window, open the “maestro” in the ADE Assembler. For this simulation, the output dc value is 1.298 V and the input dc value is 1.3 V. The difference gives the **DC Offset (1.298 V – 1.3 V = 2m V)**. From the AC Analysis curve, set the marker on the low frequency portion of the signal as shown in Figure – 4.49.

The marker reading gives the **DC Open Loop Gain** which is **50.98 dB**.

Setup a horizontal cursor at **0 dB** as shown in Figure – 4.50. The point of intersection of the cursor with the AC Analysis curve gives the Unity Gain Bandwidth.

The **Unity Gain Bandwidth** is measured as **84.51M Hz**.

 

**Figure – 4.49: DC Open Loop Gain – 50.98 dB**



 


Figure – 4.50: Unity Gain Bandwidth – 84.51M Hz

### GAIN MARGIN AND PHASE MARGIN:

The Schematic for measuring the Gain Margin and Phase Margin is shown in Figure – 4.68.


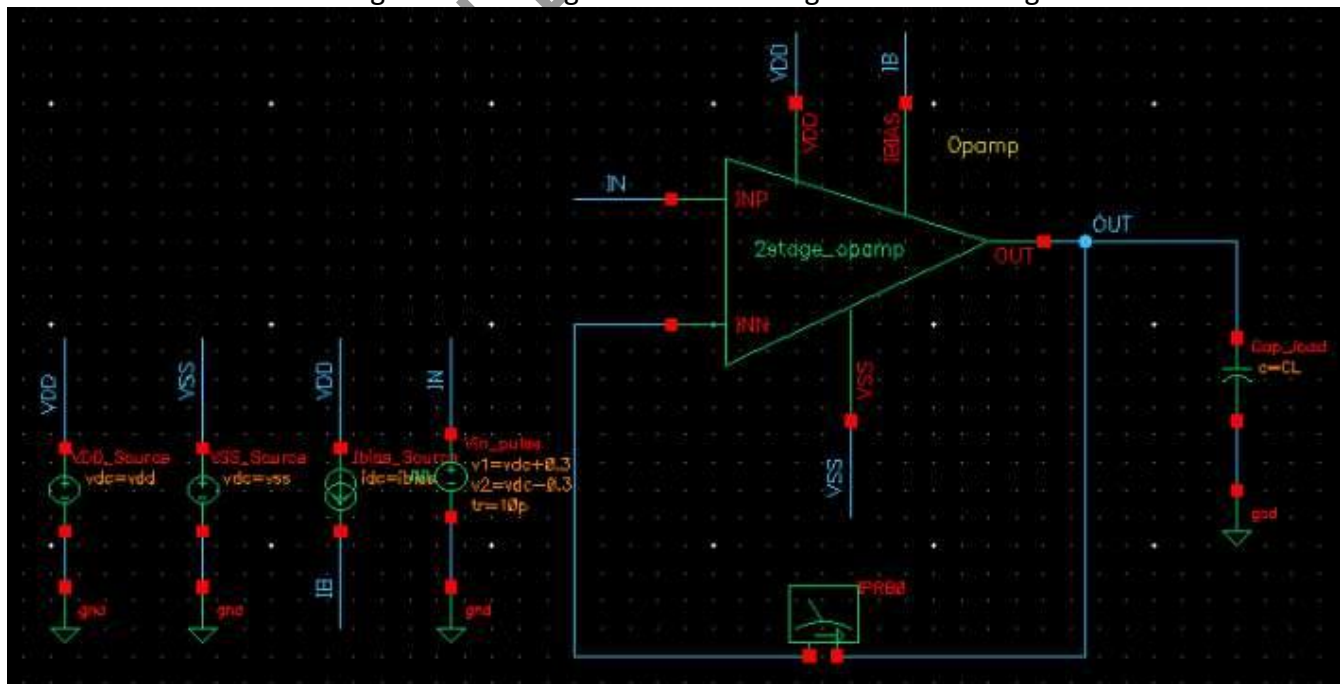


Figure – 4.68: Schematic for Gain Margin and Phase Margin measurement

The “iprobe” (available in “analogLib”) acts as a signal source for the stability analysis. Create a Test Copy for the Stability Analysis as shown in Figure – 4.69.

### LAYOUT:

Follow the techniques demonstrated in Lab – 01 to open the Layout Editor, import the devices from the Schematic, place the devices as per the requirement and complete the routing. The completed layout can be seen as shown in Figure – 4.76.

 

**Figure – 4.76: Layout for 2 – Stage Operational Amplifier**

#### **DRC:**

To check for the DRC violations, browse the “assura\_tech.lib” file, select “Assura → Run DRC”, verify the Layout Design Source, mention a “Run Name”, select “Technology → gpdk045” and click on “OK” as demonstrated in Lab – 01.

#### **LVS:**

To check for the LVS violations, select “Assura → Run LVS”, verify the Schematic Design Source and the Layout Design Source, mention a “Run Name”, select “Technology → gpdk045” and click on “OK” as demonstrated in Lab – 01.

#### **QRC:**

To extract the Parasitics, select “Assura → Quantus”, select “Technology → gpdk180”, “Output → Extracted View” from the “Setup” option, select “Extraction Type → RC” and “Ref Node → VSS” from the “Extraction” and click on “OK” as demonstrated in Lab – 01. The result can be checked from the Library Manager.

#### **BACKANNOTATION:**

Import the parasitics into the Test Schematic and re-run the simulation to check their impact by calculating the delay elements as demonstrated in Lab – 01.

## Demonstration Experiments

### Lab 9: UART

**Aim:** Write a verilog code for UART and carry out the following:

- To Verify the Functionality using test Bench
- Synthesize Design using constraints
- Tabulate Reports using various Constraints
- Identify Critical Path and calculate Max Operating Frequency

**Tool Required:**


- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

**Design Information and Block Diagram:**

The **UART** is “Universal Asynchronous Receiver/Transmitter”, and it is an inbuilt IC within a micro-controller but not like a communication protocol (I2C & SPI). The main function of UART is to serial data communication. In UART, the communication between two devices can be done in two ways namely serial data communication and parallel data communication.

The transmitter section includes three blocks namely transmit hold register, shift register and also control logic. Likewise, the receiver section includes a receive hold register, shift register, and control logic. These two sections are commonly provided by a baud-rate-generator. This generator is used for generating the speed when the transmitter section & receiver section has to transmit or receive the data.

Fig: UART

 

**Creating a Workspace :**

- Create a new sub-Directory for the Design and open a terminal from the Sub-Directory.

**a) Functional Verification using Test Bench**

**Source Code – Transmitter :**

```
// This code contains the UART Transmitter. This transmitter is able
// to transmit 8 bits of serial data, one start bit, one stop bit,
// and no parity bit. When transmit is complete o_Tx_done will be
// driven high for one clock cycle.
// Set Parameter CLKS_PER_BIT as follows:
// CLKS_PER_BIT = (Frequency of i_Clock)/(Frequency of UART)
// Example: 25 MHz Clock, 115200 baud UART
// (25000000)/(115200) = 217
```

```
module UART_TX
#(parameter CLKS_PER_BIT = 217)
(
    input    i_Clock,
    input    i_TX_DV,
    input    [7:0] i_TX_Byte,
    output    o_TX_Active,
    output reg o_TX_Serial,
```

```

output    o_TX_Done
);

parameter IDLE = 3'b000;
parameter TX_START_BIT = 3'b001;
parameter TX_DATA_BITS = 3'b010;
parameter TX_STOP_BIT = 3'b011;
parameter CLEANUP    = 3'b100;
reg [2:0] r_SM_Main    = 0;
reg [7:0] r_Clock_Count = 0;
reg [2:0] r_Bit_Index = 0;
reg [7:0] r_TX_Data    = 0;
reg    r_TX_Done    = 0;
reg    r_TX_Active = 0;

always @(posedge i_Clock)
begin
case (r_SM_Main)
IDLE :
    begin
        o_TX_Serial <= 1'b1;    // Drive Line High for Idle
        r_TX_Done    <= 1'b0;
        r_Clock_Count <= 0;
        r_Bit_Index <= 0;
        if (i_TX_DV == 1'b1)
        begin
            r_TX_Active <= 1'b1;
            r_TX_Data <= i_TX_Byte;
            r_SM_Main <= TX_START_BIT;
        end
    end
    else
        r_SM_Main <= IDLE;
    end //
case: IDLE
// Send out Start Bit. Start bit = 0
TX_START_BIT :
    begin
        o_TX_Serial <= 1'b0;

        // Wait CLKS_PER_BIT-1 clock cycles for start bit to finish
        if (r_Clock_Count < CLKS_PER_BIT-1)
        begin
            r_Clock_Count <= r_Clock_Count + 1;
            r_SM_Main    <= TX_START_BIT;
        end
        else
        begin
            r_Clock_Count <= 0;
            r_SM_Main    <= TX_DATA_BITS;
        end
    end
end // case: TX_START_BIT
// Wait CLKS_PER_BIT-1 clock cycles for data bits to finish
TX_DATA_BITS :
    begin

```

```
o_TX_Serial <= r_TX_Data[r_Bit_Index];
```

```
if (r_Clock_Count < CLKS_PER_BIT-1)
```

```
begin
```

```
    r_Clock_Count <= r_Clock_Count + 1;
```

```
    r_SM_Main <= TX_DATA_BITS;
```

```
end
```

```
else
```

```
begin
```

```
    r_Clock_Count <= 0;           // Check if we have sent out all bits
```

```
if (r_Bit_Index < 7)
```

```
begin
```

```
    r_Bit_Index <= r_Bit_Index + 1;
```

```
    r_SM_Main <= TX_DATA_BITS;
```

```
end
```

```
else
```

```
begin
```

```
    r_Bit_Index <= 0;
```

```
    r_SM_Main <=
```

```
    TX_STOP_BIT;
```

```
end
```

```
end
```

```
end // case: TX_DATA_BITS
```

```
// Send out Stop bit. Stop bit = 1
```

```
TX_STOP_BIT :
```

```
begin
```

```
    o_TX_Serial <= 1'b1;
```

```
// Wait CLKS_PER_BIT-1 clock cycles for Stop bit to finish
```

```
if (r_Clock_Count < CLKS_PER_BIT-1)
```

```
begin
```

```
    r_Clock_Count <= r_Clock_Count + 1;
```

```
    r_SM_Main <= TX_STOP_BIT;
```

```
end
```

```
else
```

```
begin
```

```
    r_TX_Done <= 1'b1; r_Clock_Count <= 0;
```

```
    r_SM_Main <= CLEANUP;
```

```
    r_TX_Active <= 1'b0;
```

```
end
```

```
end // case: TX_STOP_BIT
```

```
// Stay here 1 clock
```

```
CLEANUP :
```

```
begin
```

```
    r_TX_Done <= 1'b1;
```

```
    r_SM_Main <= IDLE;
```

```
end
```

```
default :
```

```
    r_SM_Main <= IDLE;
```

```
endcase
```

```
end
```

```

assign o_TX_Active = r_TX_Active;

assign o_TX_Done = r_TX_Done;

endmodule

```

#### Source Code – Receiver :

```

// This file contains the UART Receiver. This receiver is able to
// receive 8 bits of serial data, one start bit, one stop bit,
// and no parity bit. When receive is complete o_rx_dv will be
// driven high for one clock cycle.
// Set Parameter CLKS_PER_BIT as follows:
// CLKS_PER_BIT = (Frequency of i_Clock)/(Frequency of UART)
// Example: 25 MHz Clock, 115200 baud UART
// (25000000)/(115200) = 217

```

```

module UART_RX
#(parameter CLKS_PER_BIT =
217)(
    input    i_Clock,
    input    i_RX_Serial,
    output   o_RX_DV,
    output [7:0] o_RX_Byte
);

parameter IDLE      = 3'b000;
parameter RX_START_BIT = 3'b001;
parameter RX_DATA_BITS = 3'b010;
parameter RX_STOP_BIT = 3'b011;
parameter CLEANUP    = 3'b100;

reg [7:0] r_Clock_Count = 0;
reg [2:0] r_Bit_Index = 0; //8 bits total
reg [7:0] r_RX_Byte    = 0;
reg  r_RX_DV          = 0;
reg [2:0] r_SM_Main    = 0;

// Purpose: Control RX state machine
always @(posedge i_Clock)
begin
    case (r_SM_Main)
        IDLE :
            Begin
                r_RX_DV <= 1'b0;
                r_Clock_Count <= 0;
                r_Bit_Index <= 0;

                if (i_RX_Serial == 1'b0)          // Start bit detected

                    r_SM_Main <= RX_START_BIT;
                else
                    r_SM_Main <= IDLE;
                end

                // Check middle of start bit to make sure it's still low
                RX_START_BIT :
                    begin

```

```

    if (r_Clock_Count == (CLKS_PER_BIT-1)/2)
    begin
        if (i_RX_Serial == 1'b0)
        begin
            r_Clock_Count <= 0; // reset counter, found the middle
            r_SM_Main <= RX_DATA_BITS;
        end
        else
            r_SM_Main <= IDLE;
        end
        else
        begin
            r_Clock_Count <= r_Clock_Count + 1;
            r_SM_Main <= RX_START_BIT;
        end
    end // case: RX_START_BIT

// Wait CLKS_PER_BIT-1 clock cycles to sample serial data
RX_DATA_BITS :
begin
    if (r_Clock_Count < CLKS_PER_BIT-1)
    begin
        r_Clock_Count <= r_Clock_Count + 1;
        r_SM_Main <= RX_DATA_BITS;
    end
    else
    begin
        r_Clock_Count <= 0;
        r_RX_Byte[r_Bit_Index] <= i_RX_Serial;
        // Check if we have received all bits
        if (r_Bit_Index < 7)
        begin
            r_Bit_Index <= r_Bit_Index + 1;
            r_SM_Main <= RX_DATA_BITS;
        end
        else
        begin
            r_Bit_Index <= 0;
            r_SM_Main <= RX_STOP_BIT;
        end
    end
end // case: RX_DATA_BITS

// Receive Stop bit. Stop bit = 1
RX_STOP_BIT :
begin
    // Wait CLKS_PER_BIT-1 clock cycles for Stop bit to finish
    if (r_Clock_Count < CLKS_PER_BIT-1)
    begin
        r_Clock_Count <= r_Clock_Count + 1;
        r_SM_Main <= RX_STOP_BIT;
    end
    else
    begin
        r_RX_DV <= 1'b1;
    end
end

```

```

        r_Clock_Count <= 0;
        r_SM_Main  <= CLEANUP;
    end
end // case: RX_STOP_BIT
// Stay here 1 clock
CLEANUP :
begin
    r_SM_Main <= IDLE;
    r_RX_DV <= 1'b0;
end
default :
    r_SM_Main <= IDLE;
endcase
end
assign o_RX_DV = r_RX_DV;
assign o_RX_Byte = r_RX_Byte;
endmodule // UART_RX

```

#### Test bench :

```

// This testbench will exercise the UART RX.
// It sends out byte 0x37, and ensures the RX receives it correctly.
`timescale 1ns/10ps
`include "uart_tx.v"
`include "uart_rx.v"
module UART_TB ();
    // Testbench uses a 25 MHz clock
    // Want to interface to 115200 baud UART
    // 25000000 / 115200 = 217 Clocks Per Bit.
    parameter c_CLOCK_PERIOD_NS = 40;
    parameter c_CLKS_PER_BIT    = 217;
    parameter c_BIT_PERIOD      = 8600;
    reg r_Clock = 0;
    reg r_TX_DV = 0;
    wire w_TX_Active, w_UART_Line;
    wire w_TX_Serial;
    reg [7:0] r_TX_Byte = 0;
    wire [7:0] w_RX_Byte;

    UART_RX #(c_CLKS_PER_BIT(c_CLKS_PER_BIT)) UART_RX_Inst
        (.i_Clock(r_Clock),
         .i_RX_Serial(w_UART_Line),
         .o_RX_DV(w_RX_DV),
         .o_RX_Byte(w_RX_Byte)
        );

    UART_TX #(c_CLKS_PER_BIT(c_CLKS_PER_BIT)) UART_TX_Inst
        (.i_Clock(r_Clock),
         .i_TX_DV(r_TX_DV),
         .i_TX_Byte(r_TX_Byte),
         .o_TX_Active(w_TX_Active),
         .o_TX_Serial(w_TX_Serial),
         .o_TX_Done()
        );
    // Keeps the UART Receive input high (default) when

```



```
// UART transmitter is not active
assign w_UART_Line = w_TX_Active ? w_TX_Serial : 1'b1;
always
#(c_CLOCK_PERIOD_NS/2) r_Clock <= !r_Clock;
// Main Testing:
initial
begin
// Tell UART to send a command (exercise TX)
@(posedge r_Clock);
@(posedge r_Clock);
r_TX_DV <= 1'b1;
r_TX_Byte <= 8'h3F;
@(posedge r_Clock);
r_TX_DV <= 1'b0;
end
endmodule
```

### Waveform :

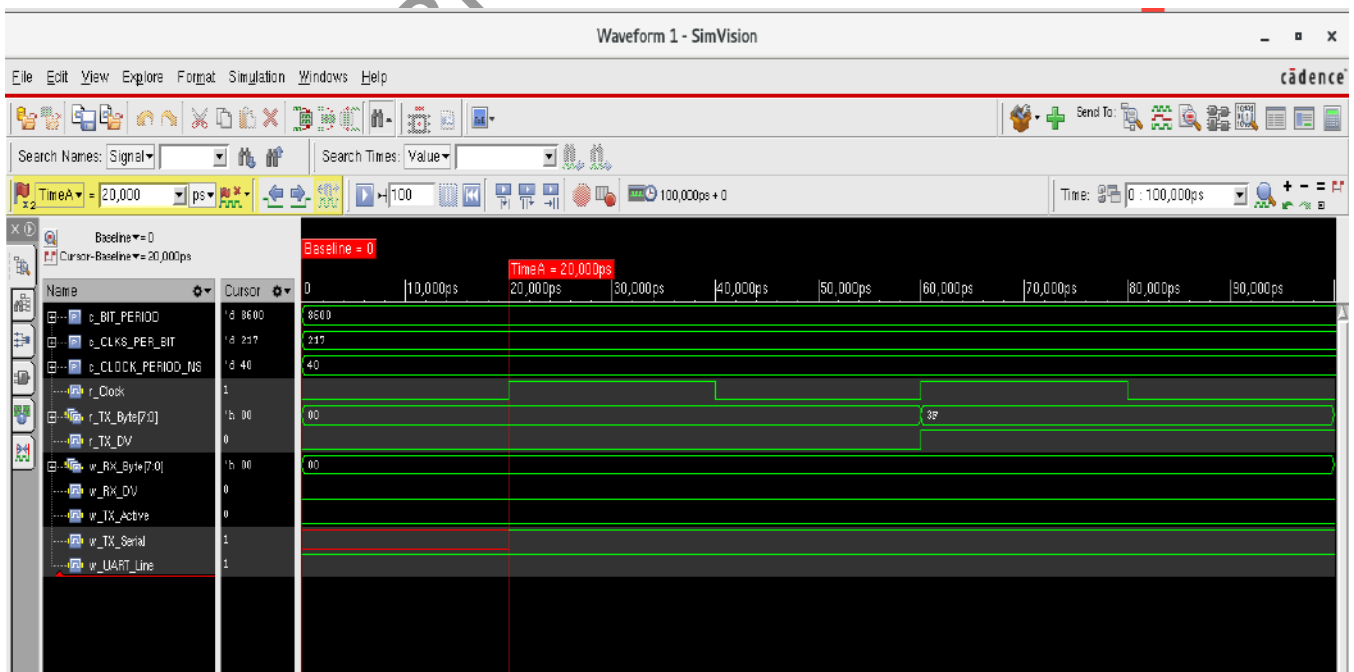
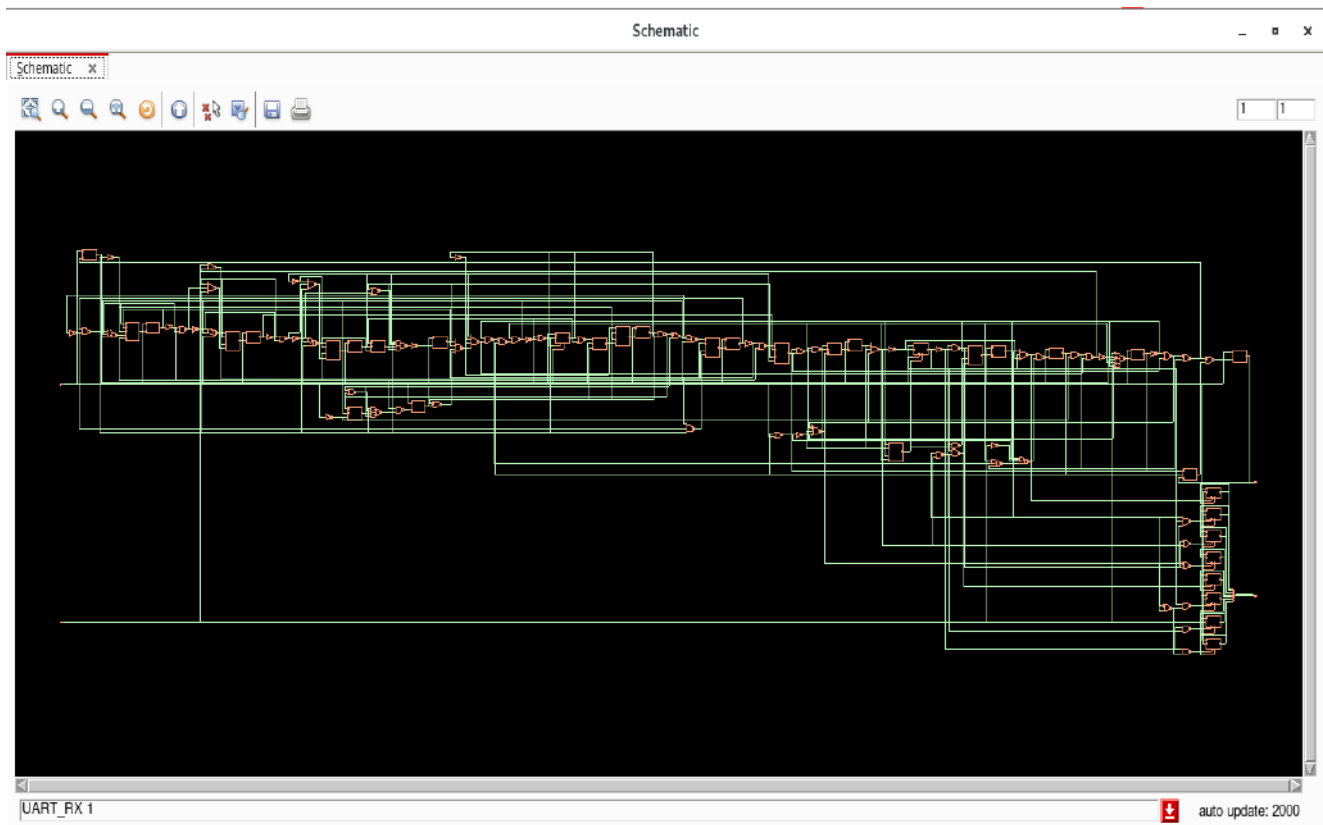


Fig: Simulation Waveform for UART

### b) Synthesize the Design

1. read\_libs /home/install/FOUNDRY/digital/90nm/dig/lib/slow.lib
2. read\_hdl {uart\_tx.v / uart\_rx.v} //Choose any one
3. elaborate
4. read\_sdc constraints\_top.sdc //Reading Top Level SDC
5. set\_db syn\_generic\_effort medium //Setting effort medium
6. set\_db syn\_map\_effort medium
7. set\_db syn\_opt\_effort medium
8. syn\_generic
9. syn\_map
10. syn\_opt //Performing Synthesis Mapping and Optimisation
11. report\_timing > uart\_timing.rep //Generates Timing report for worst datapath and dumps into file
12. report\_area > uart\_area.rep //Generates Synthesis Area report and dumps into a file
13. report\_power > uart\_power.rep //Generates Power Report [Pre-Layout]
14. report\_qor > uart\_qor.rep
15. write\_hdl > uart\_netlist.v //Creates readable Netlist File
16. write\_sdc > uart\_sdc.sdc //Creates Block Level SDC

Synthesis RTL Schematic :**Note :-**

1. You can tabulate Area, Power and Timing Constraints using any of the SDC Constraints as instructed.
2. Make sure, during synthesis the Report File Names are changed so that the latest reports do not overwrite the earlier ones.

## Lab 6: Physical Design

**Aim:** For the synthesized netlist carry out the following any two above experiments:

- Floor planning, identify the placement of pads, placement and Routing

### Tool Required:

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus
- Physical Design: Innovus

### Mandatory Inputs for PD:

- Gate Level Netlist [Output of Synthesis]
- Block Level SDC [Output of Synthesis]
- Liberty Files (.lib)
- LEF Files (Layer Exchange Format)

### Expected Outputs from PD:

- GDS II File (Graphical Data Stream for Information Interchange – Feed In for FabricationUnit).
- SPEF, SDF
  - Make sure the Synthesis for the target design is done and open a terminal from the corresponding workspace.
  - Initiate the Cadence tools and **cmd :innovus** (Press Enter)
  - For Innovus tool, a GUI opens and also the terminal enters into innovus command prompt where in the tool commands can be entered.

Physical Design involves 5 stages as following :

After Importing Design,

- Floor Planning
- Power Planning
- Placement
- CTS (Clock Tree Synthesis)
- RoutingModule

### Importing Design


To Import Design, all the Mandatory Inputs are to be loaded and this can be done either using script files named with .globals and .view/.tcl or through GUI as shown below.

The target design considered here is counter design

The procedure shall remain the same for any other design from the above discussed experiments.
 
### Note :

- For Synthesis, slow.lib was read as input. Each liberty file contains a pre-defined Process, Voltage and Temperature (PVT) values which impact the ease of charge movement.
- Process, Voltage and Temperature individually affect the ease of currents as depicted below.



- Hence, slow.lib contains PVT combination (corner) with **slow** charge movement =>

**Maximum Delay => Worst Performance**

- Similarly, fast.lib contains PVT Combination applicable across its designs to give **Fast** charge movement => **Minimum** Delay => **Best** Performance.
- When these corners are collaborated with the sdc, they can be used to analyse timing for setup in the worst case and hold in the best case.
- All these analysis views are to be manually created either in the form of script or using the GUI.

```
#####
# Generated by: Cadence Encounter 13.23-s047_1
# OS: Linux x86_64(Host ID cadence)
# Generated on: Tue May 24 02:16:38 2016
# Design:
# Command: save_global Default.globals
#####
#
# Version 1.1
#

set ::TimeLib::tsgMarkCellLatchConstructFlag 1
set conf_qxconf_file {NULL}
set conf_qxlib_file {NULL}
set defHierChar {/}
set init_design_settop 0
set init_gnd_net {VSS}
set init_lef_file {lef/gsclib090_translated.lef lef/gsclib090_translated_ref.lef}
set init_mmmc_file {Default.view}
set init_pwr_net {VDD}
set init_verilog {counter_netlist.v}
set lsgCPGainMult 1.000000
set pegDefaultResScaleFactor 1.000000
set pegDetailResScaleFactor 1.000000
```



Script under Default.globals file

```
# Version:1.0 MMMC View Definition File
# Do Not Remove Above Line
create_library_set -name MAX_timing -timing {/root/Desktop/counter/lib/90/slow.lib}
create_library_set -name Min_timing -timing {/root/Desktop/counter/lib/90/fast.lib}
create_constraint_mode -name Constraints -sdc_files {counter_sdc.sdc}
create_delay_corner -name Max_delay -library_set {MAX_timing}
create_delay_corner -name Min_delay -library_set {Min_timing}
create_analysis_view -name Worst -constraint_mode {Constraints} -delay_corner {Max_delay}
create_analysis_view -name best -constraint_mode {Constraints} -delay_corner {Min_delay}
set_analysis_view -setup {Worst} -hold {best}
```


Script under Default.view (or) Default.tcl file

**Note :** Check the paths to properly read in the input files.


- Else, if you would like to import your design using GUI, open the Innovus tool and from the
  - GUI, go to File → Import Design.
- A new pop-up window appears.
- First load the netlist. You can browse for the file and select “Top cell : Auto Assign”.



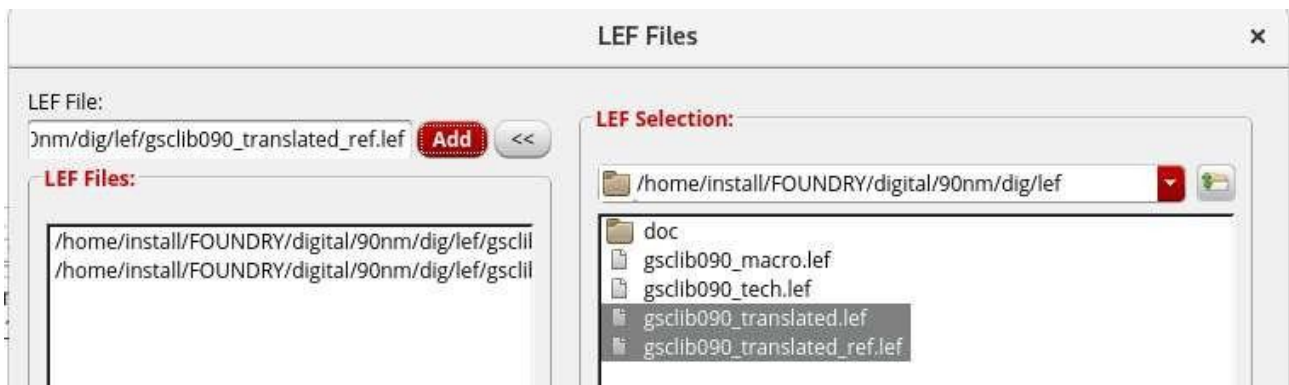
Similarly select your lef files from /home/install/FOUNDRY/digital/90nm/dig/lef/ as shown below.



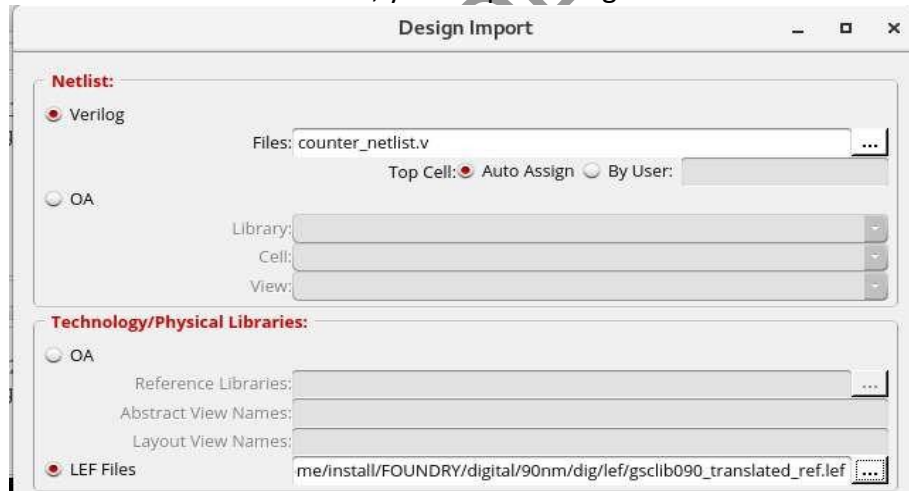
Once both the Netlist and LEF Files are loaded, your import design window is as follows.



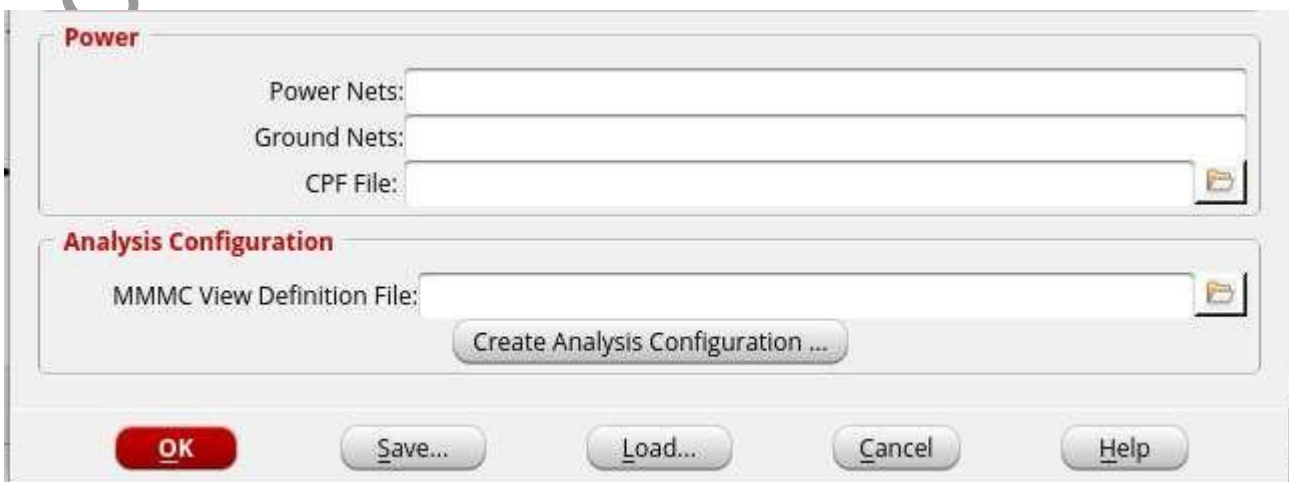- In order to load the Liberty File and SDC, create delay corners and analysis view, select the “Create Analysis Configuration” option at the bottom.



- An MMMC browser Pops Up.

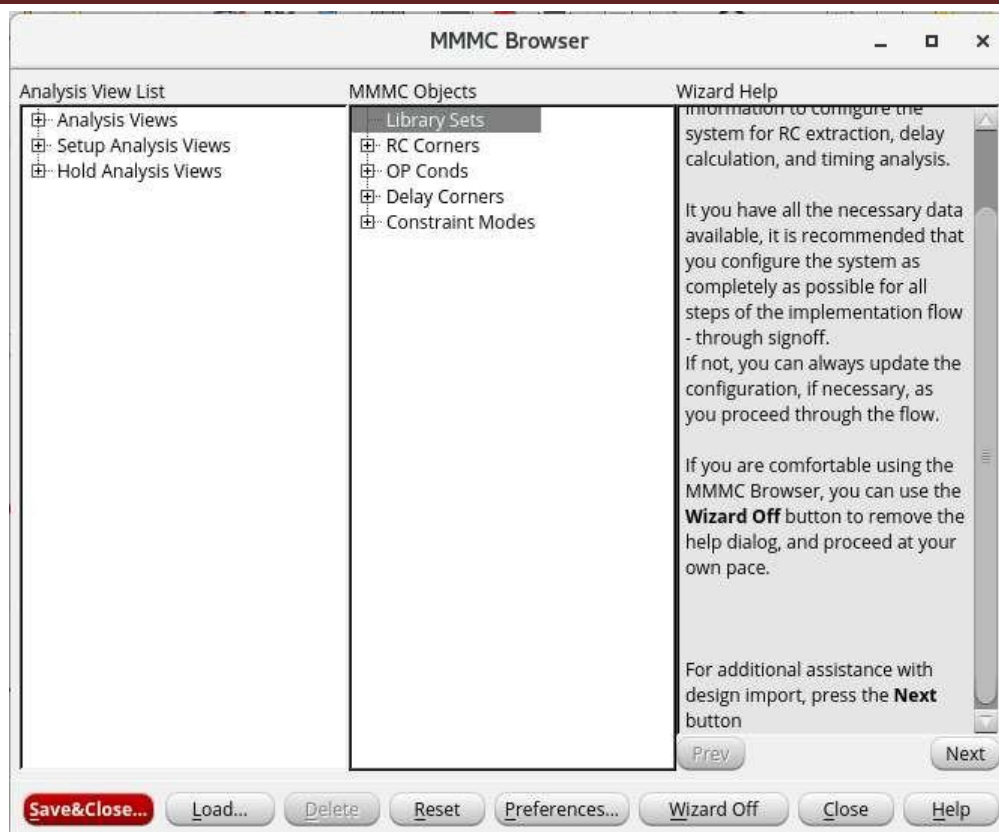


The order of adding the MMMC Objects is as follows.

1. Library Sets
2. RC Corners
3. Delay Corners
4. Constraints (SDC)

Once all of them are added, Analysis Views are created and assigned to Setup and Hold.

In order to add any of the objects, make a right click on the corresponding label → Select New.


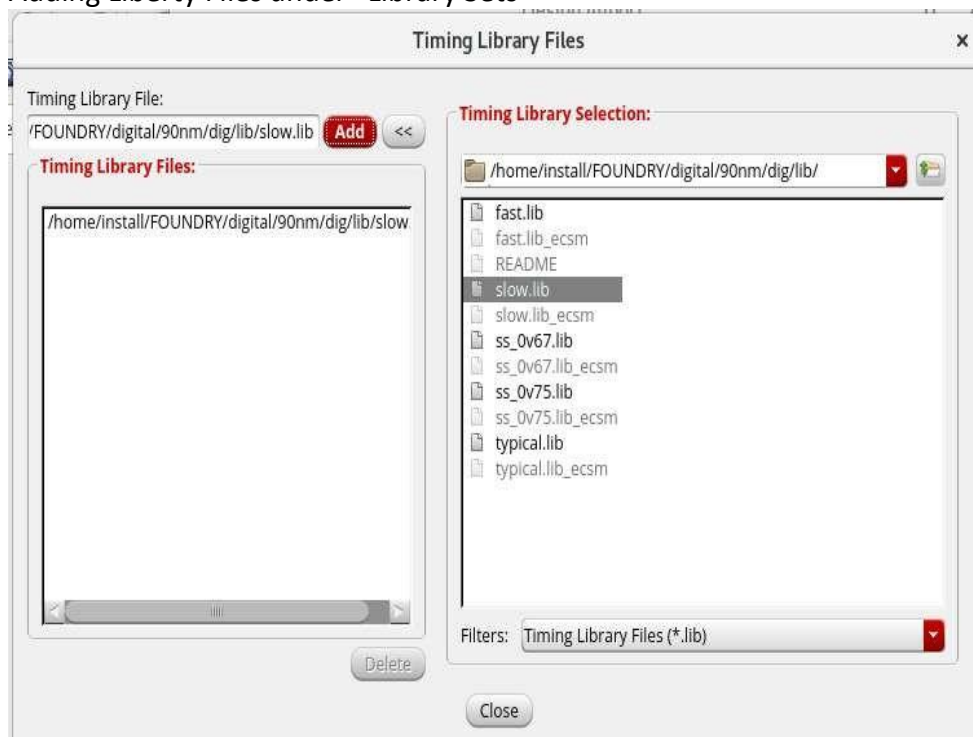
- Adding Liberty Files under “Library Sets”








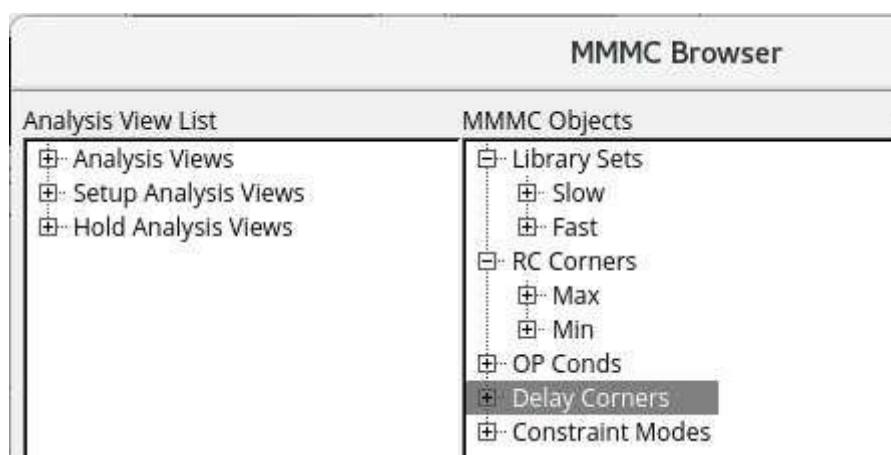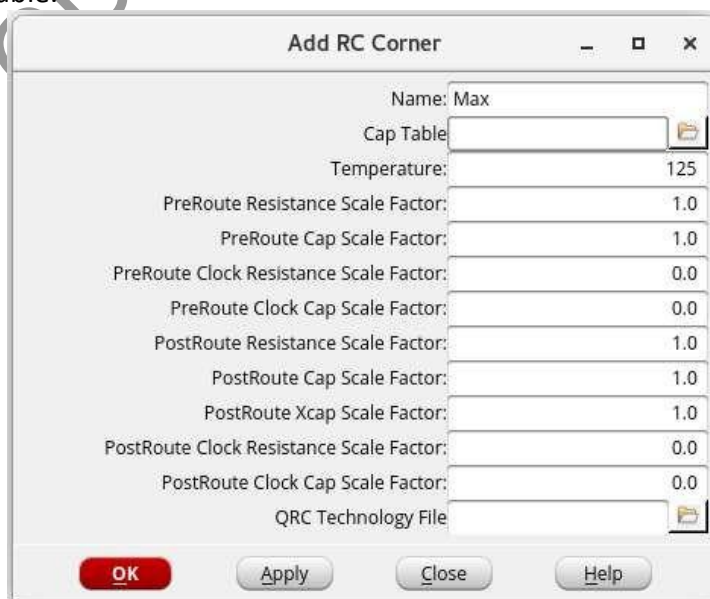- Similarly, add fast.lib with a label Fast or any identifier of your own.
- Adding RC Corners can also be done in a similar process. The temperature value can be found under the corresponding liberty file. Also, cap table and RC Tech files can be added from Foundry where available.



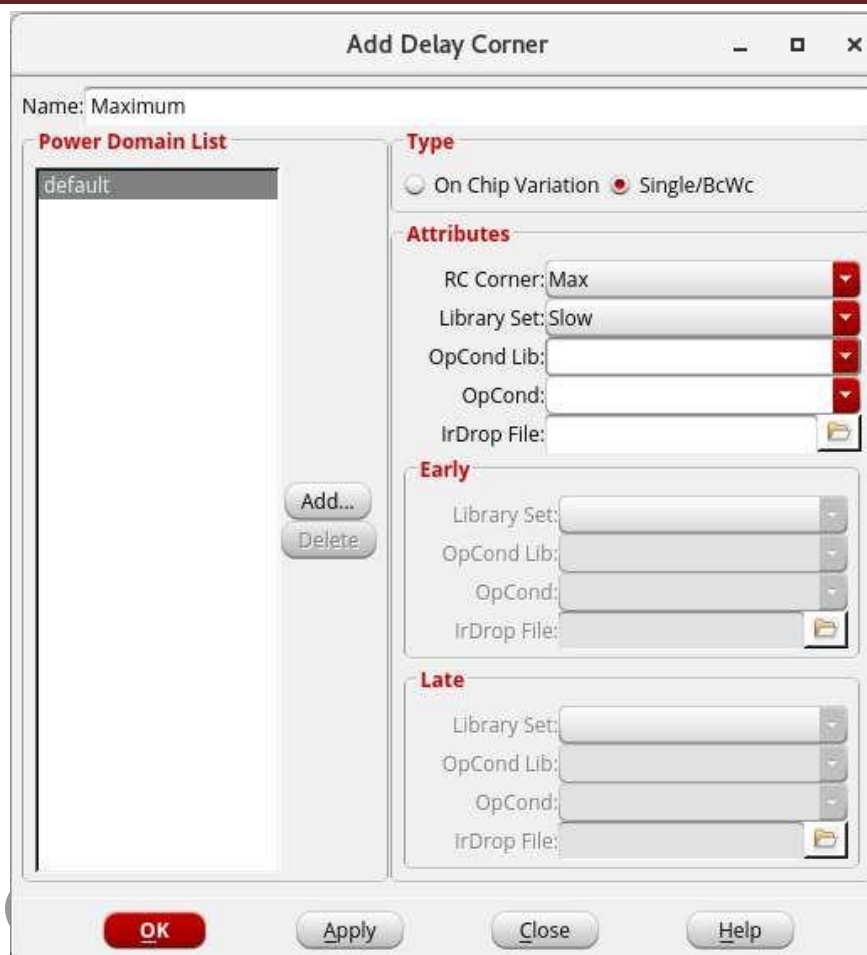- Delay Corners are formed by combining Library Sets with RC Corners.
- An example is shown below.




- Similarly, SDC can be read in under the MMMC Object of “Constraints”.





 - Analysis Views are formed from combinations of SDC and Delay Corner.






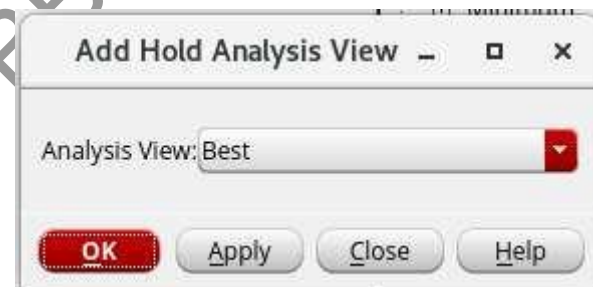 
- Once “Best” and “Worst” Analysis views are created, assign them to Setup and Hold.



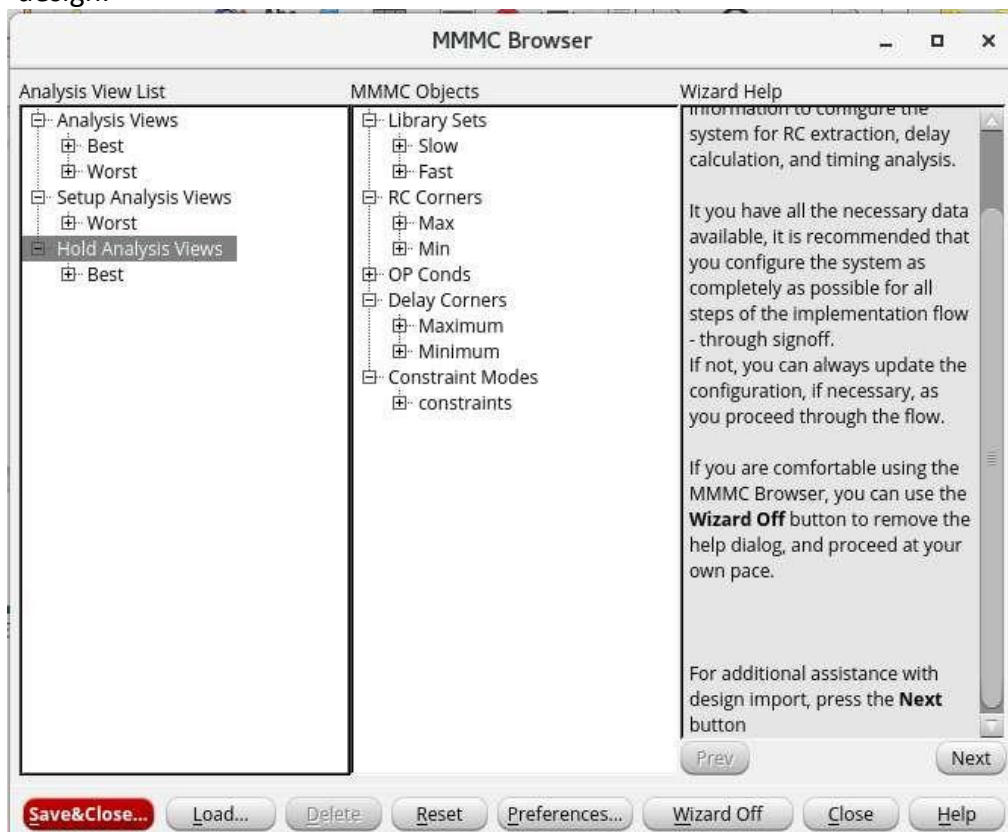- Once all the process is done, Click on “Save&Close” and save the script generated with any name of your choice.
- Make sure the file extension remains .view or .tcl
- After saving the script, go back to Import Design window and Click “OK” to load your design.



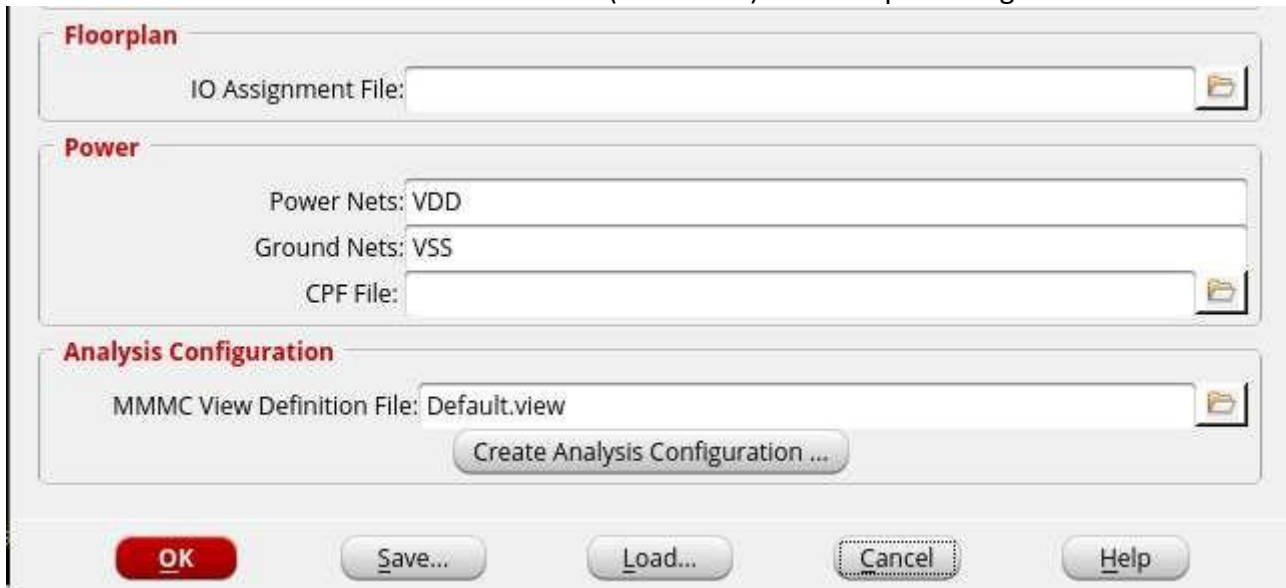- Add Power and Ground Net names (Identifiers) under Import design window.



- A rectangular or square box appears in your GUI if and only if all the inputs are read properly.
- If the box does not appear, check for errors in your log (Either on terminal or log file from pwd)





- The internal area of the box is called "Core Area".
- The horizontal lines running along the width of Core are "Standard Cell Rows". Every alternate of them are marked indicating alternate VDD and VSS rows.
- This setup is called "**Flipped Standard Cell Rows**".

### → Floorplan

Steps under Floorplan :

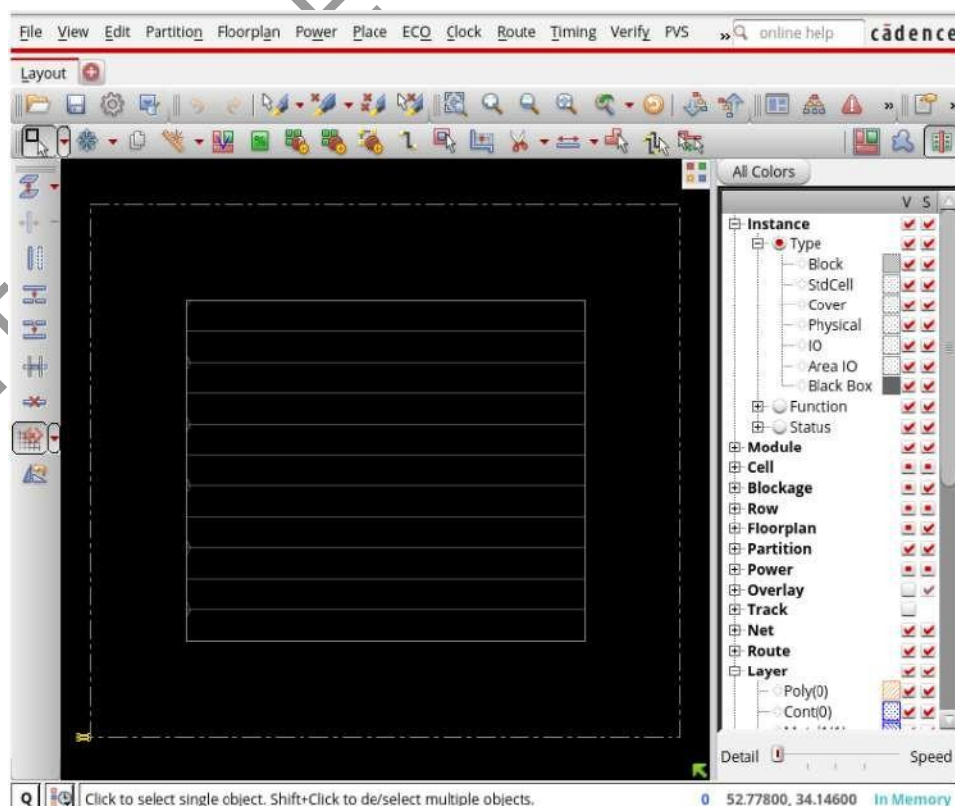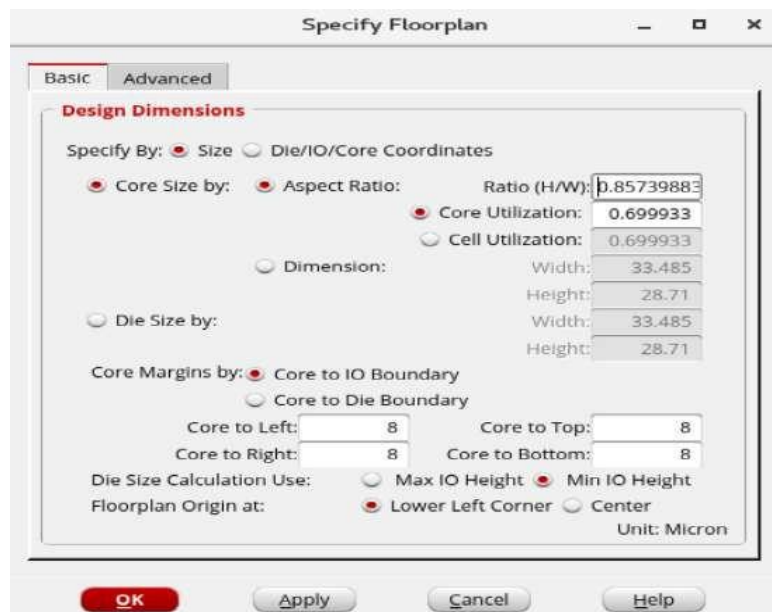1. Aspect Ratio [Ratio of Vertical Height to Horizontal Width of Core]
2. Core Utilisation [The total Core Area % to be used for Floor Planning]
3. Channel Spacing between Core Boundary to IO Boundary
  - Select Floorplan → Specify Floorplan to modify/add concerned values to the above Factors. On adding/modifying the concerned values, the core area is also modified



- The Yellow patch on the Left Bottom are the group of “Unassigned pins” which are to be placed along the IO Boundary along with the Standard Cells [Gates].

### → Power Planning

Steps under Power Planning :

1. Connect Global Net Connects
2. Adding Power Rings
3. Adding Power Strings
4. Special Route

Under Connect Global Net Connects, we create two pins, one for VDD and one for VSS connecting them to corresponding Global Nets as mentioned in Globals file / Power and Ground Nets.

1. Select Power → Connect Global Nets.. to create “Pin” and “Connect to Global Net” as shown and use “Add to list”.
2. Click on “Apply” to direct the tool in enforcing the Pins and Net connects to Design and then Close the window.




- In order to Tap in Power from a distant Power supply, Wider Nets and Parallel connections improve efficiency. Moreover, the cells that would be placed inside the core area are expected to have shorter Nets for lower resistance.
- Hence Power Rings [Around Core Boundary] and Power Stripes [Across Core Boundary] are added which satisfies the above conditions.
- Select Power → Power Planning → Add Rings to add Power rings 'around Core Boundary'.




- Select the Nets from Browse option OR Directly type in the Global Net Names separated by a space being Case and Spelling Sensitive.
- Select the Highest Metals marked 'H' [Horizontal] for Top and Bottom and Metals marked 'V' [Vertical] for Right and Bottom. This is because Highest metals have Highest Widths and thus Lowest Resistance.
- Click on Update after the selection and "Set Offset : Centre in Channel" in order to get the Minimum Width and Minimum Spacing of the corresponding Metals and then Click "OK".

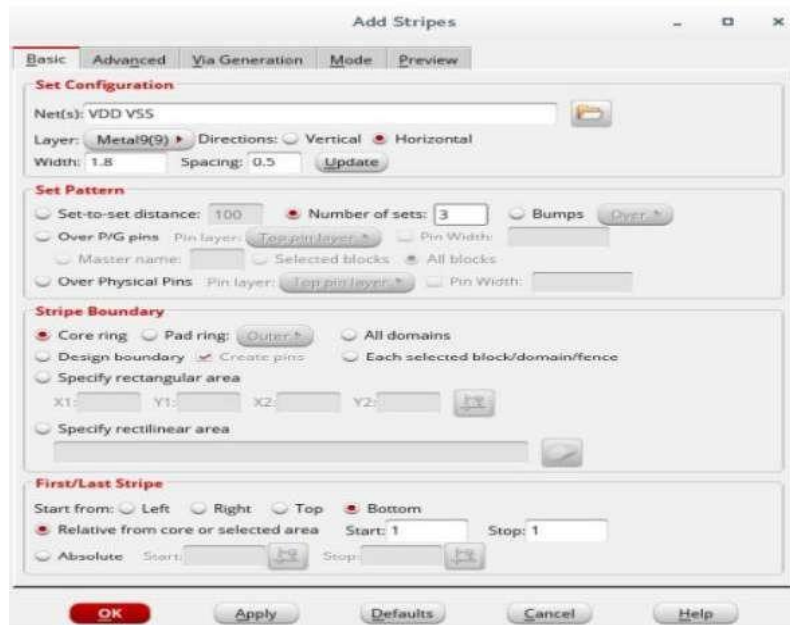- Similarly, Power Stripes are added using similar content to that of Power Rings



Factors to be considered under Power Stripes :

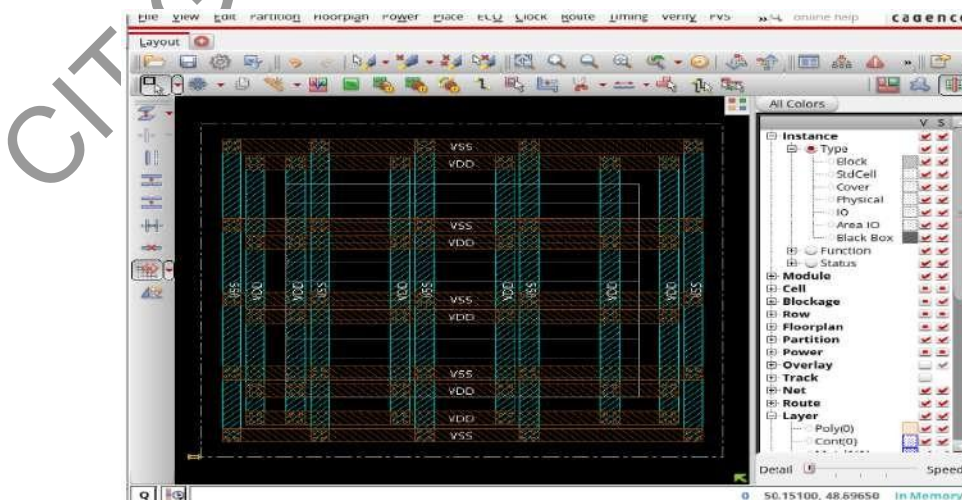- Nets
- Metal and It's Direction
- Width and Spacing [Updated]
- Set to Set Distance = ( Minimum Width of Metal + Min. Spacing ) x 2




- On adding Power Stripes, The Power mesh setup is complete as shown. However, There are no Vias that could connect Metal 9 or Metal 8 directly with Metal 1 [VDD or VSS of Standard Cells are generally made up of Metal 1].
- The connection between the Highest and Lowest Metals is done through Stacking of Vias done using "Special Route".
- To perform Special Route, Select Route → Special Route → Add Nets → OK.
- After the Special Route is complete, all the Standard Cell Rows turn to the Color coded for Metal 1 as shown below.

The complete Power Planning process makes sure Every Standard Cell receives enough power to operate smoothly.




## → Pre – Placement :

 


- After Power Planning, a few Physical Cells are added namely, End Caps and Well Taps.
- End Caps : They are Physical Cells which are added to the Left and Right Core Boundaries acting as blockages to avoid Standard Cells from moving out of boundary.
- Well Taps : They act like Shunt Resistance to avoid Latch Up effects.

To add End Caps, Select Place → Physical Cell → Add End Caps and “Select” the FILL’s from the available list.

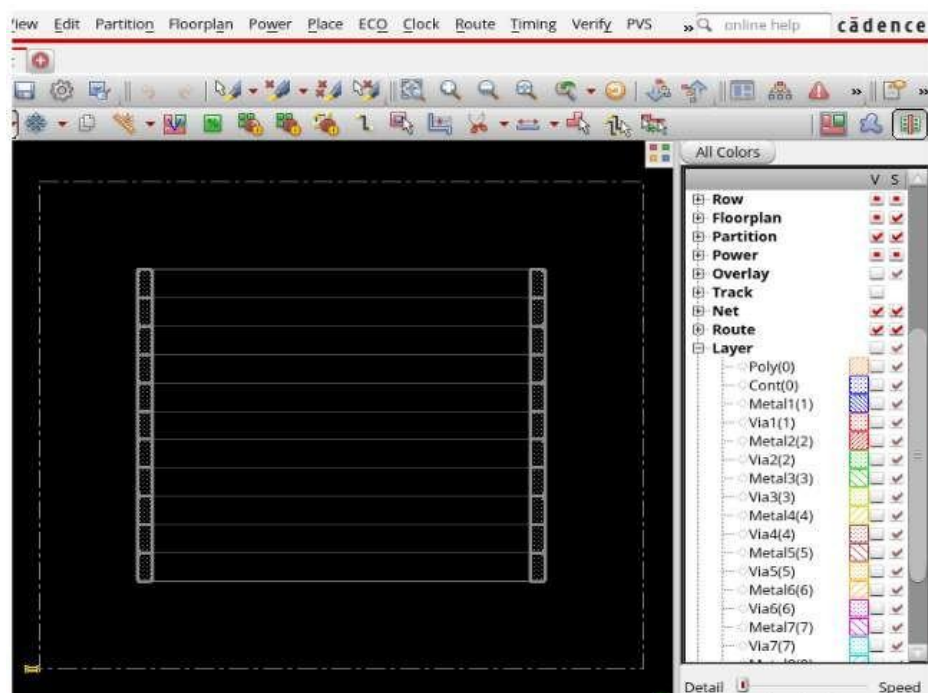
- Higher Fills have Higher Widths. As shown Below, The End Caps are added below your Power Mesh.
- To add Well Taps, Select Place → Physical Cell → Add Well Tap → Select → Fill [X → Strength of Fill = 1,2,4 etc] → Distance Interval [Could be given in range of 30-45u] → OK




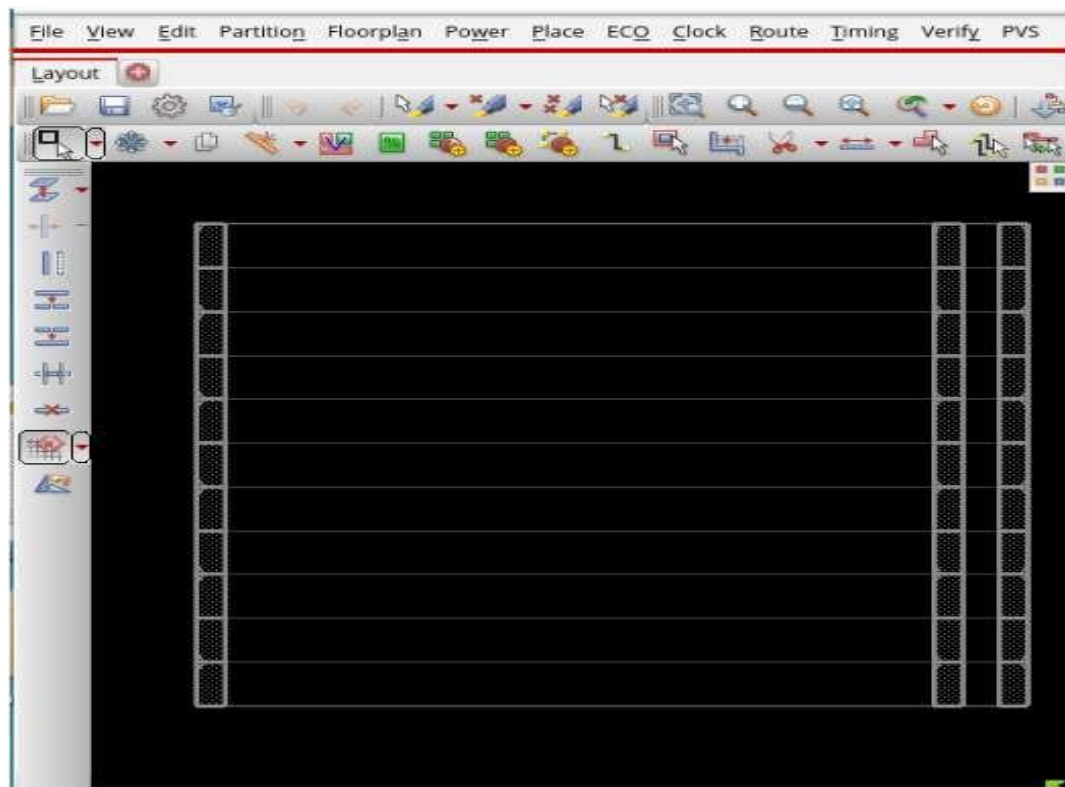


### → Placement

 1. The Placement stage deals with Placing of Standard Cells as well as Pins.
2. Select Place → Place Standard Cell → Run Full Placement → Mode → Enable 'Place I/O Pins' → OK → OK.



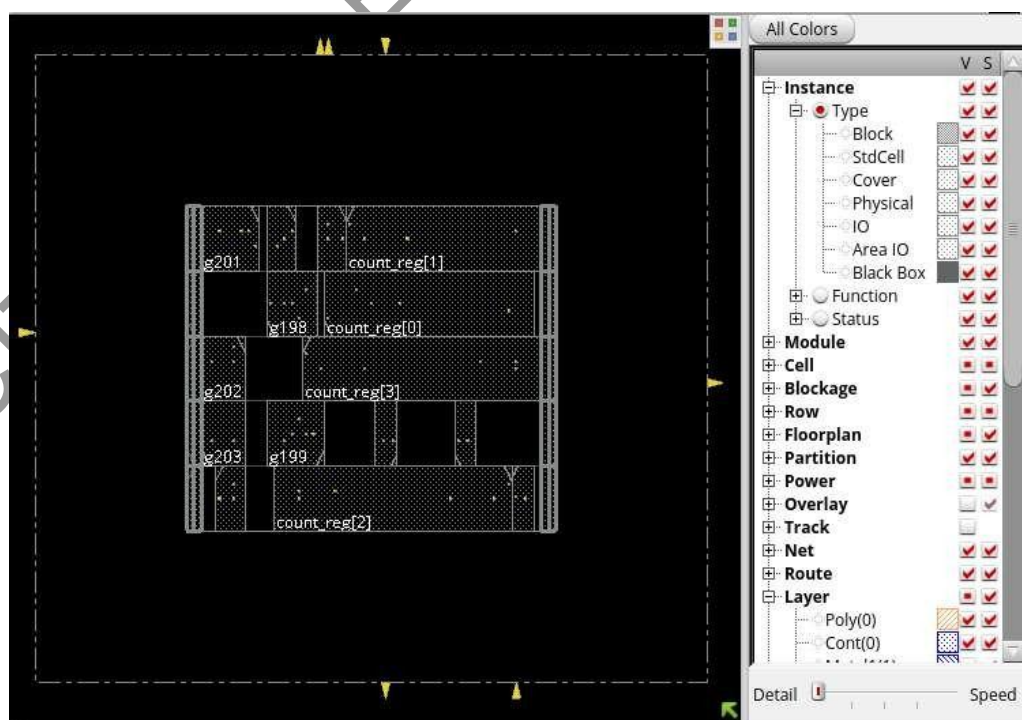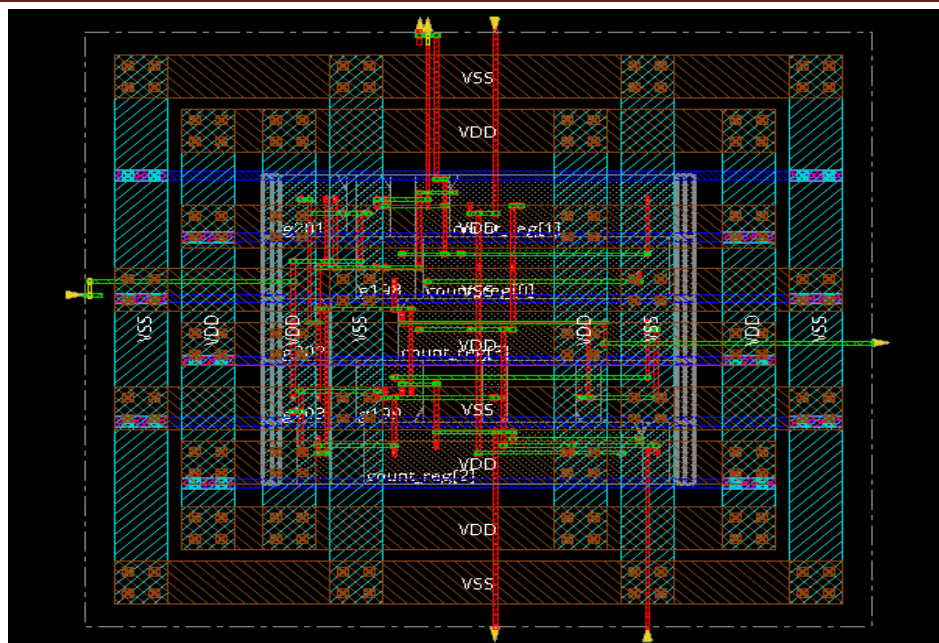- All the Standard Cells and Pins are placed as per the communication between them, i.e., Two communicating Cells are placed as close as possible so that shorter Net lengths can be used for connections as Shorter Net Lengths enable Better Timing Results.



- You can toggle the Layer Visibility from the list on the Right. The List of Layers available are shown on the right under "Layer" tab with colour coding.

#### → Report Generation and Optimization :

- Timing Report :
  - To generate Timing Report, Timing → Report Timing → Design Stage – PreCTS
  - Analysis Type – Setup → OK
  - The Timing report Summary can be seen on the Terminal.
- Area Report :
  - cmd** : report\_area
- Power Report :
  - cmd** : report\_power

```

innovus 9> innovus 9> report_area
Depth  Name          #Inst  Area (um^2)
-----
0       counter          15     134.7282
-

```



Setup views included: Worst			
Setup mode	all	reg2reg	default
WNS (ns):	0.605	0.845	0.605
TNS (ns):	0.000	0.000	0.000
Violating Paths:	0	0	0
All Paths:	16	8	11

DRVs	Real		Total
	Nr nets (terms)	Worst Vio	Nr nets (terms)
max_cap	0 (0)	0.000	0 (0)
max_tran	0 (0)	0.000	0 (0)
max_fanout	0 (0)	0	0 (0)
max_length	0 (0)	0	0 (0)

```

* Power View : Worst
*
* User-Defined Activity : N.A.
*
* Activity File: N.A.
*
* Hierarchical Global Activity: N.A.
*
* Global Activity: N.A.
*
* Sequential Element Activity: N.A.
*
* Primary Input Activity: 0.200000
*
* Default icg ratio: N.A.
*
* Global Comb ClockGate Ratio: N.A.
*
* Power Units = 1mW
*
* Time Units = 1e-09 secs
*
* report_power

```

```

Total Power
-----
Total Internal Power:      0.04747067      90.0866%
Total Switching Power:    0.00449045      8.5217%
Total Leakage Power:      0.00073336      1.3917%
Total Power:              0.05269448

```

- In case of any Violating paths, the design could be optimized in the following way.
- To optimize the Design, **Select ECO → Optimize Design → Design Stage [PreCTS] → Optimization Type – Setup → OK**



- After you run the optimization, the terminal displays the latest Timing report and updated area and power reports can be checked.
- This step Optimizes your design in terms of Timing, Area and Power. You can GenerateTiming, Area, Power in similar way as above report Post – Optimization to compare theReports.


### Clock Tree Synthesis

- The CTS Stage is meant to build a Clock Distribution Network such that every Register (Flip Flop) acquires Clock at the same time (Atleast Approximately) to keep them in propercommunication.
- A Script can be used to Build the Clock Tree as follows :

```
extractRC
```

```
add_ndr -width {Metal1 0.12 Metal2 0.14 Metal3 0.14 Metal4 0.14 Metal5 0.14 Metal6 0.14 Metal7 0.14 Metal8 0.14 Metal9 0.14 } -spacing {Metal1 0.12 Metal2 0.14 Metal3 0.14 Metal4 0.14 Metal5 0.14 Metal6 0.14 Metal7 0.14 Metal8 0.14 Metal9 0.14 } -name 2w2s
create_route_type -name clkroute -non_default_rule 2w2s -bottom_preferred_layer Metal5 -top_preferred_layer Metal6
set_ccopt_property route_type clkroute -net_type trunk
set_ccopt_property route_type clkroute -net_type leaf
set_ccopt_property buffer_cells {CLKBUF8 CLKBUF12}
set_ccopt_property inverter_cells {CLKINV8 CLKINV12}
set_ccopt_property clock_gating_cells TLATNTSCA*
create_ccopt_clock_tree_spec -file ccopt.spec
```

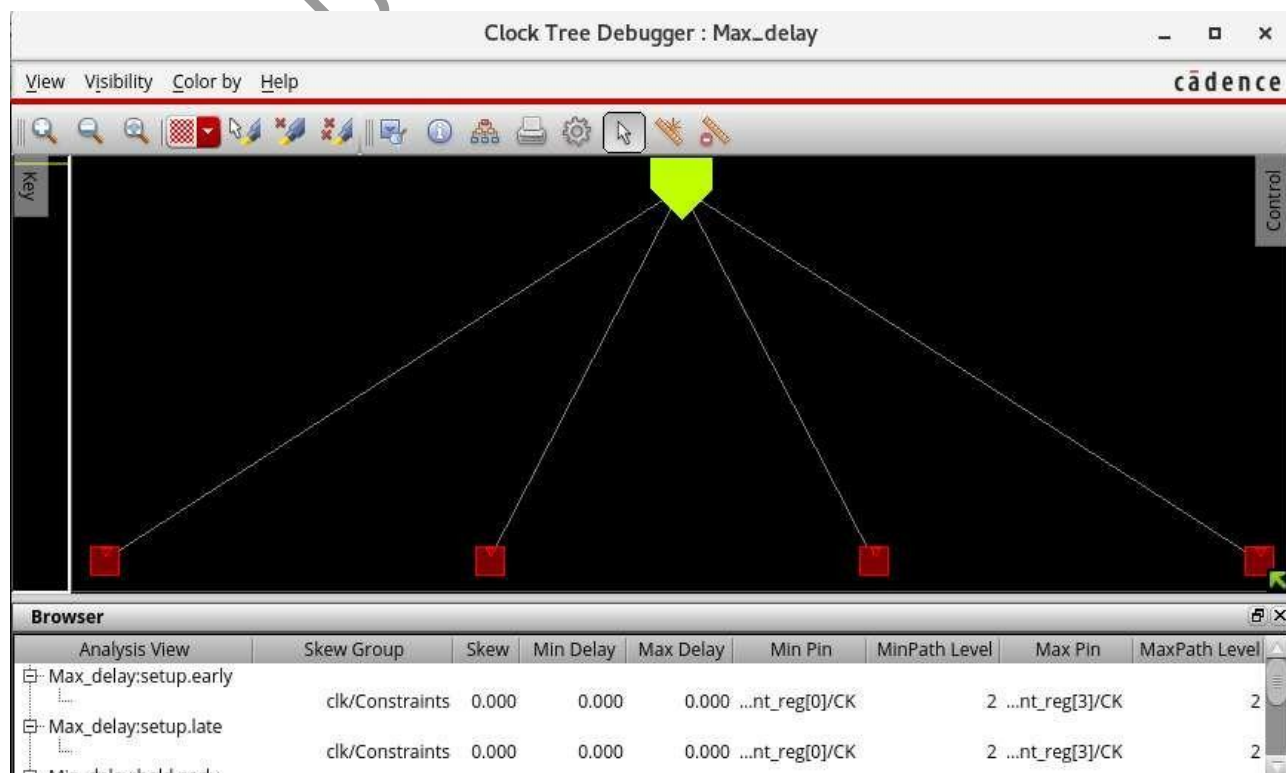
- Source the Script as shown in the above snapshot through the Terminal and then Select Clock → CCOpt Clock Tree Debugger → OK to build and view clock tree.



- The Red Boxes are the Clock Pins of various Flip Flops in the Design while Yellow Pentagon on the top represents Clock Source.
- The Clock Tree is built with Clock Buffers and Clock Inverters added to boost up the ClockSignal.

#### Report Generation and Design Optimization :

- CTS Stage adds real clock into the Design and hence “Hold” Analysis also becomes prominent. Hence, Optimizations can be done for both Setup & Hold, Timing Reports are to be Generated for Setup and Hold Individually.

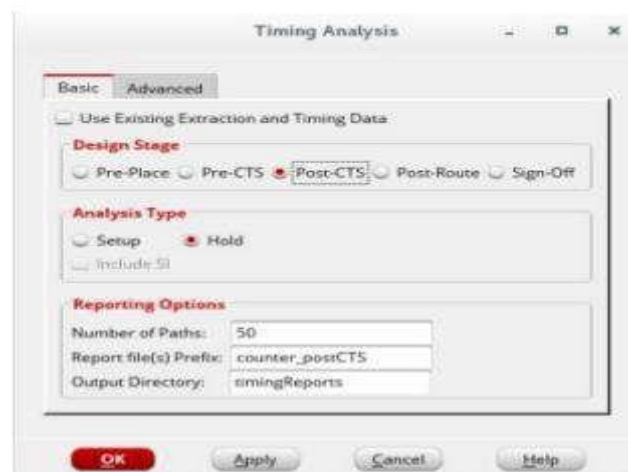Setup Timing Analysis :Hold Timing Analysis :

For Area and Power Report Generation,

**report\_area & report\_power** commands can be used.

Design Optimizations :

Routing :

1. All the net connections shown in the GUI till CTS are only based on the Logical connectivity.
2. These connections are to be replaced with real Metals avoiding Opens, Shorts, Signal Integrity [Cross Talks], Antenna Violations etc.
3. To run Routing, Select Route → Nano Route → Route and enable Timing Driven and SI Driven for Design Physical Efficiency and Reliability.

**NanoRoute**

**Routing Phase**

☒ Global Route

☒ Detail Route Start Iteration default End Iteration default

Post Route Optimization ☐ Optimize Via ☐ Optimize Wire

**Concurrent Routing Features**

☒ Fix Antenna ☐ Insert Diodes Diode Cell Name

☒ Timing Driven Effort 5 Congestion 1 Timing S.M.A.R.T.

☒ SI Driven

☐ Post Route SI SI Victim File

☐ Litho Driven

☐ Post Route Litho Repair

**Routing Control**

☐ Selected Nets Only Bottom Layer default Top Layer default

☐ ECO Route

☐ Area Route Area Select Area and Route

**Job Control**

☒ Auto Stop


Number of Local CPU(s): 1

Number of CPU(s) per Remote Machine: 1

Number of Remote Machine(s): 0

Set Multiple CPU...

**OK** Apply Attribute Mode... Save Load Cancel Help

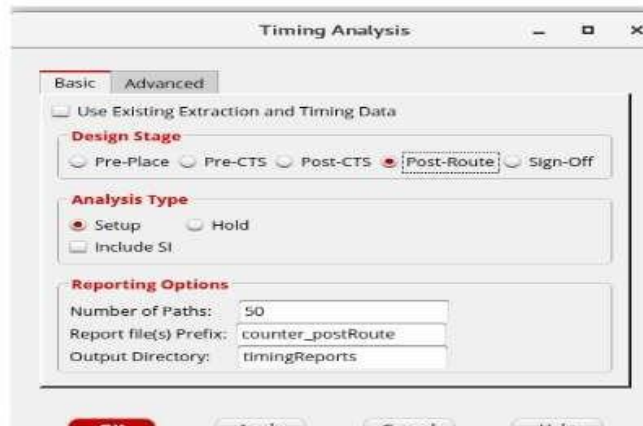**Report Generation and Design Optimization :****Setup Report :****Hold Report :****Area and Power Reports :**

Use the commands `report_area` and `report_power` for Area and PowerReports respectively.

**Design Optimization :**

```
innovus 5>
innovus 5> setAnalysisMode -analysisType onChipVariation -cpr both
innovus 6> 
```

Enter the above shown command in the Terminal in order to run the Design Optimization first Post-Route.



- As an alternate to the `setAnalysisMode` command, you can use the GUI at Tools → SetMode → Set Analysis Mode → Select On-Chip-Variation and CPPR.
- The Report generation is same as shown prior to Design Optimization.




## Saving Database :

1. Saving Design => File → Save Design → Data Type : Innovus → <DesignName>.enc → OK



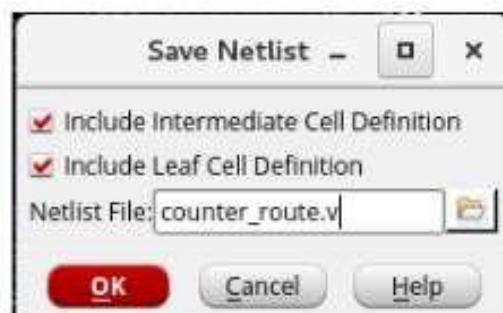2. Saving Netlist => File → Save → Netlist → <NetlistName>.v → OK



It is recommended to save Netlist and Design at every stage. To restore a Design Data Base, type source <DesignName>.enc in the terminal.

3. Saving GDS => File → Save → GDS/OASIS → <FileName>.gds → OK




## Physical Verification – Capturing DRC and LVS :


- After saving the routed Database, you can proceed for Physical Verification and capture the DRC and LVS reports.
- Inputs Required – DRC :
  - Technology Library and Rule Set
  - GDS format giles of all Standard Cells (Given by Cadence at /home/install/FOUNDRY/90nm/dig/gds for 90nm Tech node)
- Outputs – DRC :

- DRC Violation Report
- Physical Netlist (Optional)

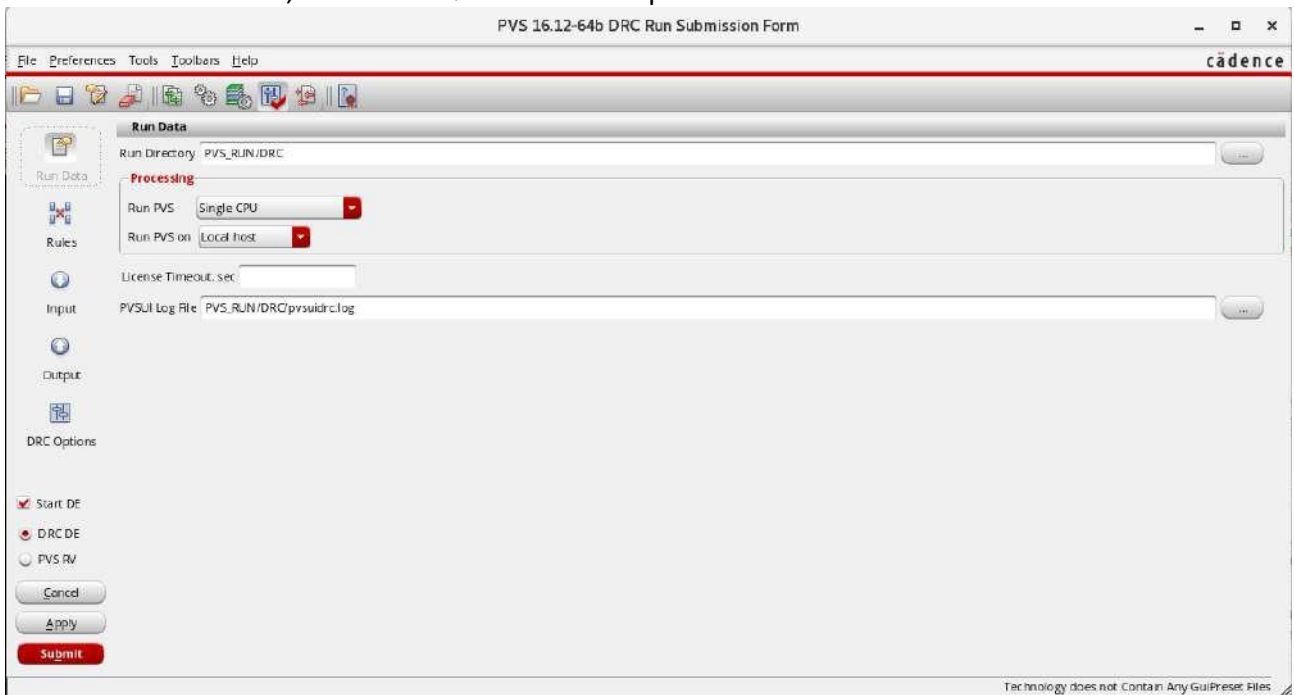From the Innovus GUI, select PVS → Run DRC to open the “DRC Submission Form”.



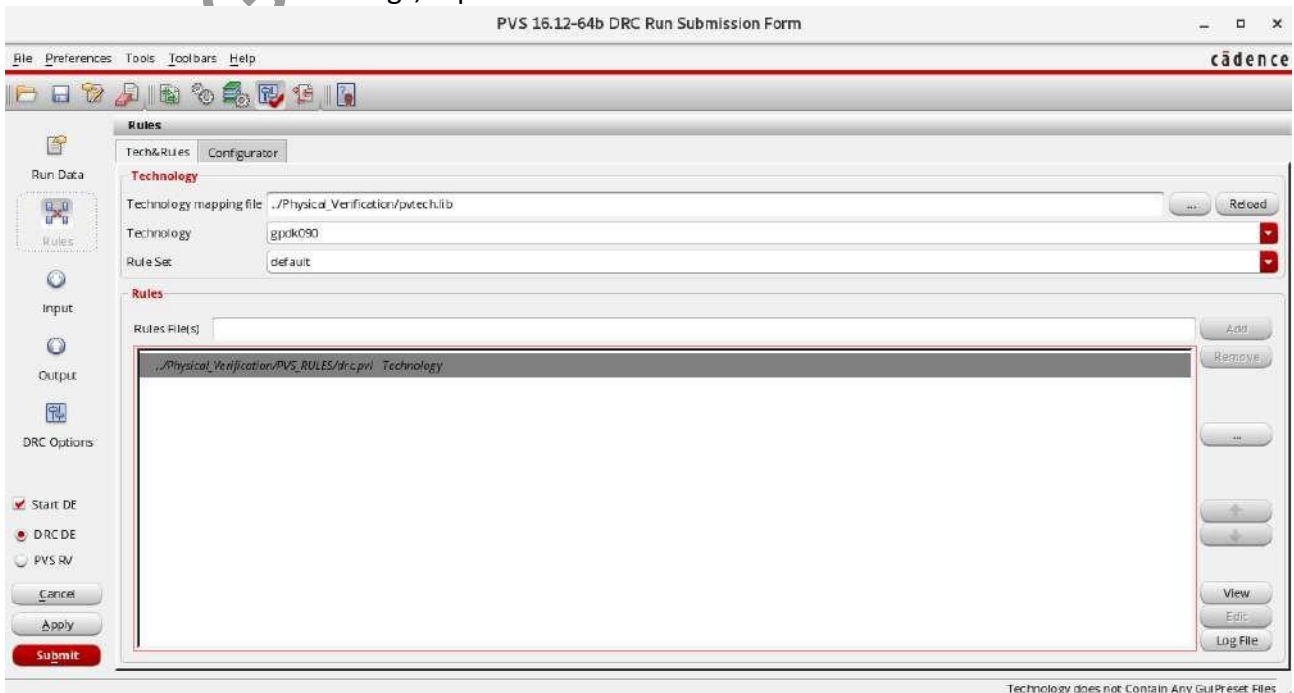The DRC Run Submission Form begins with mentioning the Run Directory. The Run Directory is the location where all the logs, reports and other files concerned with PVS are saved.




The technology Library is to be loaded under “Rules tab”.


- The Technology Library is specific for PVS Tool and technology node on which the design is created.
- On reading the tech lib, the rule set is loaded and the corresponding fabrication rules are read in to be checked against the design.



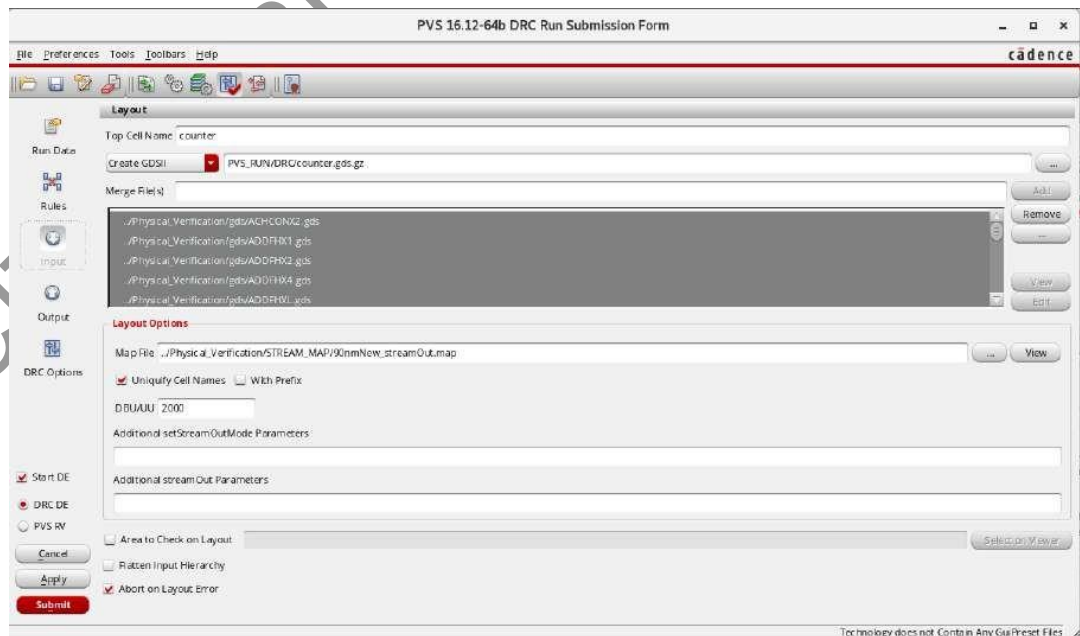- The GDS format files of all standard cells available with the corresponding technology node are also provided by the vendor. Select all of them to add.




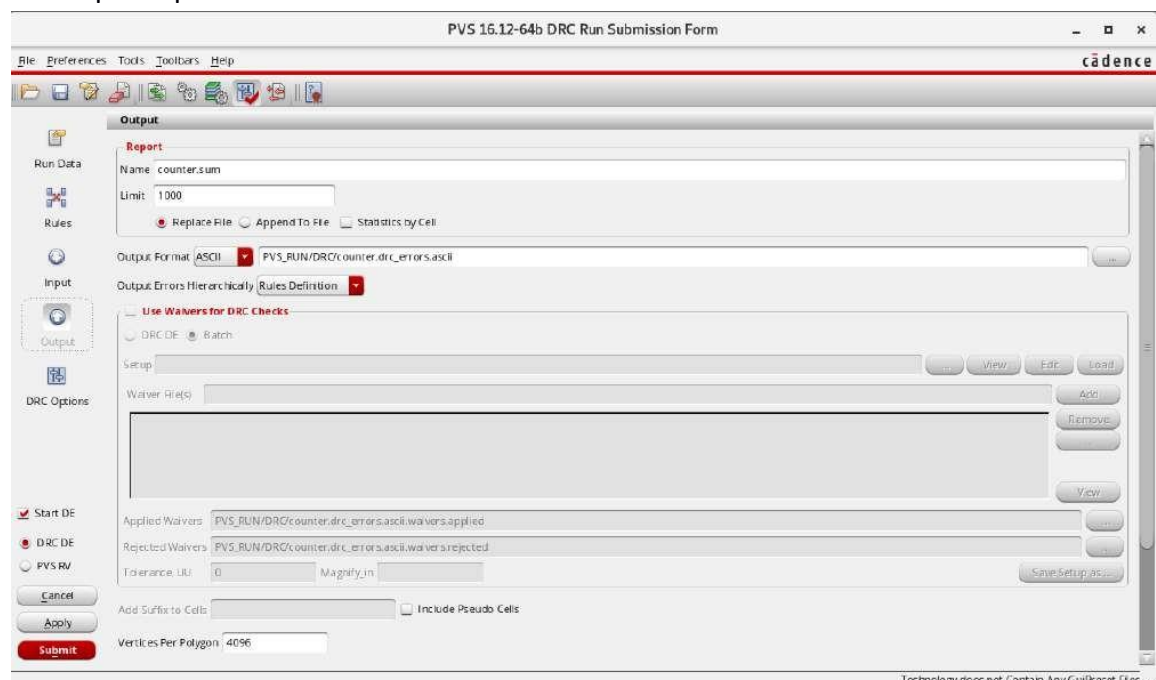- The output report can be named and saved as shown.







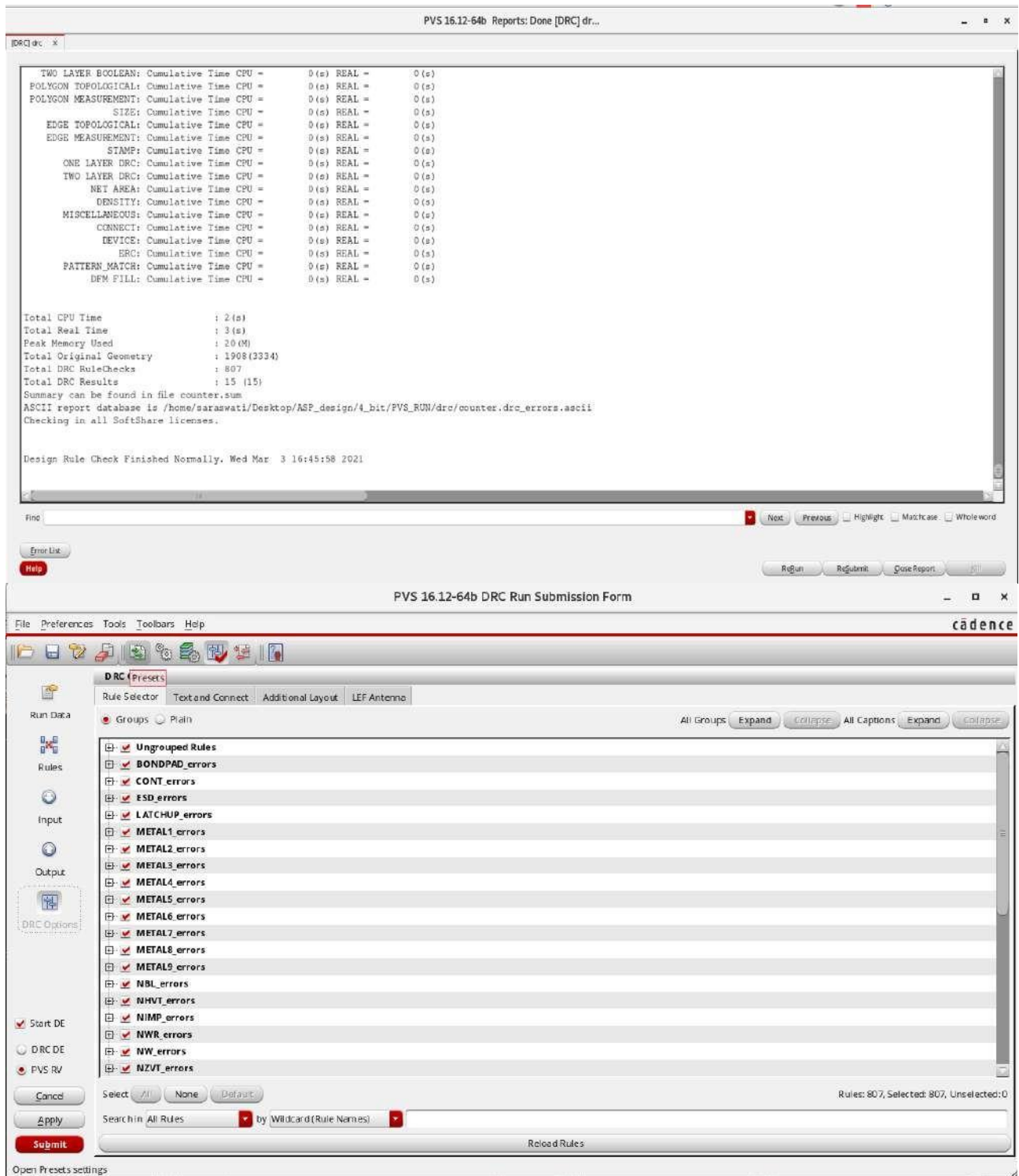- Hit "Submit" to run the DRC and the following windows appear.



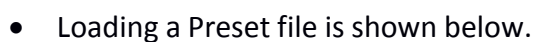 - All the list of DRC Errors can be seen in the above window of which the location of the DRC Violation occurring can be highlighted dealing one to one.



**Note :** A Physical Netlist can be saved after the DRC Run as shown below.

The image shows two windows. The top window is a terminal titled 'saraswati@saraswati:4\_bit'. It shows the following commands and output:

```

innovus 41>
innovus 41>
innovus 41>
innovus 41> saveNetlist -phys phy_netlist/counter_phy_netlist.v -includePowerGround -excludeLeafCell -excludeCellInst {FILL1 FILL2} -includePhysicalCell {FILL1 FILL2}
Writing Netlist "phy_netlist/counter_phy_netlist.v" ...
Pwr name (VDD).
Gnd name (VSS).
1 Pwr names and 1 Gnd names.
Creating all pg connections for top cell (counter).
innovus 42>

```

The bottom window is a text editor titled 'counter\_phy\_netlist.v'. It shows the netlist content generated by Cadence Innovus 17.14-s077.1. The netlist includes module declarations, internal wires, and module instantiations.

```

/*
#####
# Generated by: Cadence Innovus 17.14-s077.1
# OS: Linux x86_64(Host ID saraswati)
# Generated on: Wed Mar 3 17:06:55 2021
# Design: counter
# Command: saveNetlist -phys phy_netlist/counter_phy_netlist.v -includePowerGround -excludeLeafCell -excludeCellInst {FILL1 FILL2} -includePhysicalCell {FILL1 FILL2}
#####
*/
// Generated by Cadence Genus(TM) Synthesis Solution 17.22-s017.1
// Generated on: Mar 2 2021 13:56:16 IST (Mar 2 2021 08:26:16 UTC)
// Verification Directory fv/counter
module counter (
    count,
    control,
    reset,
    clk,
    VDD,
    VSS);
    output [3:0] count;
    input control;
    input reset;
    input clk;
    inout VDD;
    inout VSS;

    // Internal wires
    wire n_0;
    wire n_1;
    wire n_3;
    wire n_4;
    wire n_5;
    wire n_6;
    wire n_7;
    wire n_8;
    wire n_9;
    wire n_10;
    wire n_11;
    wire n_12;

    // Module instantiations
    SDFFRHQX1 \count_reg[3] (

```

- Inputs Required – LVS :
  - Technology Library
  - Standard Cell GDS Files
  - Spice Netlist of all Standard Cells (Provided by Library Vendor)
- Outputs – LVS :
  - LVS Match/Mismatch Report
- From the Innovus GUI, Select PVS → Run LVS to open the LVS run submission form.

The screenshot shows the 'Run Data' tab of the PVS 16.12-64b LVS Run Submission Form. The interface includes a menu bar (File, Preferences, Tools, Toolbars, Help) and a toolbar. On the left, there is a sidebar with icons for Run Data, Rules, Input, Output, and LVS Options. The main area is titled 'Run Data' and contains the following fields:

- Run Directory:** PVS\_RUN/LVS
- Processing:**
  - Run PVS:** Single CPU
  - Run PVS on:** Local host
- License Timeout, sec:** (empty field)
- Input:** PVSUI Log File: PVS\_RUN/LVS/pvsuilvs.log
- Output:** (empty field)
- LVS Options:** (empty field)

At the bottom left, there is a checkbox for 'Start LVS DE' which is checked. Below it are three buttons: 'Cancel', 'Apply', and 'Submit'. At the bottom right, a status bar indicates 'Technology does not Contain Any GuiPreset Files'.

- Provide the Run directory and log file name (Along with path – Optional)
- Load the Tech Lib, GDS Files and Spice Netlist of all Standard Cells under the corresponding technology node.

The screenshot shows the 'Rules' tab of the PVS 16.12-64b LVS Run Submission Form. The interface includes a menu bar (File, Preferences, Tools, Toolbars, Help) and a toolbar. On the left, there is a sidebar with icons for Run Data, Rules, Input, Output, and LVS Options. The main area is titled 'Rules' and contains the following fields:

- Tech&Rules:** Configurator, Include PVL
- Technology:**
  - Technology mapping file:** ../Physical\_Verification/pvtechlib
  - Technology:** gpd090
  - Rule Set:** default
- Rules:**
  - Rules File(s):** ../Physical\_Verification/PVS\_RULES/lvs.pvl Technology

At the bottom left, there is a checkbox for 'Start LVS DE' which is checked. Below it are three buttons: 'Cancel', 'Apply', and 'Submit'. At the bottom right, a status bar indicates 'Technology does not Contain Any GuiPreset Files'.

PVS 16.12-64b LVS Run Submission Form

File Preferences Tools Toolbars Help

cadence

Run Data Rules Input Output LVS Options

Start LVS DE ☒

Cancel Apply Submit

**Input**

Layout

Top Cell Name: counter

Create GDSII: PVS\_RUN/LVS/counter.gds.gz

Merge File(s):

- ../Physical\_Verification/gds/ACHCONX2.gds
- ../Physical\_Verification/gds/ADDFHX1.gds
- ../Physical\_Verification/gds/ADDFHX2.gds
- ../Physical\_Verification/gds/ADDFHX4.gds
- ../Physical\_Verification/gds/ADDFHXL.gds

Layout Options

Map File: ../Physical\_Verification/STREAM\_MAP/90nmNew\_streamOut.map

☒ Unify Cell Names ☐ With Prefix

DBU/UM: 2000

Additional setStreamOutMode Parameters:

Additional streamOut Parameters:

Create SPICE: PVS\_RUN/LVS/counter.spi

☒ Abort on Layout Error

Technology does not Contain Any GuiPreset Files

PVS 16.12-64b LVS Run Submission Form

File Preferences Tools Toolbars Help

cadence

Run Data Rules Input Output LVS Options

Start LVS DE ☒

Cancel Apply Submit

**Input**

Create SPICE: PVS\_RUN/LVS/counter.spi

☒ Abort on Layout Error

**Schematic**

☐ Innovus ☒ Netlist

☐ Check Schematic

Top Cell Name: counter

Netlist File(s) Type: SPICE

- SPICE: ../Physical\_Verification/Spice\_Netlist/all.spi
- Verilog: ../Physical\_Verification/Phys\_Netlist/design\_phyNetlist.v

CPF File:

Technology does not Contain Any GuiPreset Files



PVS 16.12-64b LVS Run Submission Form

File Preferences Tools Toolbars Help

cadence

**Output**

**H-Cell Settings**

☒ Automatch

☐ HCell

☐ GenHier Cells

☒ Run ERC Checks

**ERC Report**

Name: counter.sum

Limit: 1000

☒ Replace File ☐ Append To File ☐ Statistics by Cell

Output Format: ASCII PVS\_RUN/LVS/counter\_erc\_errors.asci

Output Errors Hierarchically: Rules Definition ☐ Output Complete Pathchk Results

☐ Use Waivers for ERC Checks

**LVS Report**

Name: counter.rep

Options: -none

Limit: 50 Mismatched Nets Limit: 100

**Additional Output**

☐ Create Quantus QRC Input Data

QRC Data DIR: sydb

Start LVS DE ☒

Cancel Apply Submit

Keep Layers: None

Technology does not Contain Any GuiPreset Files

- On successful completion of LVS Run, the following windows appear.

Applications Places PVS 16.12-64b LVS Run Status

PVS 16.12-64b Reports: Done [LVS] LV...

PVS 16.12-64b LVS Run Status

Run Summary

Total CPU Time : 1(s)

Total Real Time : 5(s)

Peak Memory Used : 228.90(M)

LVS Summary

Total CPU Time : 1(s)

Total Real Time : 8(s)

Peak Memory Used : 228.90(M)

Run Result : MATCH

Run Summary : [INFO] ERC Results: Empty

Run Summary : [INFO] Extraction Clean

ERC Summary File : counter.sum

Extraction Report File : counter.rep

Comparison Report File : counter.rep.cls

Checking in all SoftShare licenses.

PVS Comparison Finished. Wed Mar 3 17:09:30 2021

Find

Next Previous Highlight Matchcase Whole word

Error List

Help

Run Run Submit Done Report

1/4

PVS 16.12-64b | LVS Debug Environment | LVS Run : LVS | Comparison

File View Zoom Errors Layout Schematic Options Tools Toolbars Help

cadence

Files ERC Extraction Comparison

Matched

Group by Cell

Group by Cell Category

PVS LVS COMPARISON SUMMARY

CELL MATCH STATISTICS

CELL MATCH SUMMARY

LVS RULES

SCFFHQ1

DIFFHQ1

CAI21X1

CAI22X1

NAND2K1

NAND3K1

NAND2K1

NOR2K1

PVS LVS COMPARISON SUMMARY

PVS LVS COMPARISON

Version : 16.12-m208

NVN Run Start : Wed Mar 3 17:09:45 2021

ERC Summary File : counter.sum

Extraction Report File : counter.rep

Comparison Report File : counter.rep.cls

Top Cell : counter <vs> counter

Run Result : MATCH

Run Summary : [INFO] ERC Results: Empty

Run Summary : [INFO] Extraction Clean

**PVS 16.12-64b | LVS Debug Environment | LVS Run : LVS | Comparison**

File View Zoom Errors Layout Schematic Options Tools Toolbars Help

Layout Schematic Fit and Zoom 0.60 Pan None

Files ERC Extraction Comparison

Matched Group by Cell Error Count Status Details

Group by Cell

- OA122X1
- NAND2X1
- NAND3BX1
- NAND2BX1
- NOR2X1
- CLKINVX1
- INVXL
- DFFRX1
- counter

STATISTICS INITIAL CORRESPONDENCES

**counter : STATISTICS**

Cell	Original lay : sch	Filtered lay : sch	Reduced lay : sch
CLKINVX1	2 : 2	2 : 2	2 : 2
DFFRHQX1	1 : 1	1 : 1	1 : 1
DFFRX1	1 : 1	1 : 1	1 : 1
INVXL	1 : 1	1 : 1	1 : 1
NAND2BX1	2 : 2	2 : 2	2 : 2
NAND2X1	2 : 2	2 : 2	2 : 2
NAND3BX1	1 : 1	1 : 1	1 : 1
NOR2X1	1 : 1	1 : 1	1 : 1
OA1211X1	1 : 1	1 : 1	1 : 1
OA122X1	1 : 1	1 : 1	1 : 1
SDFFRHX1	2 : 2	2 : 2	2 : 2

**PVS 16.12-64b Reports: Done [LVS] LV...**

Applications Places PVS 16.12-64b | LVS Debug Environment | LVS Run : LVS | Files

WED 17:11

**PVS 16.12-64b | LVS Debug Environment | LVS Run : LVS | Files**

File View Zoom Errors Layout Schematic Options Tools Toolbars Help

Layout Schematic Fit and Zoom 0.60 Pan None

Files ERC Extraction Comparison

Input Files

- Control File (pvsrunvts)
- Technology (gds2vts)
- Layout GDSII (vts2gds)
- Schematic Netlist (kts2pl)
- Schematic Netlist (count...)

Log Files

- PVS Job Log (pvsrunvts.log)

Output Files

- Comparison Report (count...)
- ERC Summary (counter...)
- Extracted Spice File (cou...)
- Comparison Report (cou...)

Report File Name : counter.rep  
 ERC Summary File : counter.sum  
 LVS Comparison Report : counter.rep.cls  
 LVS Softchk Report : counter.softchk  
 Layout Name : /home/saraswati/Desktop/ASP\_design/4\_bit/PVS\_RUN/LVS  
 User Name : saraswati  
 Creation Time : Wed Mar 3 17:09:38 2021  
 Current directory : /home/saraswati/Desktop/ASP\_design/4\_bit/PVS\_RUN/LVS  
 PVS Version : 16.12-s208 Thu Mar 22 23:09:45 EDT 2016

Find Next Previous Highlight Matchcase Whole word

Run Run Submit Done Report

Run Summary

Total CPU Time : 1(s)  
 Total Real Time : 5(s)  
 Peak Memory Used : 228.90(M)

LVS Summary

Total CPU Time : 1(s)  
 Total Real Time : 8(s)  
 Peak Memory Used : 228.90(M)

Run Result : MATCH

Run Summary : [INFO] ERC Results: Empty  
 Run Summary : [INFO] Extraction Clean

ERC Summary File : counter.sum  
 Extraction Report File : counter.rep  
 Comparison Report File : counter.rep.cls

Checking in all SoftShare licenses.

PVS Comparison Finished, Wed Mar 3 17:09:50 2021

Find Error List Help

/home/saraswati/Desktop/ASP\_design/4\_bit/PVS\_RUN/LVS

[inbox - saraswati@centos] [pvs\_netlist] [saraswati@centos:~] [innoset(TM) Implementatio...] [PVS 16.12-64b LVS Run Su...] [PVS 16.12-64b Reports: D...] [PVS 16.12-64b | LVS De...] 1/4

**PVS 16.12-64b | LVS Debug Environment | LVS Run : LVS | ERC**

File View Zoom Errors Layout Schematic Options Tools Toolbars Help

Layout Schematic Fit and Zoom 0.60 Pan None

Files ERC Extraction Comparison

Group by Category Error Count


- PVS ERC SUMMARY
- ORIGINAL LAYER STATISTICS
- FLAG STATEMENT WARNINGS
- RULECHECK RESULTS STATISTICS
- RUN SUMMARY

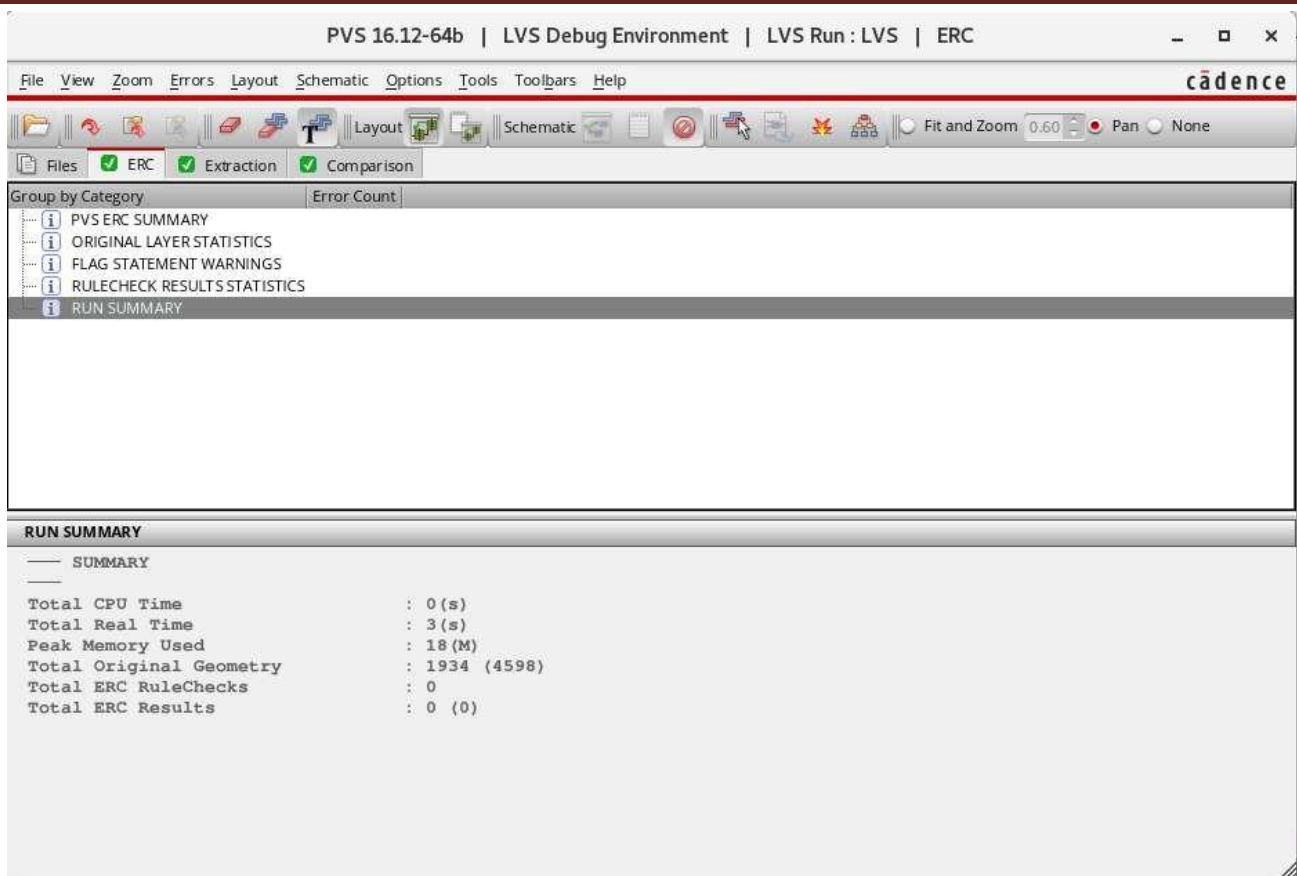**RUN SUMMARY**

SUMMARY

Total CPU Time : 0 (s)  
 Total Real Time : 3 (s)  
 Peak Memory Used : 18 (M)  
 Total Original Geometry : 1934 (4598)  
 Total ERC RuleChecks : 0  
 Total ERC Results : 0 (0)





- You can create a GDS file along with Stream out file either using the GUI as File → Save → GDS/Oasis or use the following command.
- **Cmd** : streamOut <GDSFileName>.gds -streamOut <streamOut>.map